
Induction Motors Drive: Other Considerations


- Start-Up
- Capabilities
- Generator Mode
- Harmonics


Induction Motor Drives : Speed Control

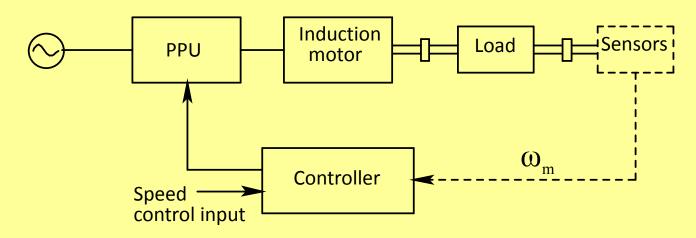


- ☐ Efficient speed control over a wide range
 - Reduced voltage control (inefficient)
 - Frequency control (efficient)
- ☐ PPU drives induction motor with variable frequency to maintain low slip
- ☐ As frequency decreases, voltage must also decrease to avoid magnetic saturation

Start-up Considerations

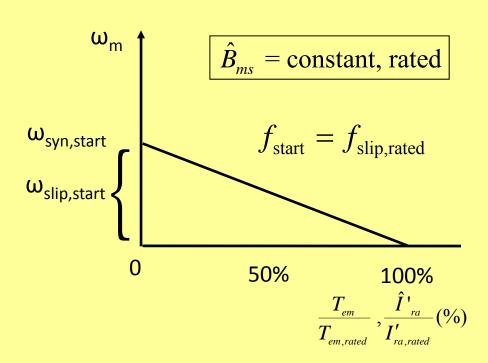

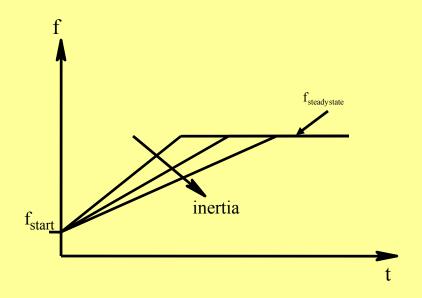


Capability Below and Above Rated Speed

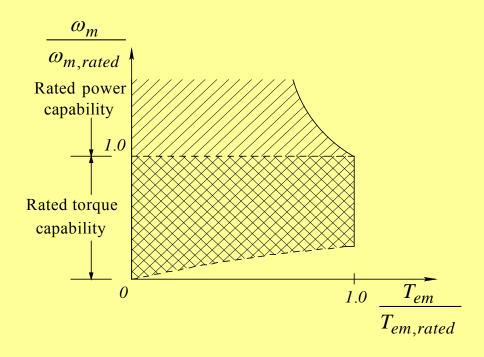


- lacktriangle Voltages limited to rated values, therefore \hat{B}_{ms} declines at higher speeds (Flux Weakening)
- Currents limited to rated values, therefore torque declines when \hat{B}_{ms} declines

Generator Mode

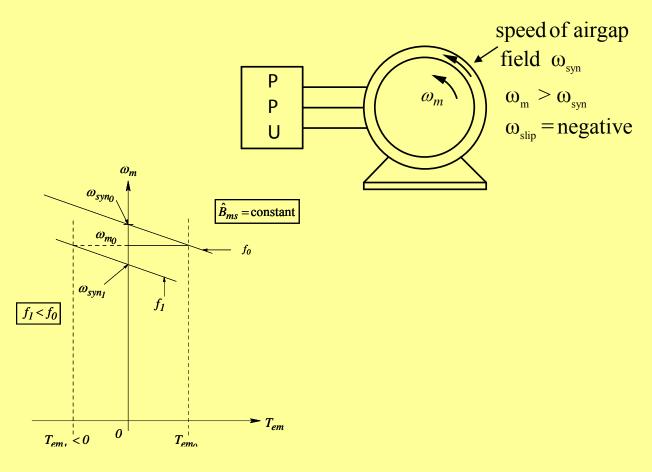

- $\hfill \Box$ To initiate braking, lower ω_{syn} to some value less than ω_{m}
- ☐ Braking torque can be adjusted by setting the negative slip frequency


Speed Control of Induction Motor Drives

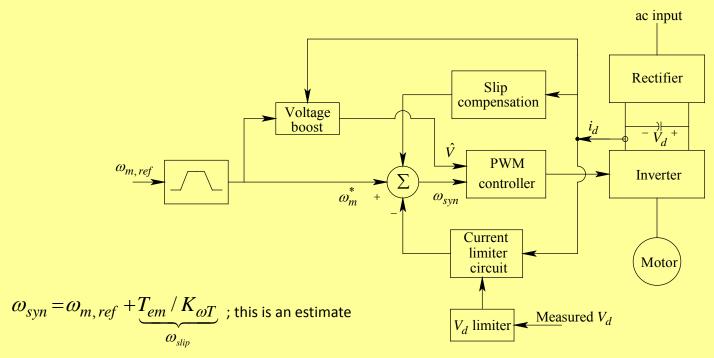


 $V_a = k_f f + k_{vT} T_{em}$


- $oxedsymbol{\square}$ $\omega_{m,ref}$ is passed through a rate limiter to avoid over driving the motor
- ☐ This method does not give precise speed control

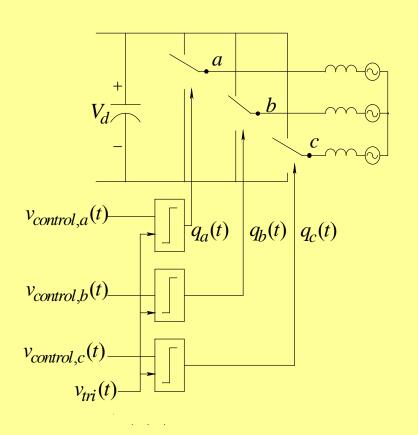
Pulse-Width-Modulated Power Processing Unit



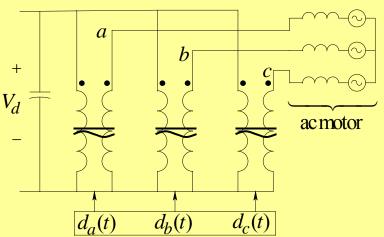


Harmonics in PPU

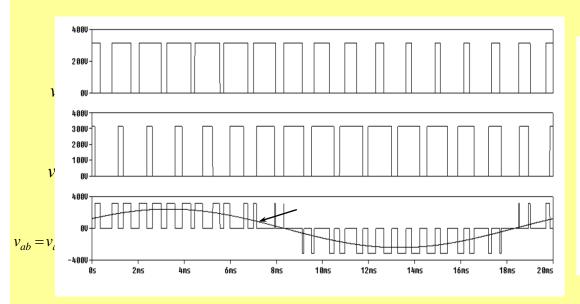

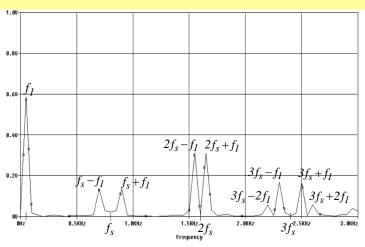


- ☐ PPU with switching frequency of 800 Hz generating a fundamental sine wave of 50 Hz
- ☐ Frequency spectrum shows large 50 Hz component and smaller components at higher frequencies due to switching
- ☐ These higher frequency components add to the losses in the motor

PPU – Supplied Induction Motor

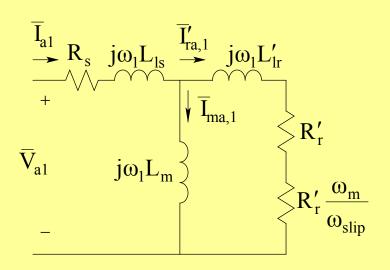

Fundamental Frequency Model

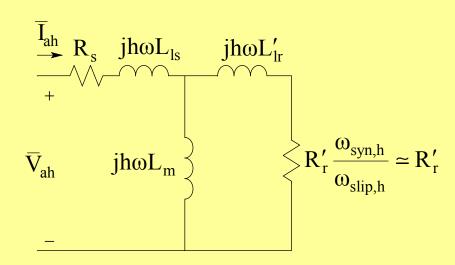



Harmonic Frequency Model

At harmonic frequencies $R_{eq} \simeq R'_r$ Magnetizing inductance can be ignored Harmonic currents controlled by leakage inductance

$$\hat{\mathbf{I}}_{ah} \simeq \frac{\hat{\mathbf{V}}_{ah}}{(\mathbf{X}_{ls,h} + \mathbf{X}'_{lr,h})}$$

PPU – Supplied Induction Motor Model

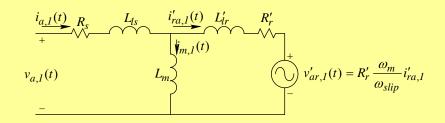

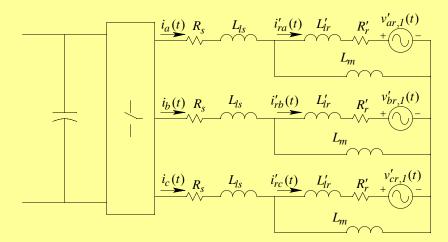

☐ Fundamental frequency drop across resistor replaced with AC voltage source

Summary

- Start-Up
- Capabilities
- Generator Mode
- Harmonics