

Transformers

- Transformers
 - Basic Principle
 - Equivalent Circuit
 - Parameter Estimation
- Permanent Magnets

Transformers

- Tightly coupled coils (low leakage inductance)
- Essential for power transmission and distribution
- Helpful in understanding induction machines

Transformers - Development

□ Single coil

Assuming zero resistance and zero leakage inductance




$$e_1 = N_1 \frac{d\phi_m}{dt}$$

ϕ_m determined completely by applied voltage:


$$\phi_m = \frac{1}{N_1} \int e_1 d\tau$$

□ Two coils
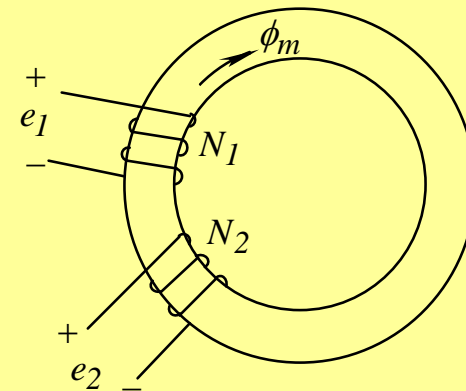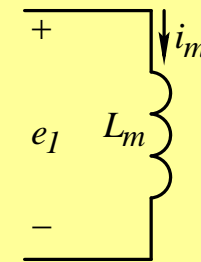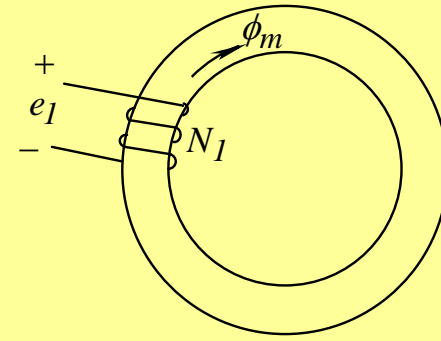
$$e_2(t) = N_2 \frac{d\phi_m}{dt} \quad \& \quad e_1(t) = N_1 \frac{d\phi_m}{dt}$$
$$\Rightarrow \frac{e_1(t)}{e_2(t)} = \frac{N_1}{N_2}$$



Transformer Model

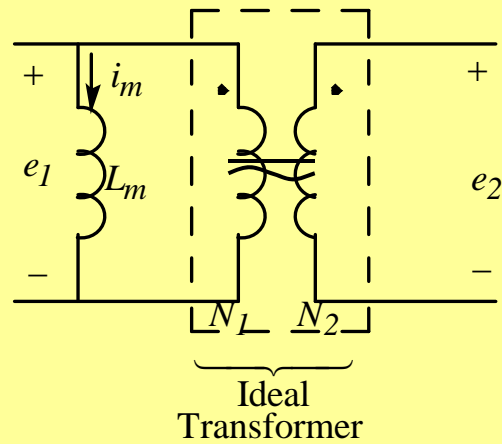

- Dot polarity
- Magnetizing inductance



Transformer with Secondary Loaded

- ϕ_m determined by e_1 alone
 hence i_2 in secondary induces
 i_2' in the primary such that

$$N_1 i_2' = N_2 i_2$$


$$\Rightarrow \frac{i_2'}{i_2} = \frac{N_2}{N_1}$$
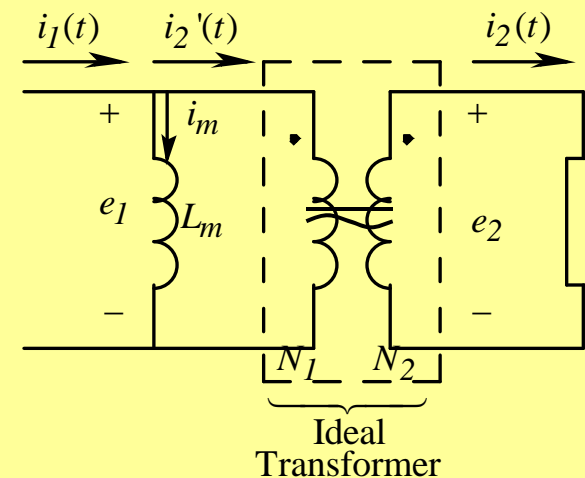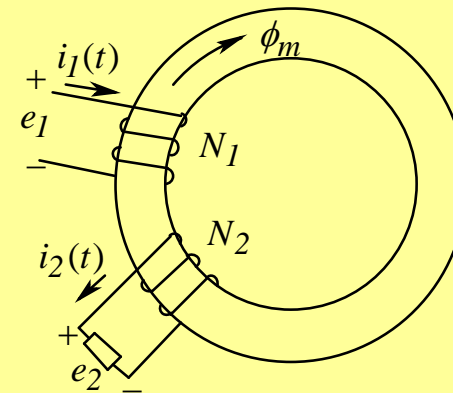
$$i_1(t) = \underbrace{i_2'(t)}_{\text{reflected load current}} + \underbrace{i_m(t)}_{\text{magnetizing current}}$$




Real Transformers

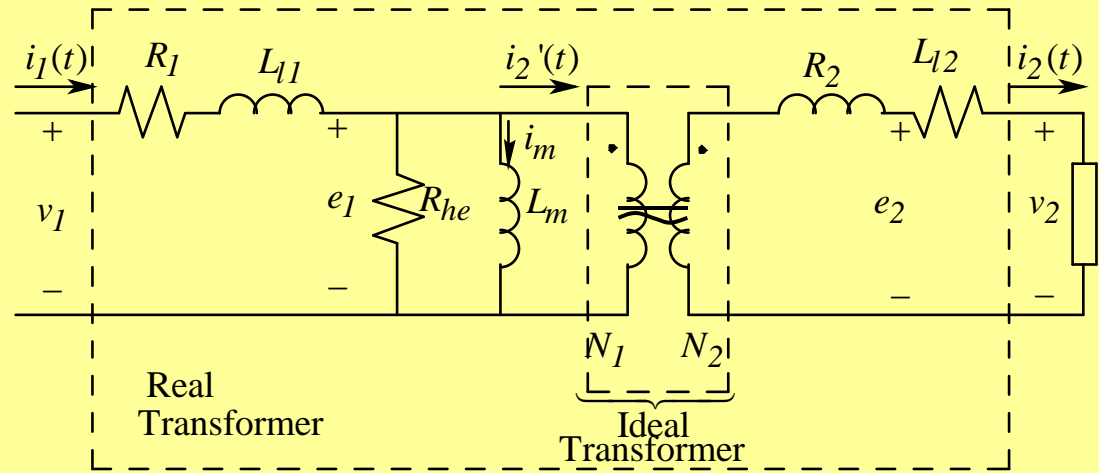
- Add leakages
- Core loss
 - hysteresis
 - eddy currents
- Winding resistances



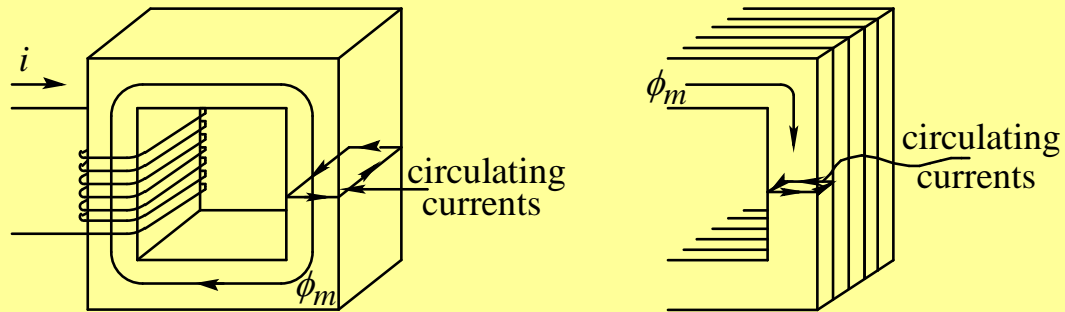- Laminations to reduce eddy current loss



Determining Transformer Model Parameters

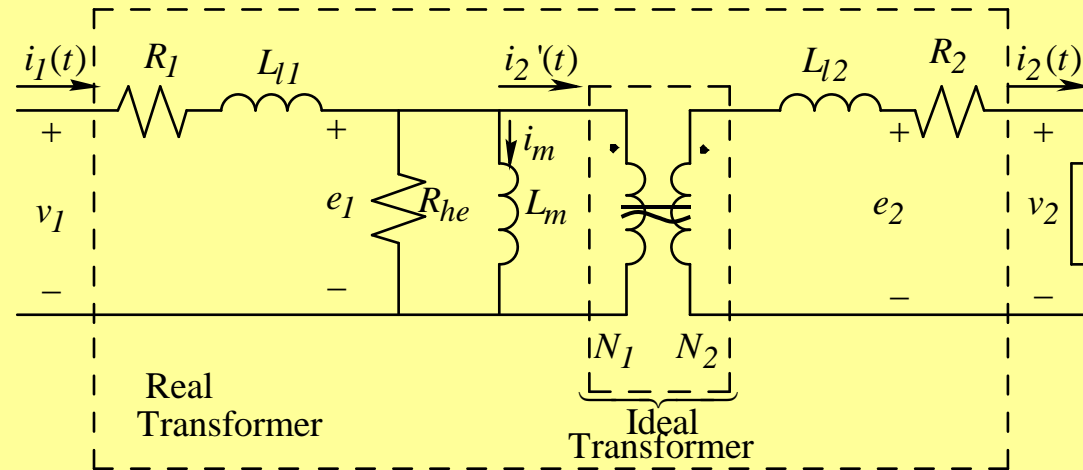

- Open circuit test
 - ◆ Core loss, R_{he}
 - ◆ Magnetizing inductance, L_m

- Short circuit test
 - ◆ Winding resistance, R_1, R_2
 - ◆ Leakage inductance, L_{l1}, L_{l2}

Open Circuit Test


- Secondary unloaded (open circuit)
- Rated voltage applied to primary
- Measure

◆ To find R_{he}

$$R_{he} = \frac{V_{oc}^2}{P_{oc}}$$

◆ To find L_m

$$|R_{he} || jX_m| = \frac{V_{oc}}{I_{oc}}$$

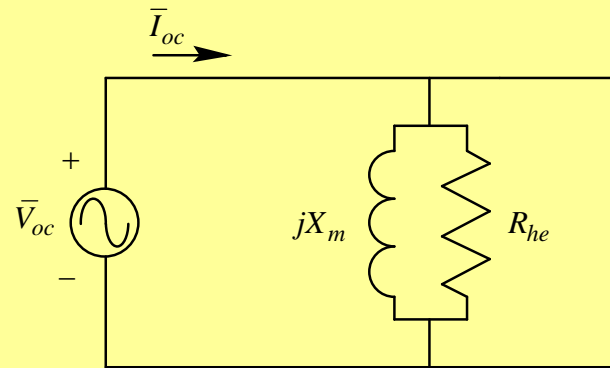


Short Circuit Test

- One winding shorted
 - small voltage applied to other winding
- Measure V_{SC} , and I_{SC} , and P_{SC}

◆ To find R_1 and R_2

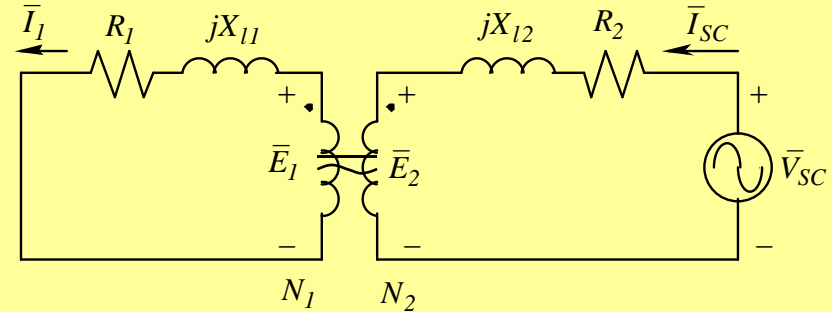
$$R_2 = \frac{1}{2} \frac{P_{SC}}{I_{SC}^2} \quad R_1 = R_2 \left(\frac{N_1}{N_2} \right)^2$$



◆ To find L_{l1} and L_{l2}


$$|2R_2 + j2X_{l2}| = \frac{V_{SC}}{I_{SC}}$$
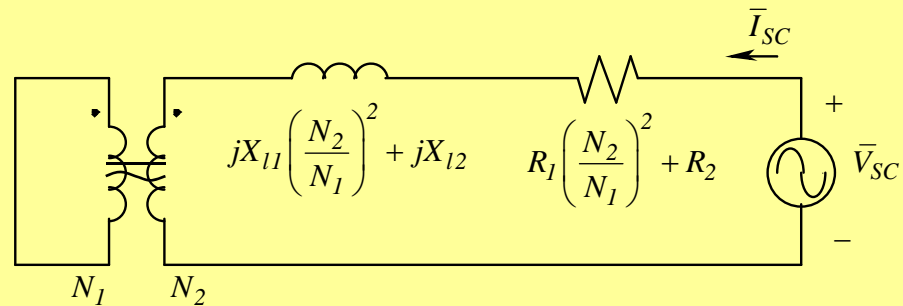
$$X_{l1} = X_{l2} \left(\frac{N_1}{N_2} \right)^2$$



Permanent Magnets

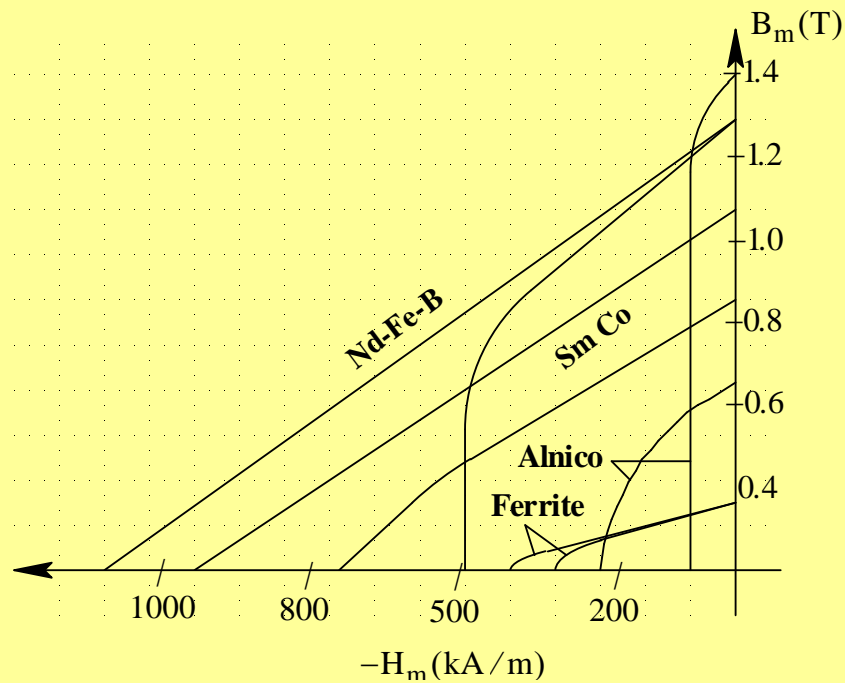- Typically used in smaller motors
- Applicable power range increasing due to new materials
- In simplest analysis, treated simply as a source of magnetic flux



Summary

- Transformers
 - Basic Principle
 - Equivalent Circuit
 - Parameter Estimation
- Permanent Magnets