

Clock Clear

Fig. 6-1 4-Bit Register

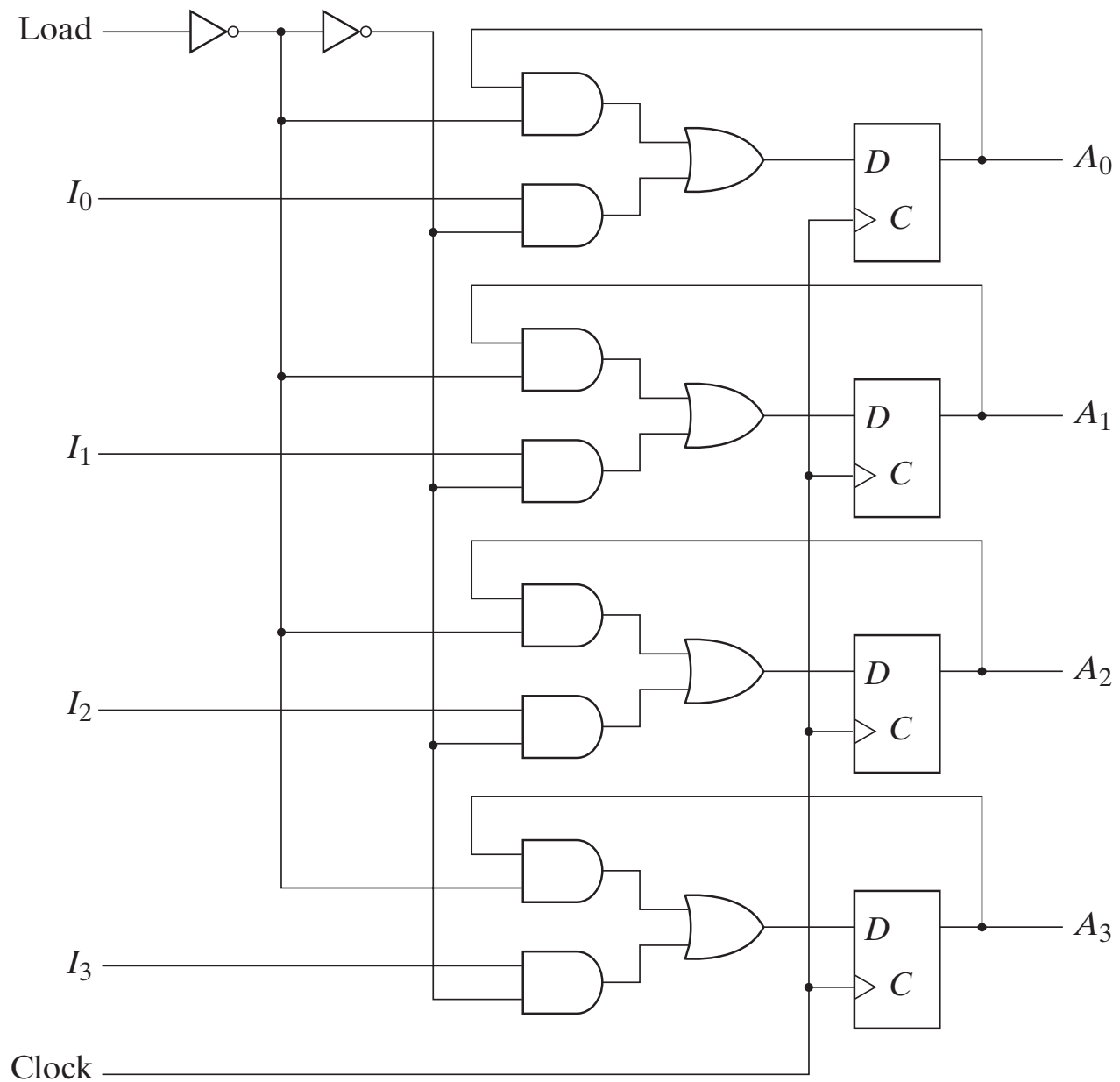


Fig. 6-2 4-Bit Register with Parallel Load



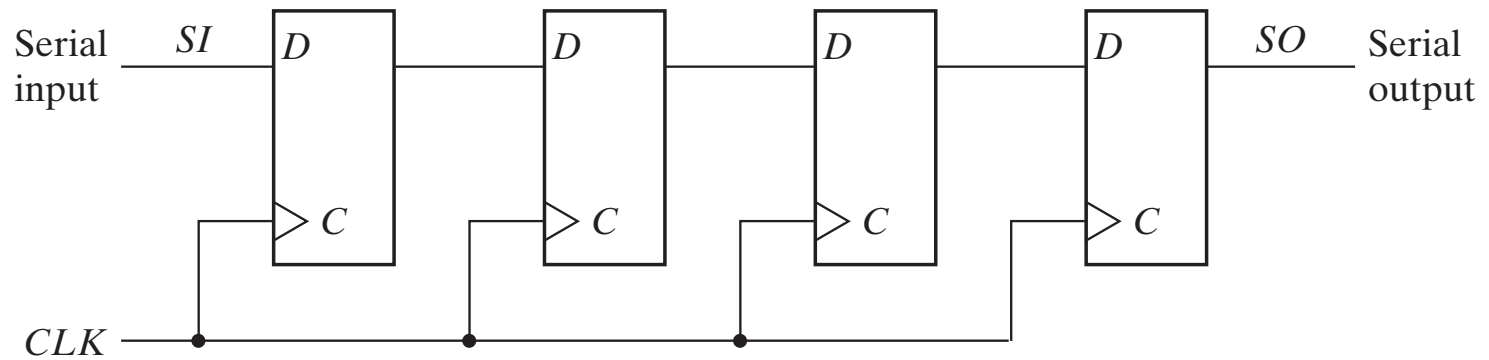


Fig. 6-3 4-Bit Shift Register

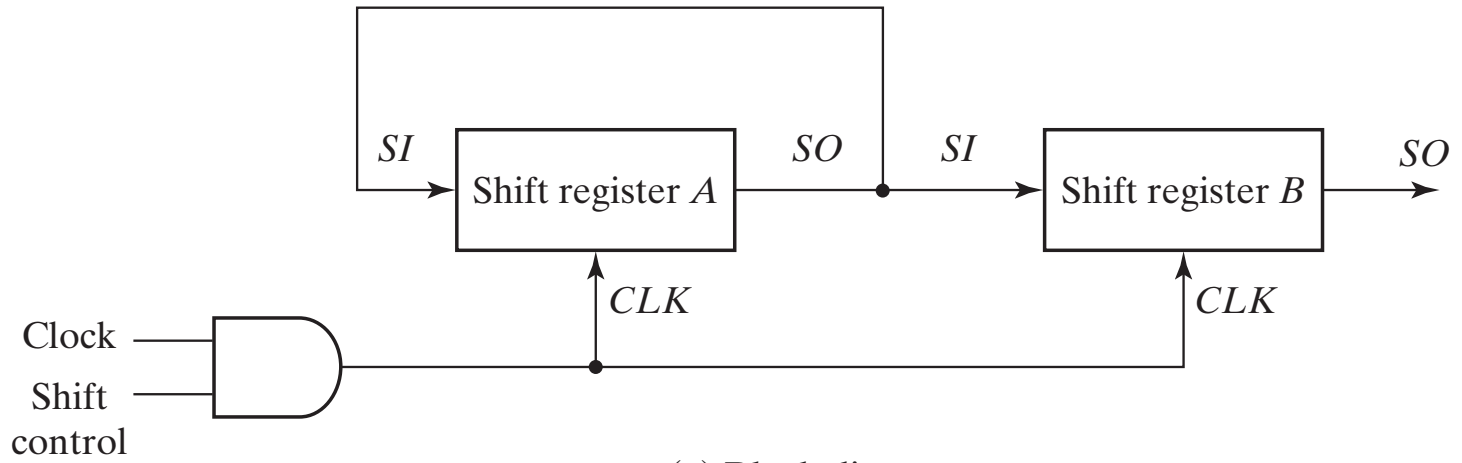

(a) Block diagram

 

(b) Timing diagram

Fig. 6-4 Serial Transfer from Register A to register B

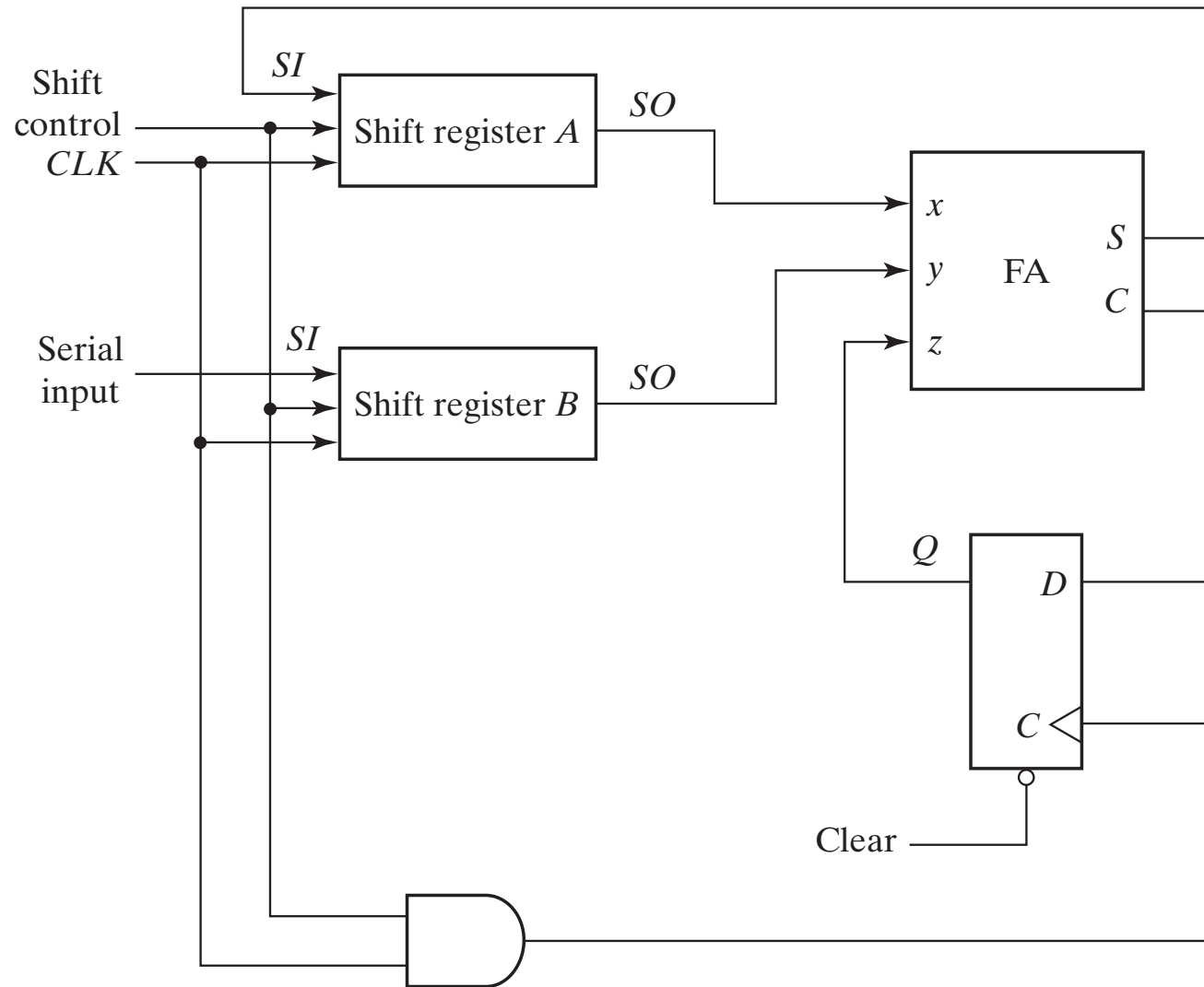


Fig. 6-5 Serial Adder

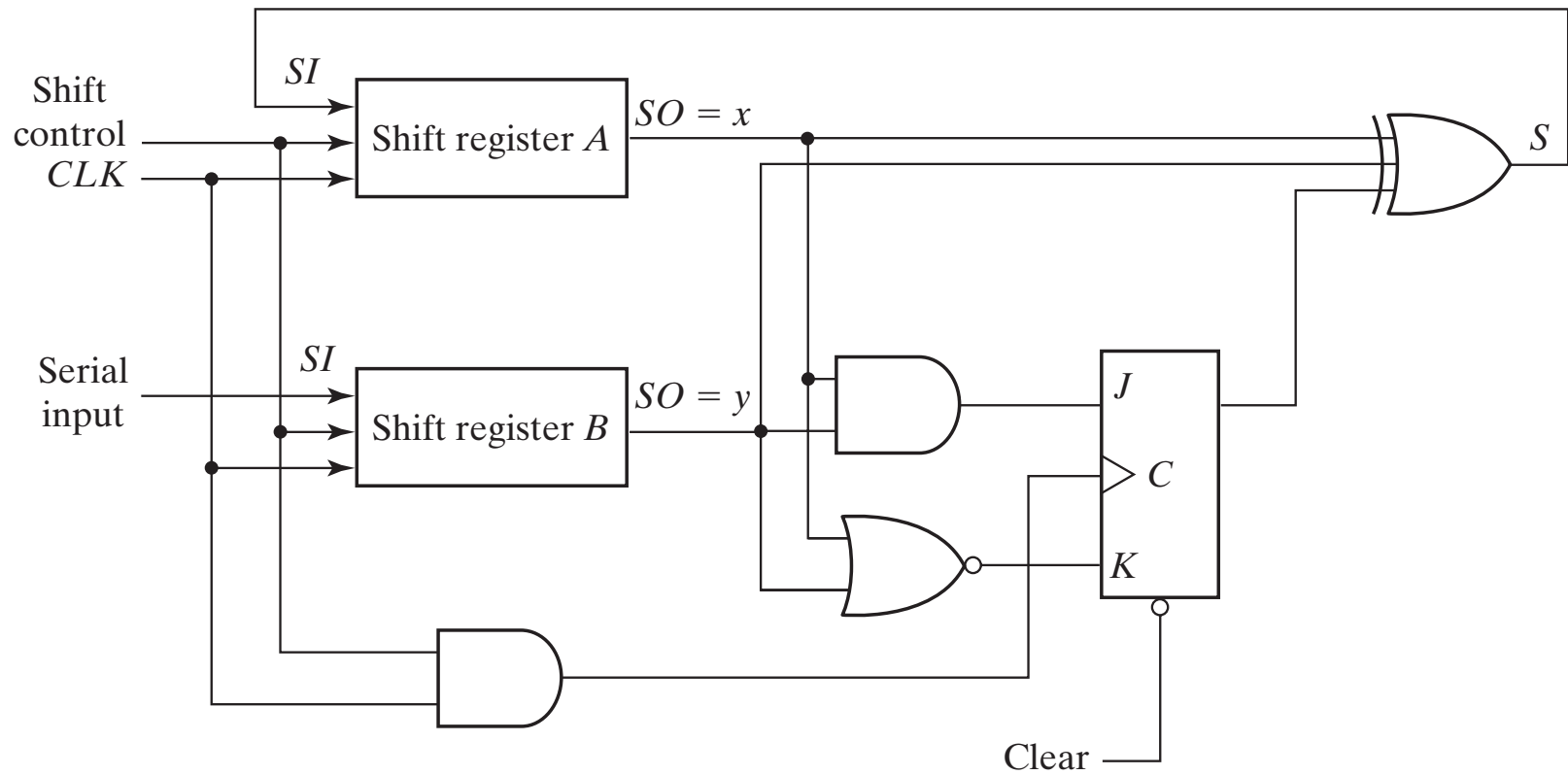


Fig. 6-6 Second form of Serial Adder



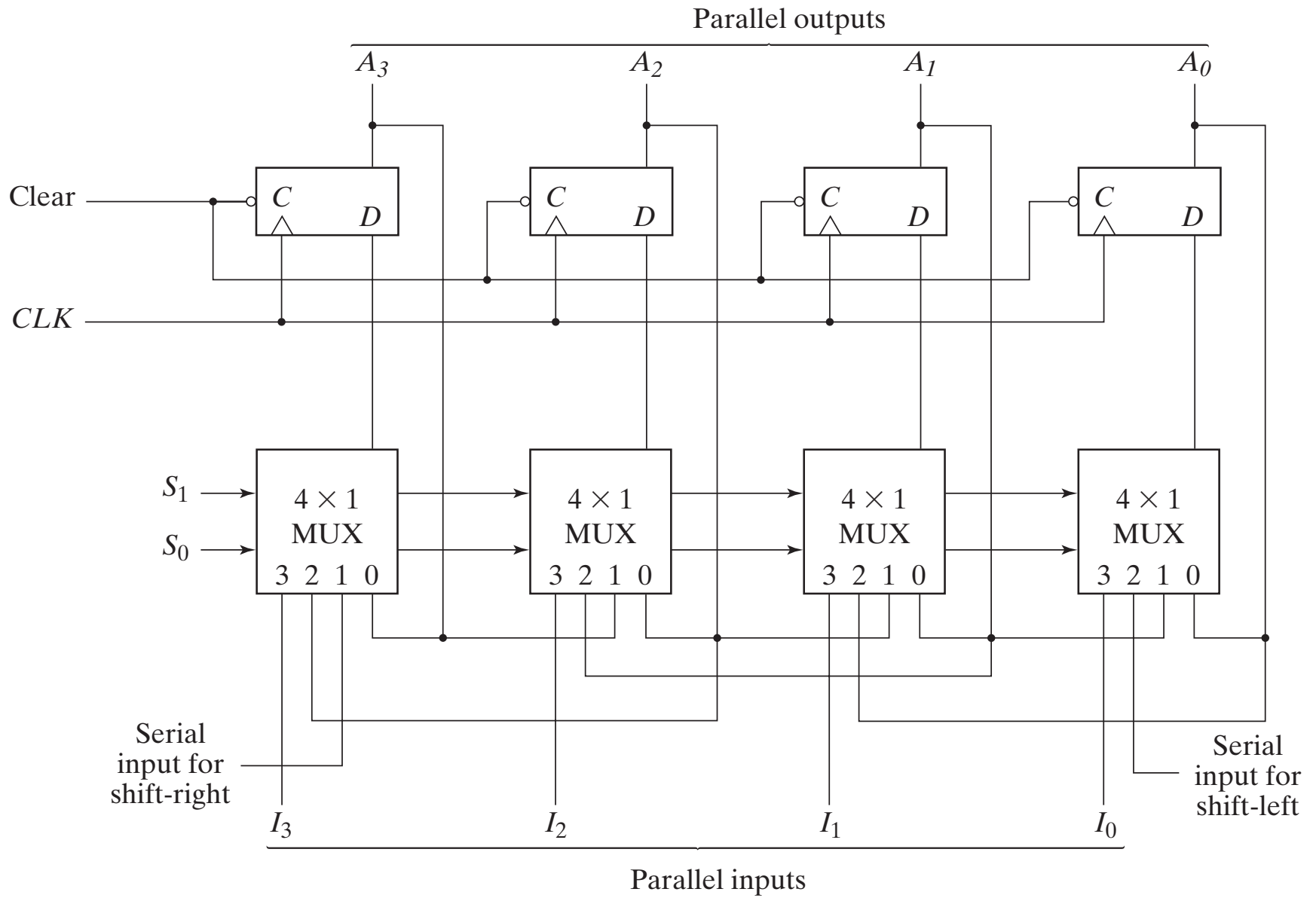


Fig. 6-7 4-Bit Universal Shift Register

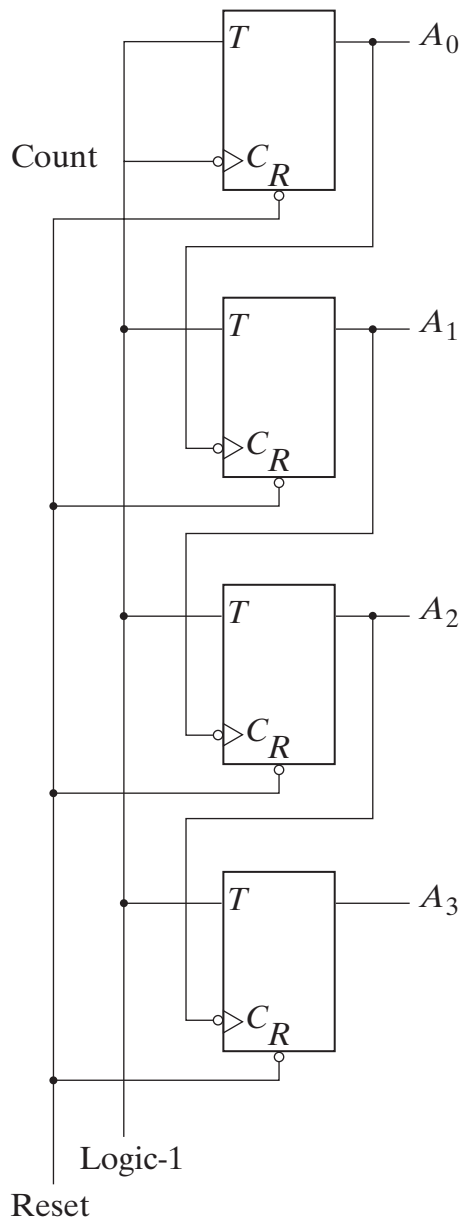

(a) With T flip-flops

 

(b) With D flip-flops

Fig. 6-8 4-Bit Binary Ripple Counter


 


Fig. 6-9 State Diagram of a Decimal BCD-Counter

 

Logic-1

Fig. 6-10 BCD Ripple Counter

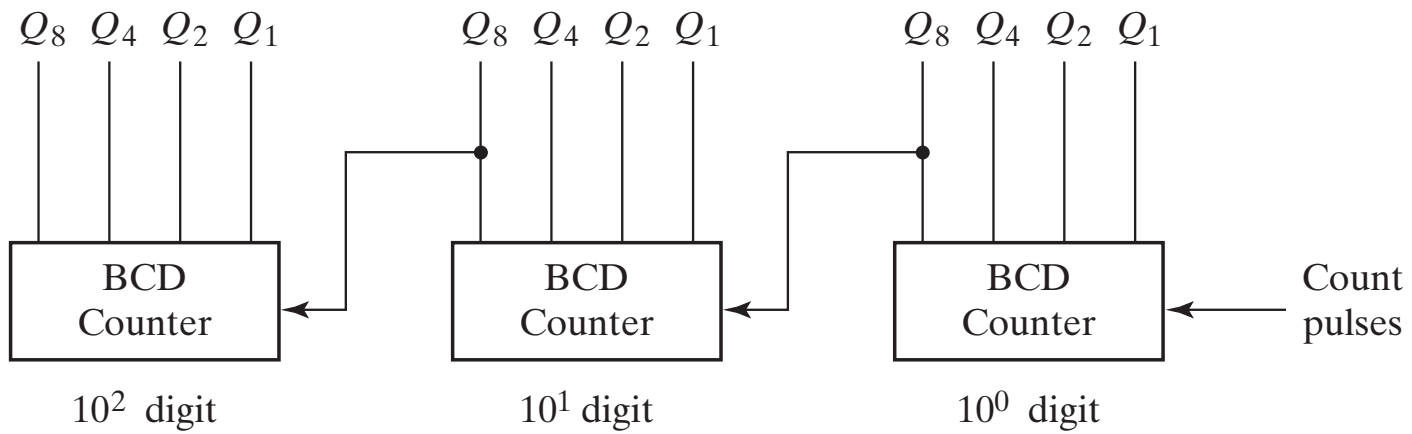


Fig. 6-11 Block Diagram of a Three-Decade Decimal BCD Counter

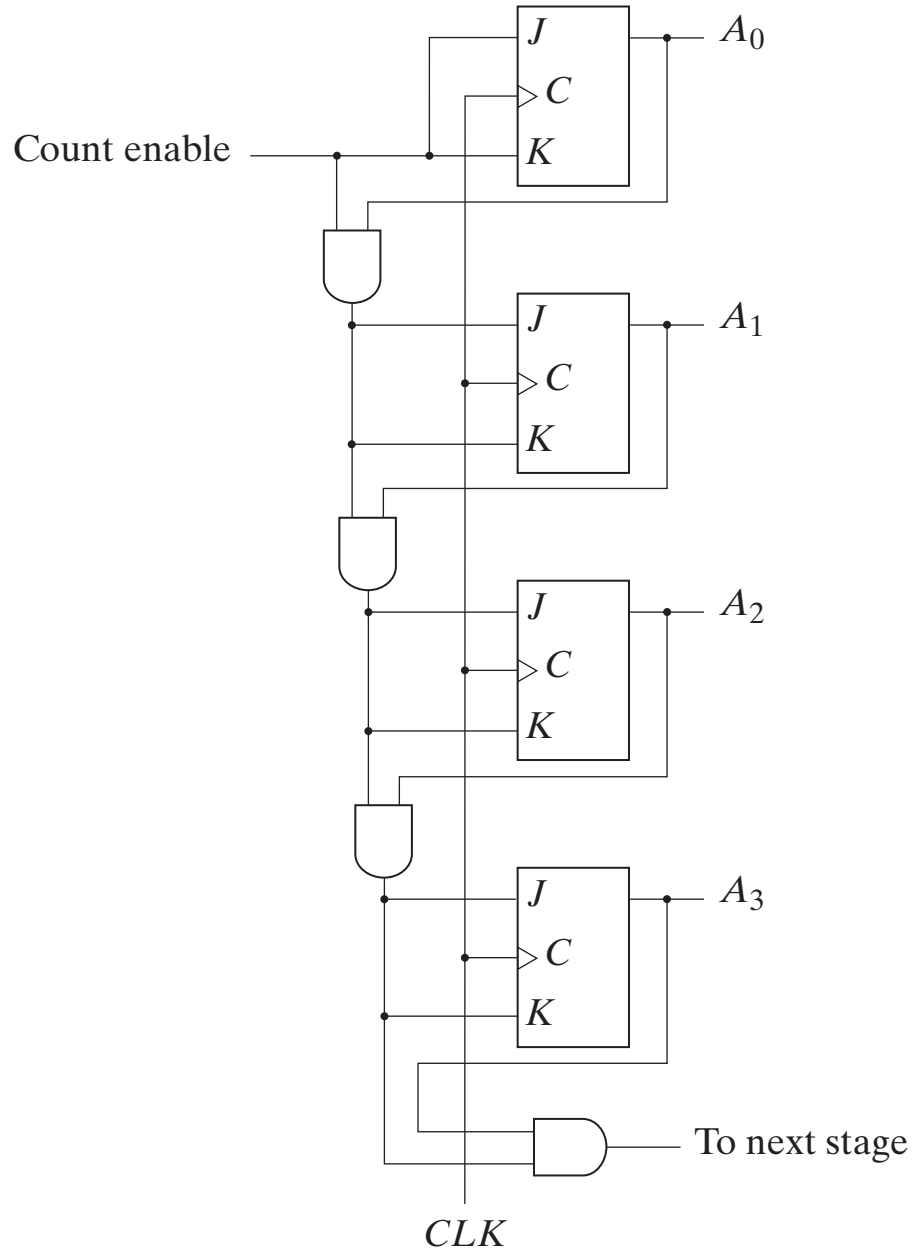


Fig. 6-12 4-Bit Synchronous Binary Counter

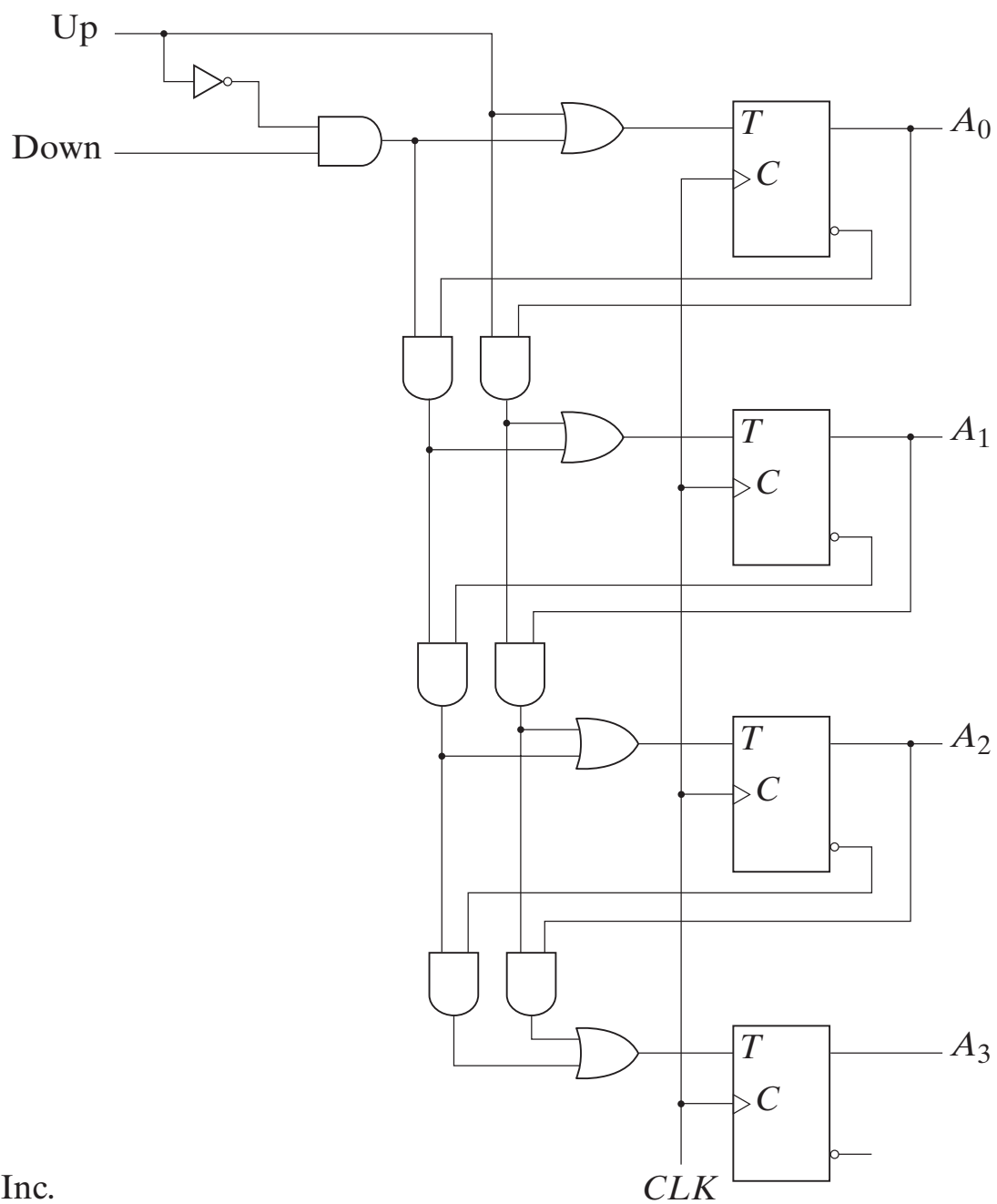


Fig. 6-13 4-Bit Up-Down Binary Counter



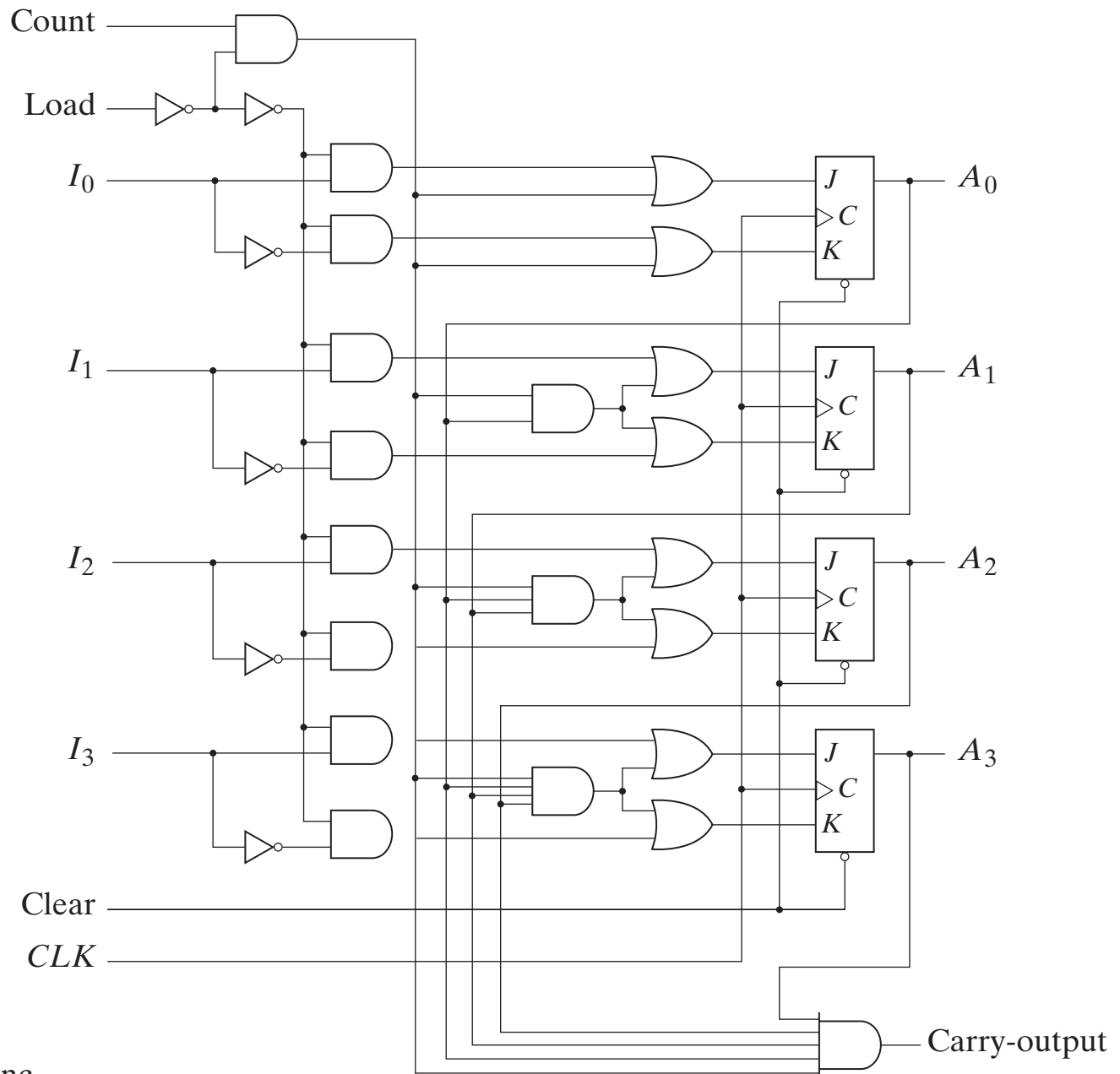


Fig. 6-14 4-Bit Binary Counter with Parallel Load

 

(a) Using the load input

 

(b) Using the clear input

Fig. 6-15 Two ways to Achieve a BCD Counter Using a Counter with Parallel Load



 
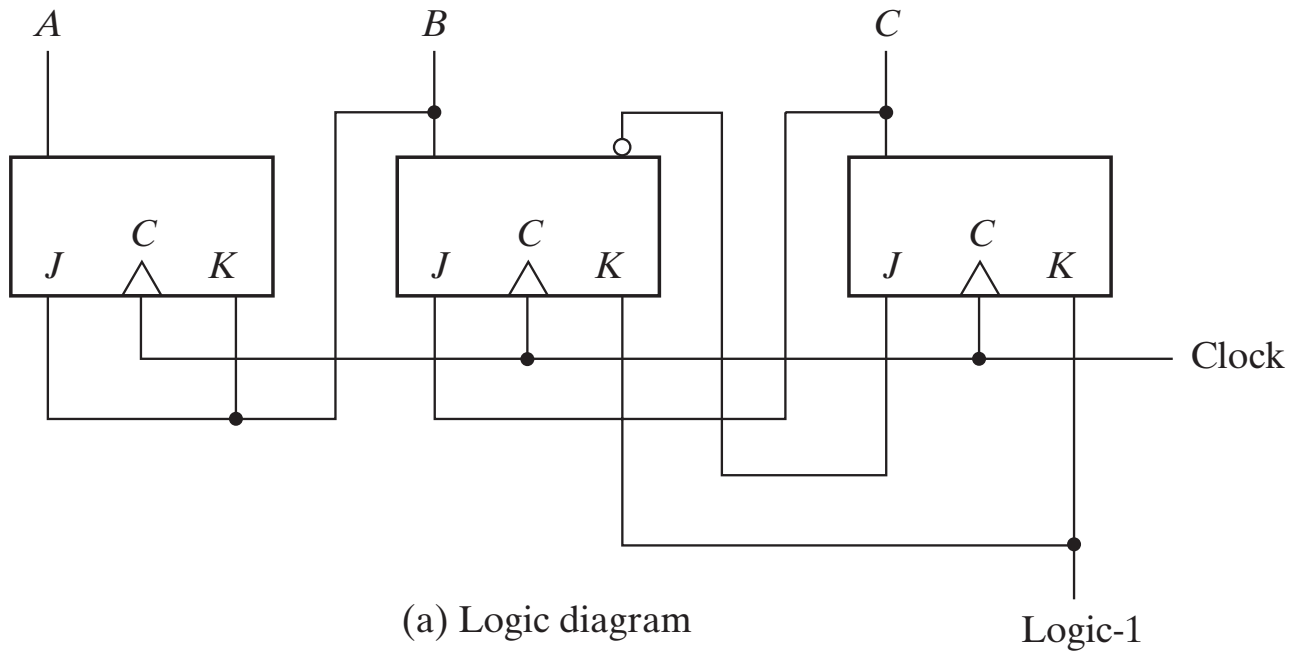



Fig. 6-16 Counter with Unused States

 


(a) Ring-counter (initial value = 1000)

 

(b) Counter and decoder

 

(c) Sequence of four timing signals

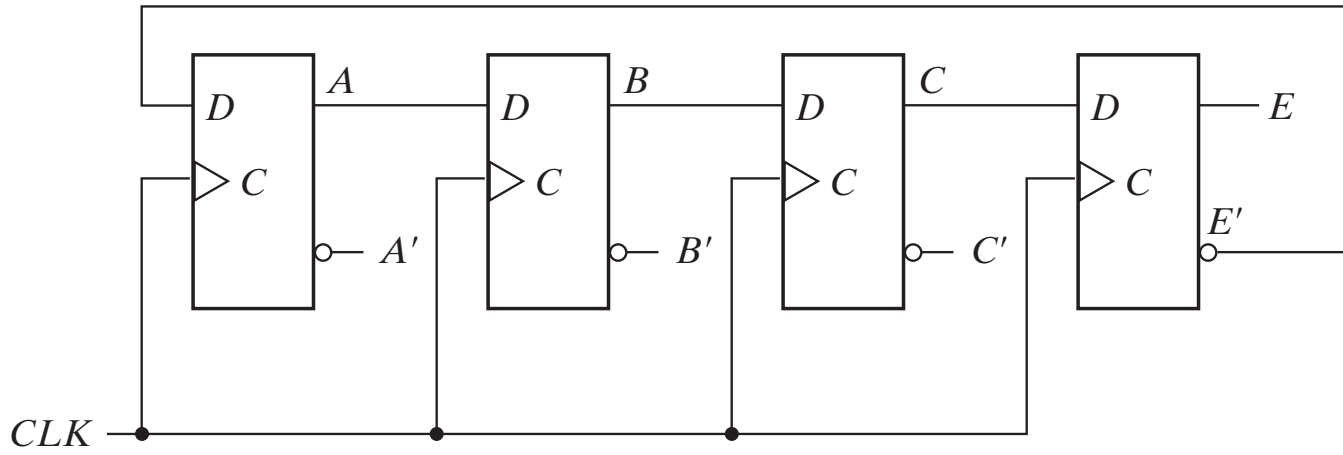


(a) Four-stage switch-tail ring counter


Sequence number	Flip-flop outputs				AND gate required for output
	A	B	C	E	
1	0	0	0	0	$A'E'$
2	1	0	0	0	AB'
3	1	1	0	0	BC'
4	1	1	1	0	CE'
5	1	1	1	1	AE
6	0	1	1	1	$A'B$
7	0	0	1	1	$B'C$
8	0	0	0	1	$C'E$

(b) Count sequence and required decoding

Fig. 6-18 Construction of a Johnson Counter

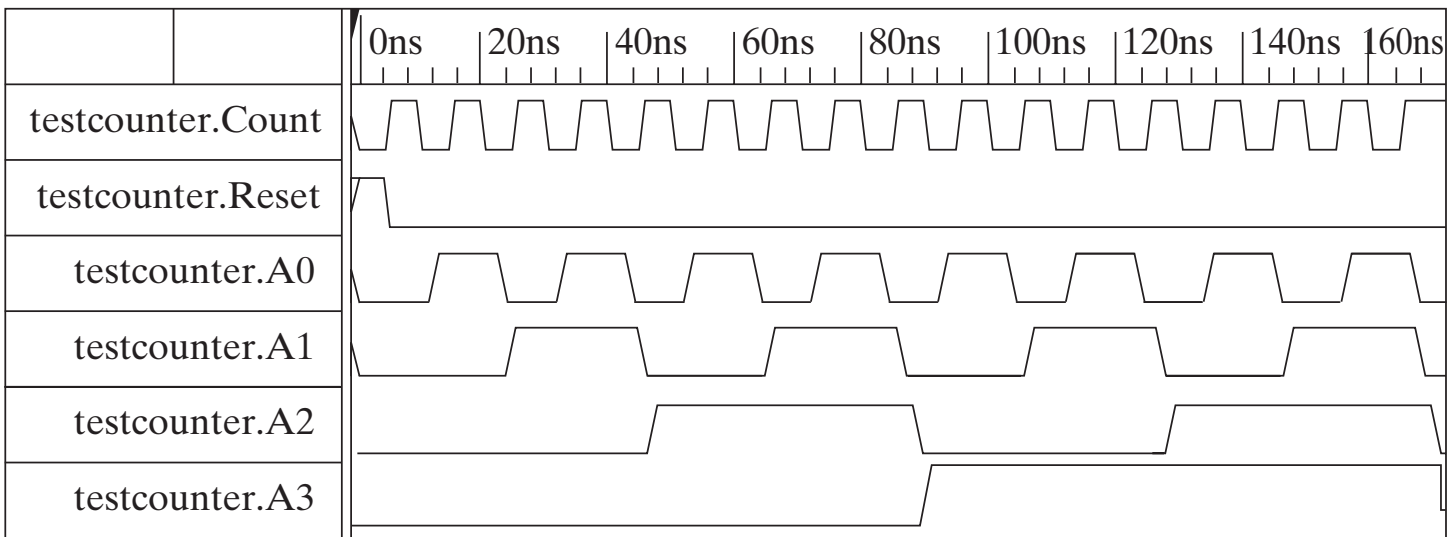

(a) From 0 to 170 ns

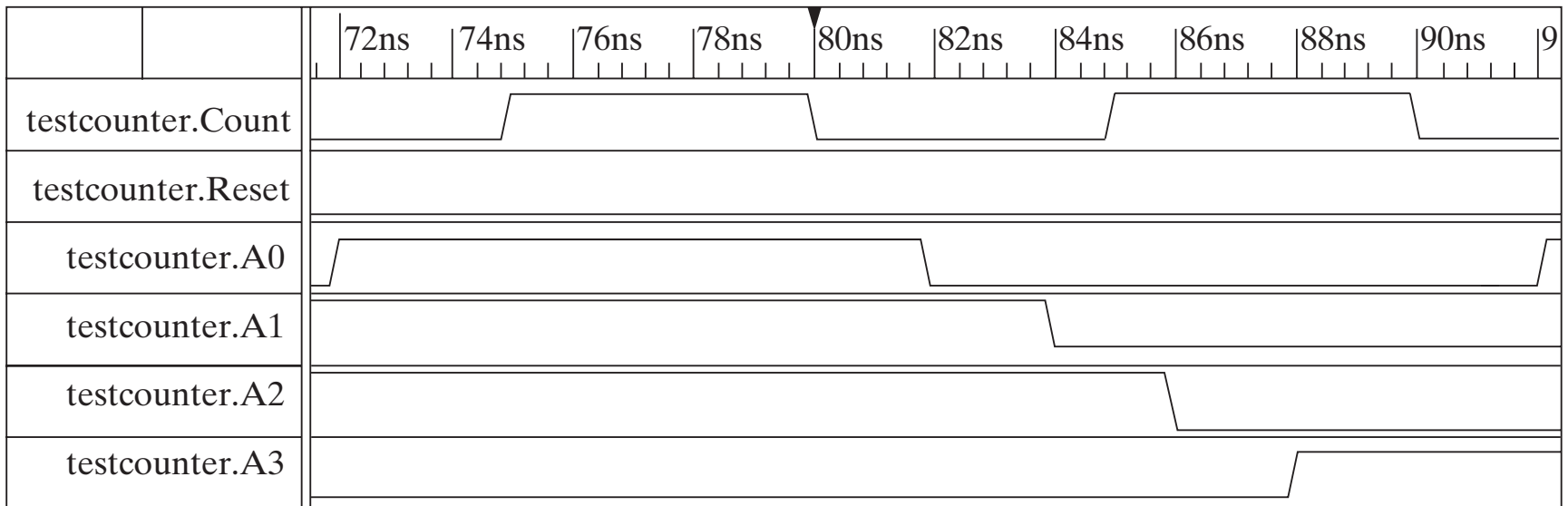

(b) From 70 to 92 ns

 


Fig. P6-21