



Switching, snubbers

or

turn-on and turn off
the
effect of inductance

BASIC


turn on a current step, inductive load.

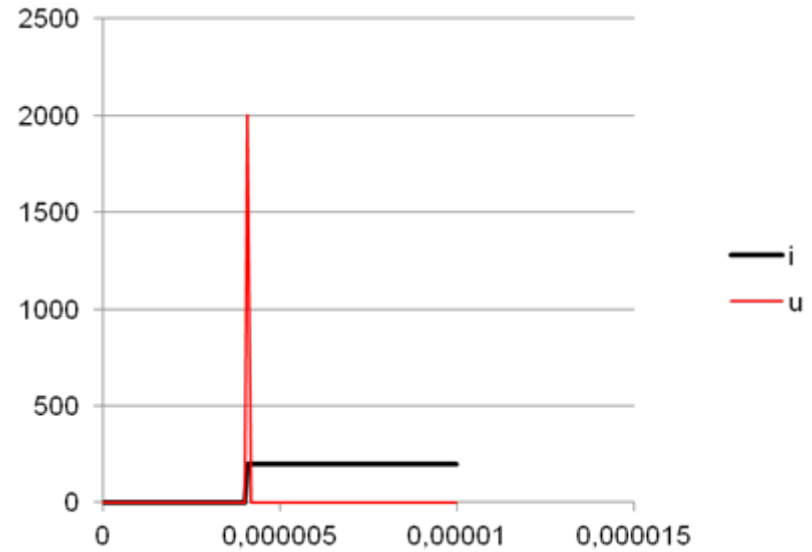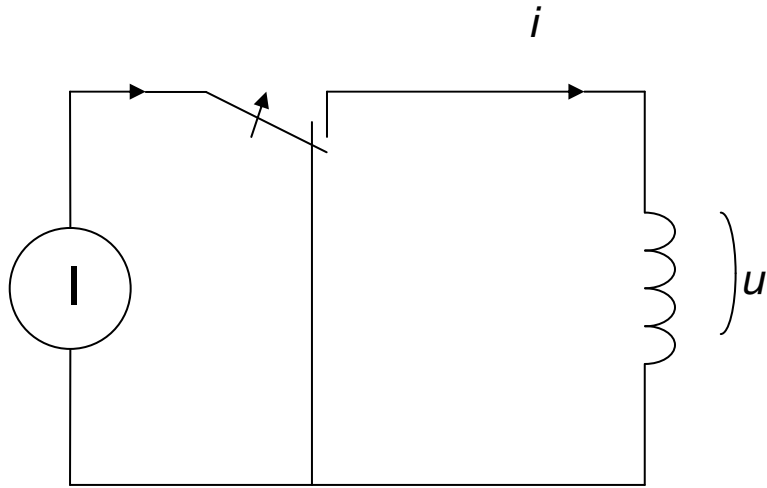


$$u = L \cdot \frac{di}{dt}$$

BASIC

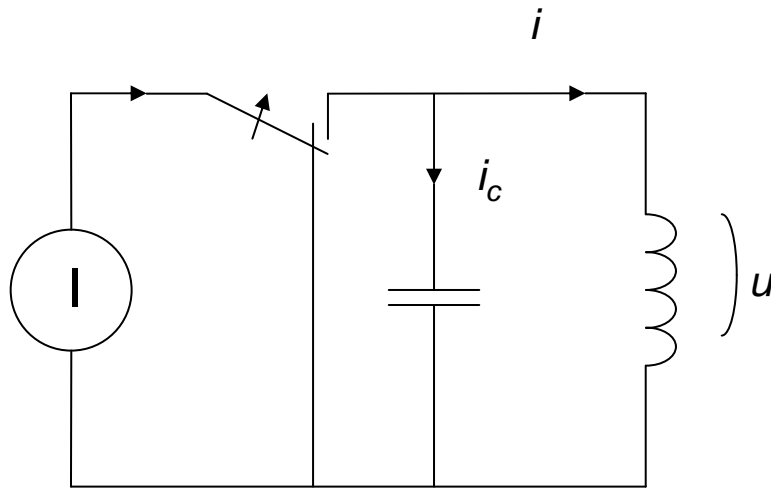turn on current step, inductive load.
Counter measure with capacitor





$$u = L \cdot \frac{di}{dt}$$

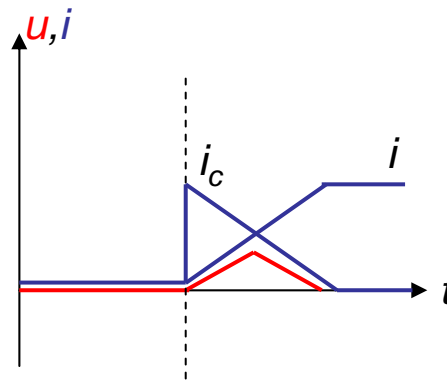

BASIC


turn off a current step, inductive load.

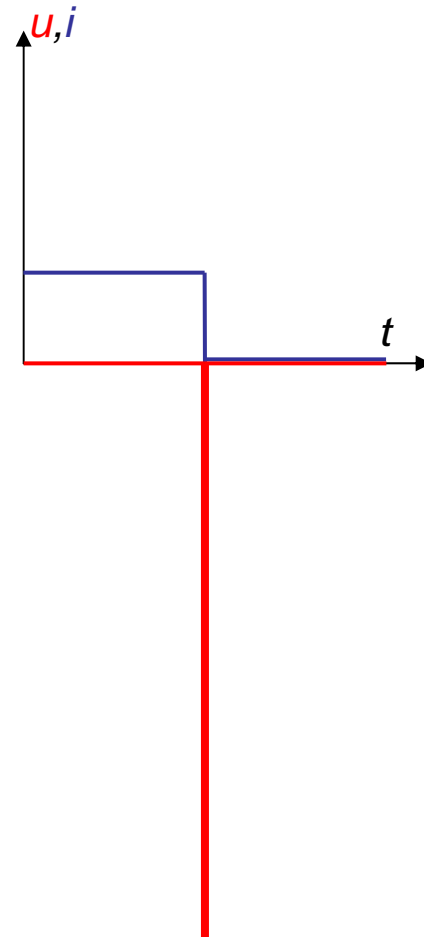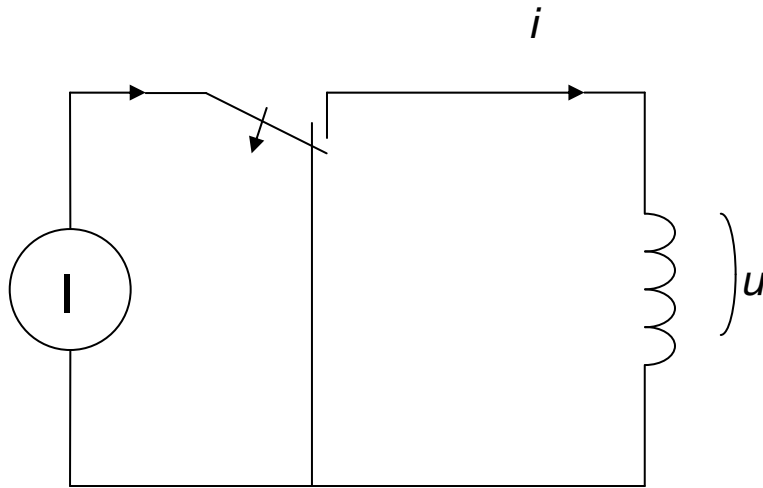

$$u = L \cdot \frac{di}{dt}$$


BASIC

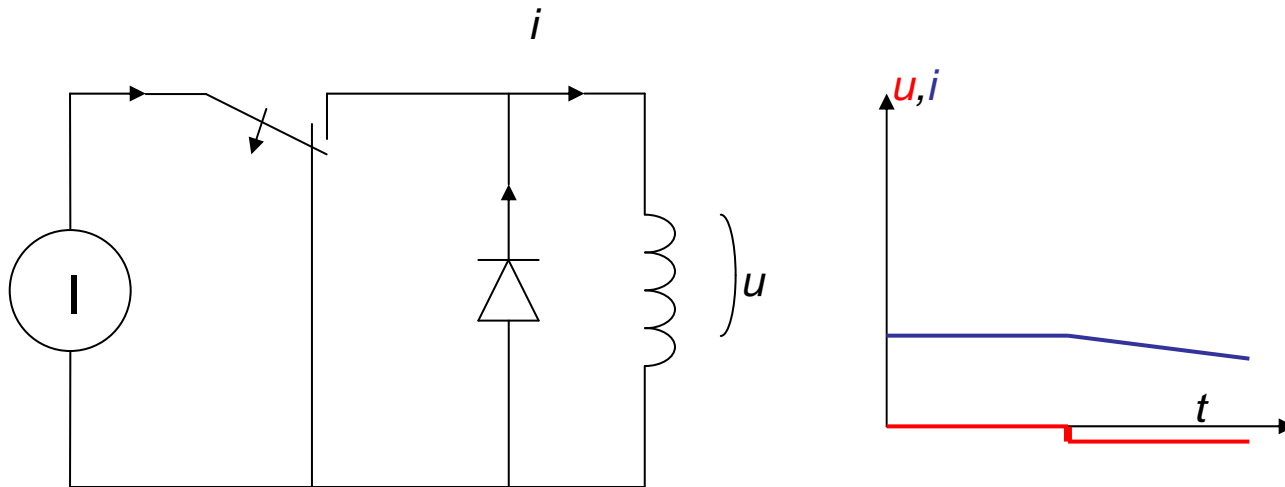turn off current step, inductive load.
Counter measure with freewheeling diode




BASIC

current ramp, inductive load

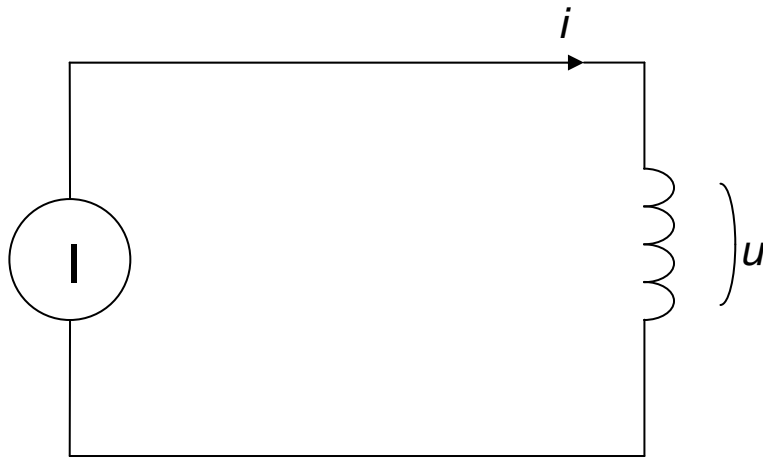



$$u = L \cdot \frac{di}{dt}$$

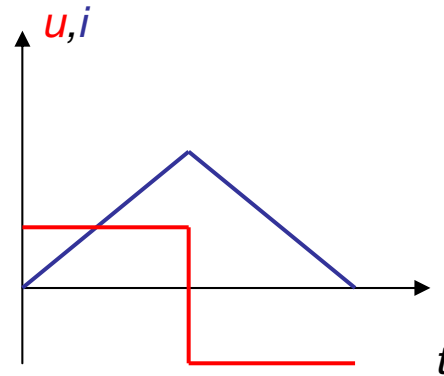

BASIC

turn on voltage step with inductive load.


No problem

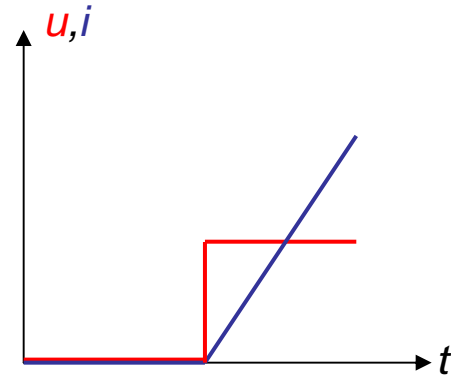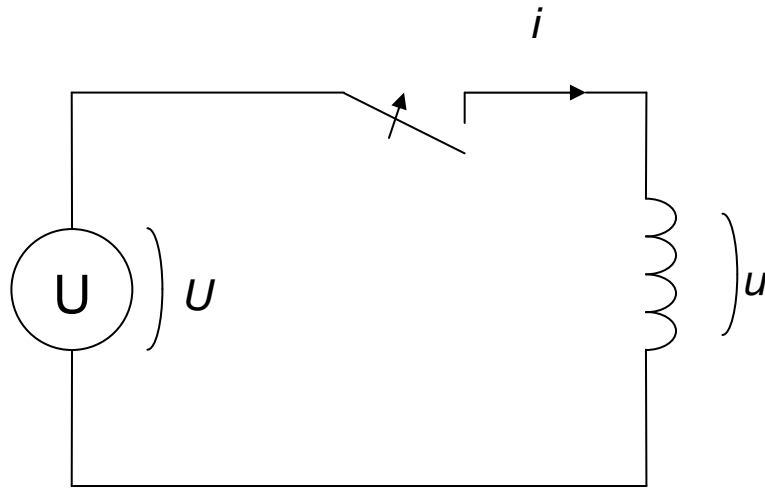


$$u = L \cdot \frac{di}{dt}$$

BASIC

turn off voltage step, inductive load

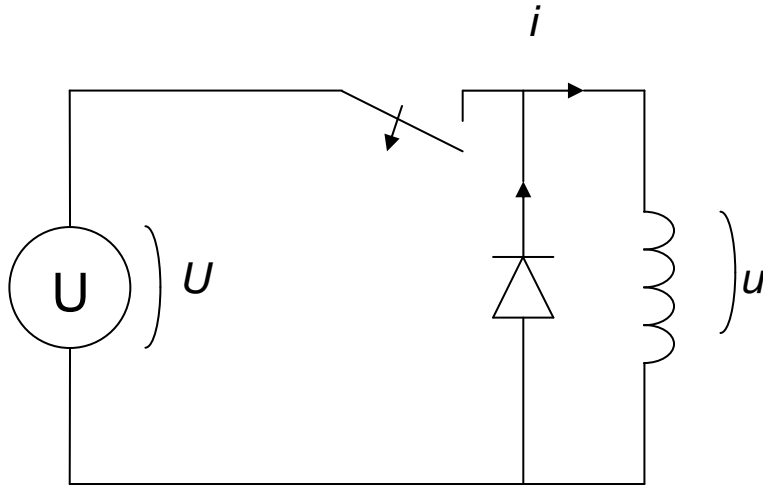


$$u = L \cdot \frac{di}{dt}$$

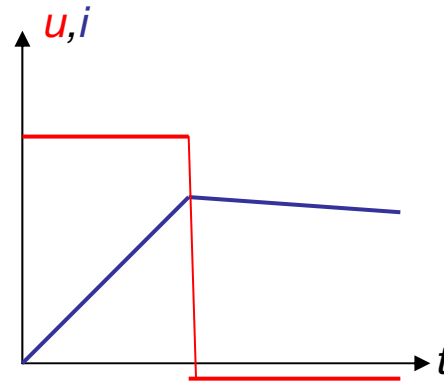

Summary


An inductance keeps a current
"constant"

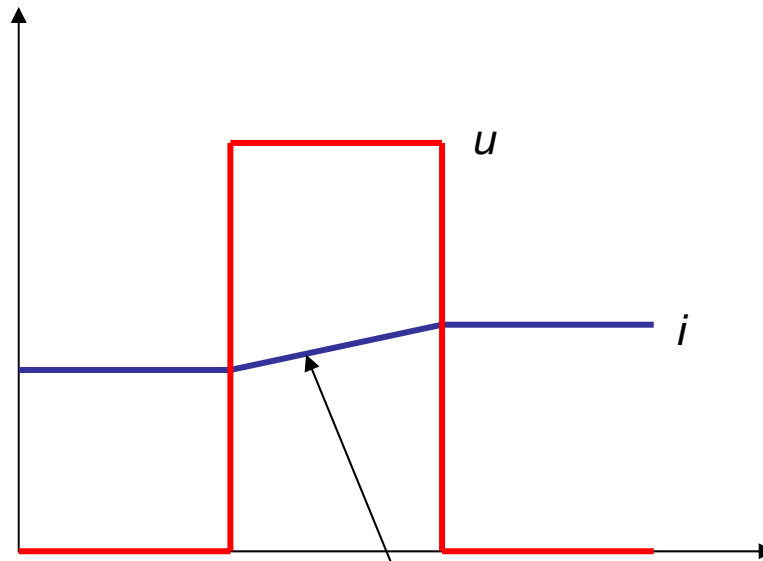

$$\frac{di}{dt} = \frac{u}{L}$$


Summary

A capacitance keeps a voltage
"constant"

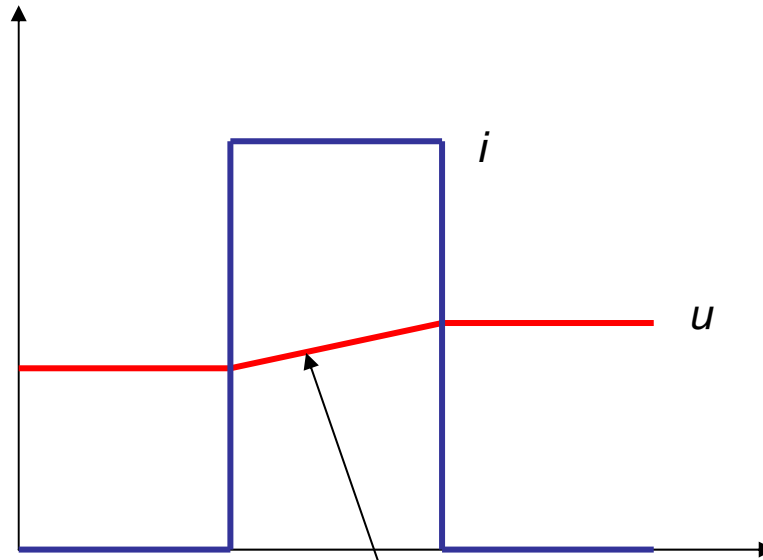


$$\frac{du}{dt} = \frac{i}{C}$$



Step-down chopper

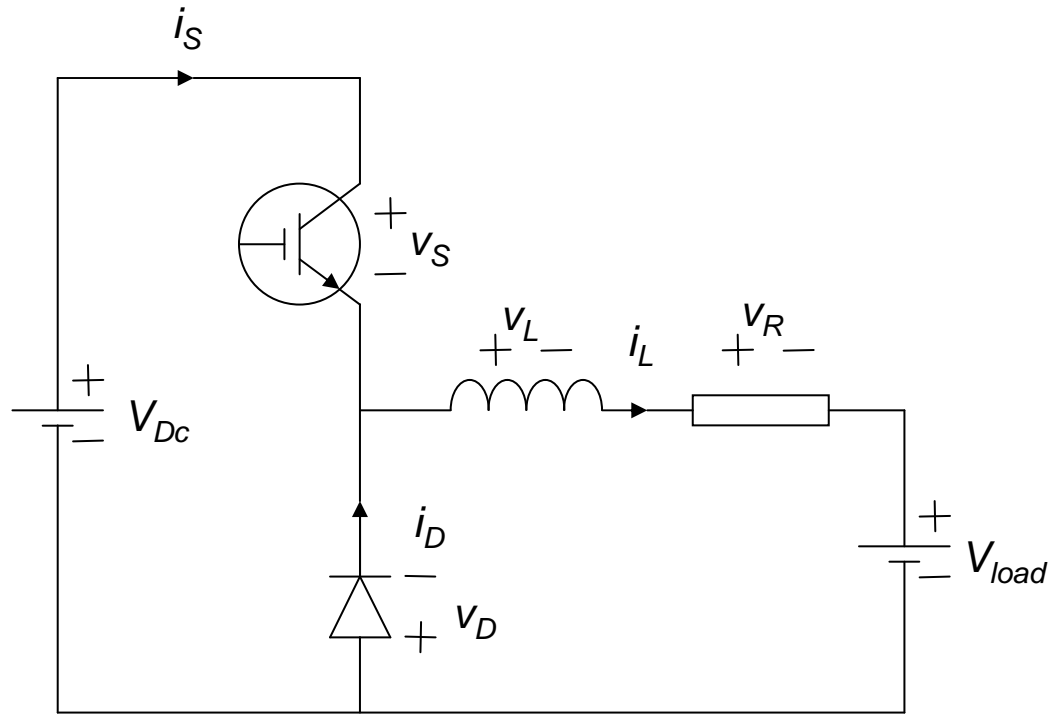


Switching diodes

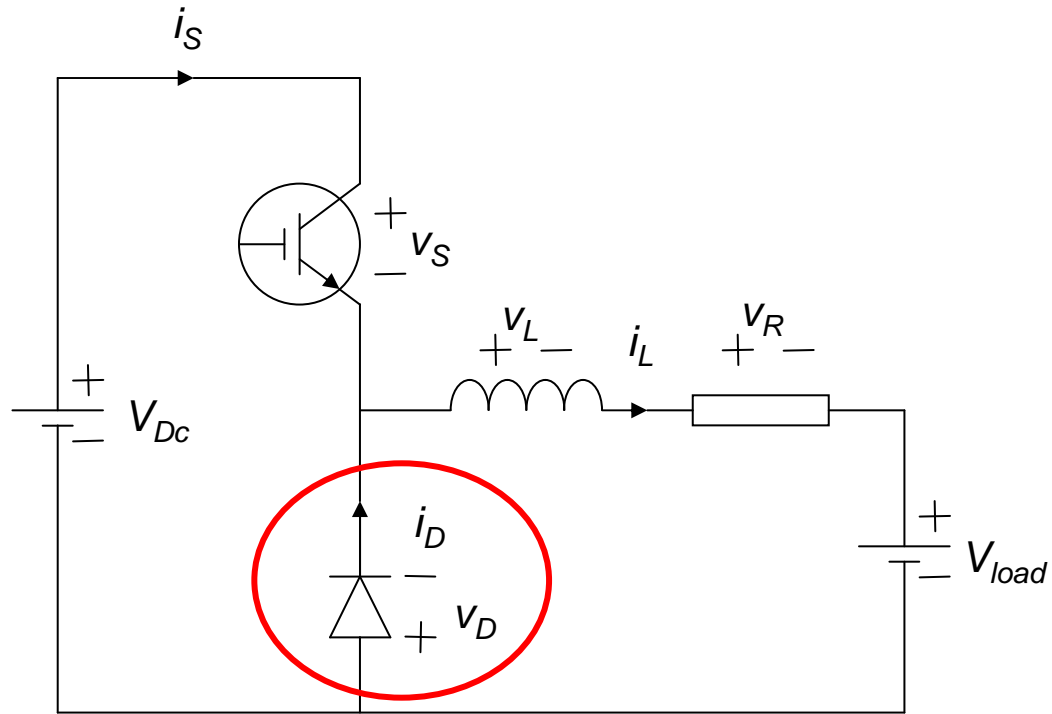



Transistor turn on

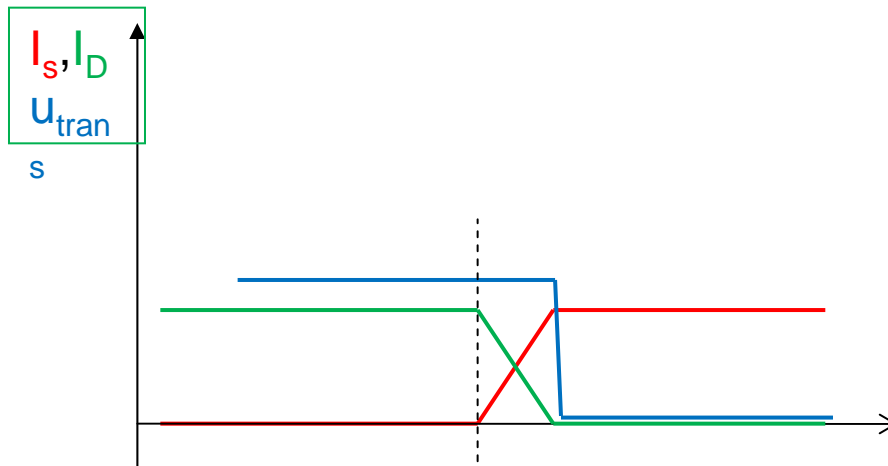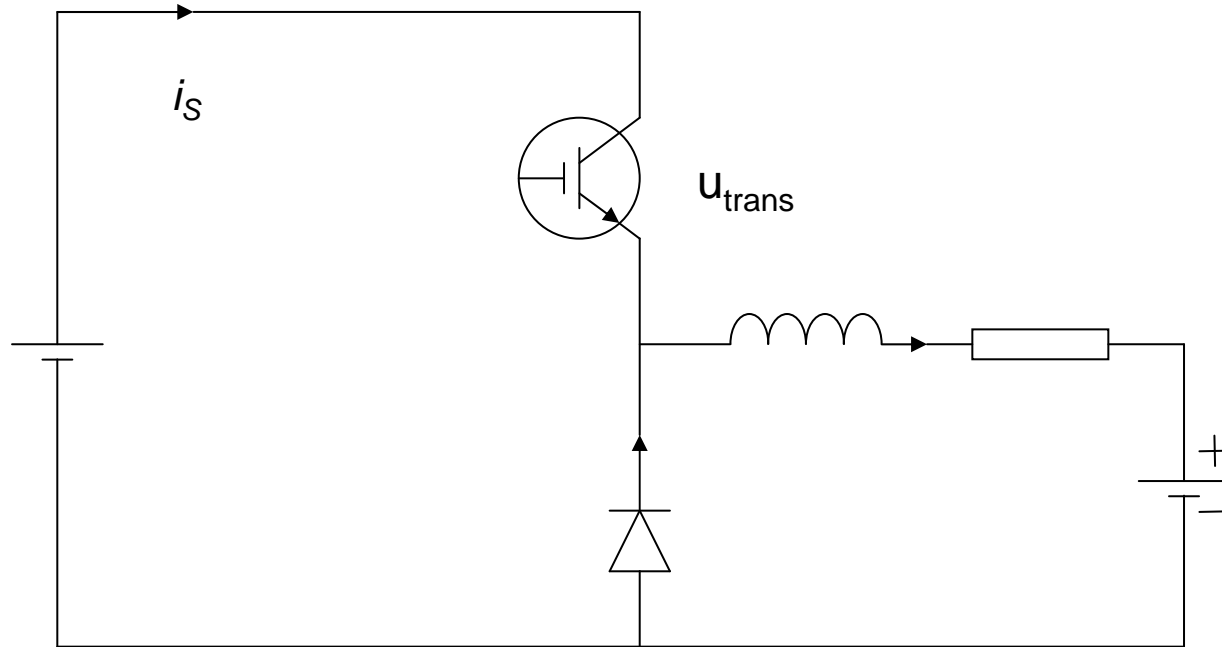



Transistor turn on. Reverse recovery 1

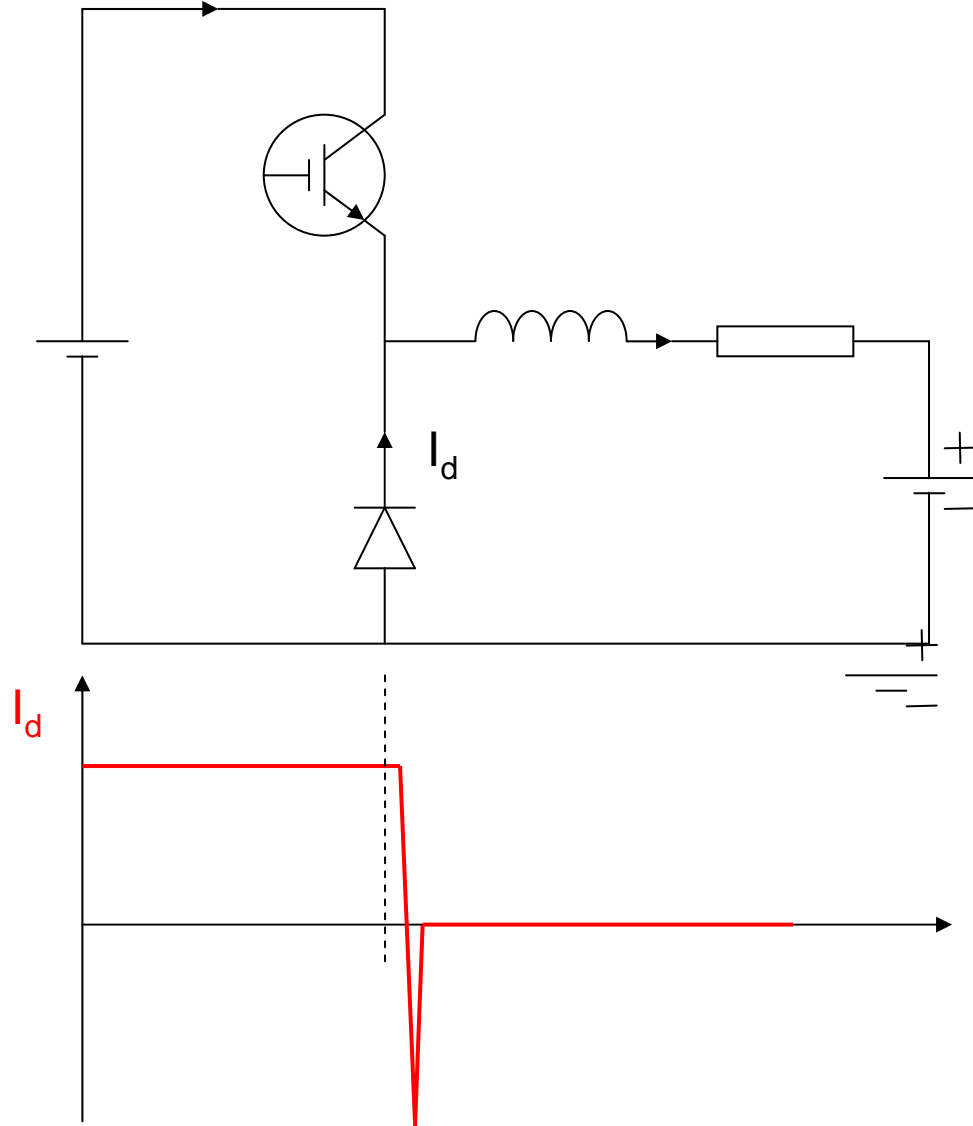

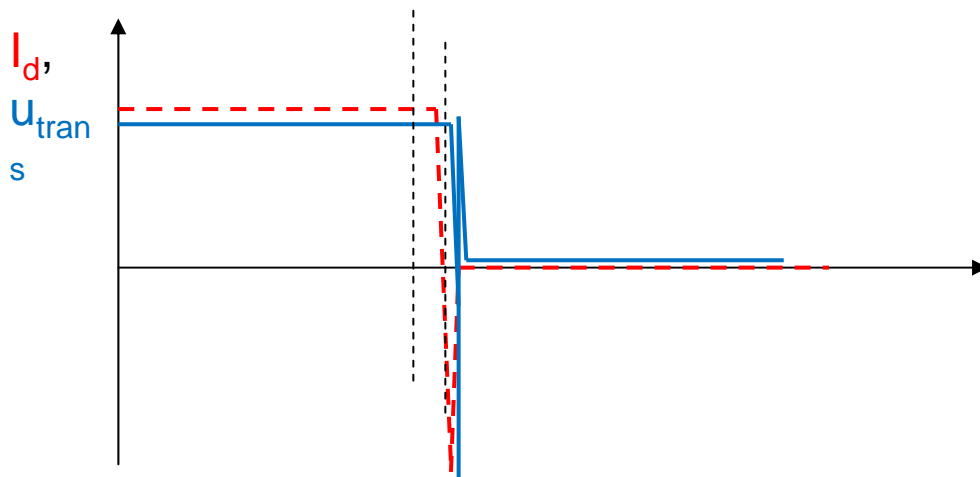
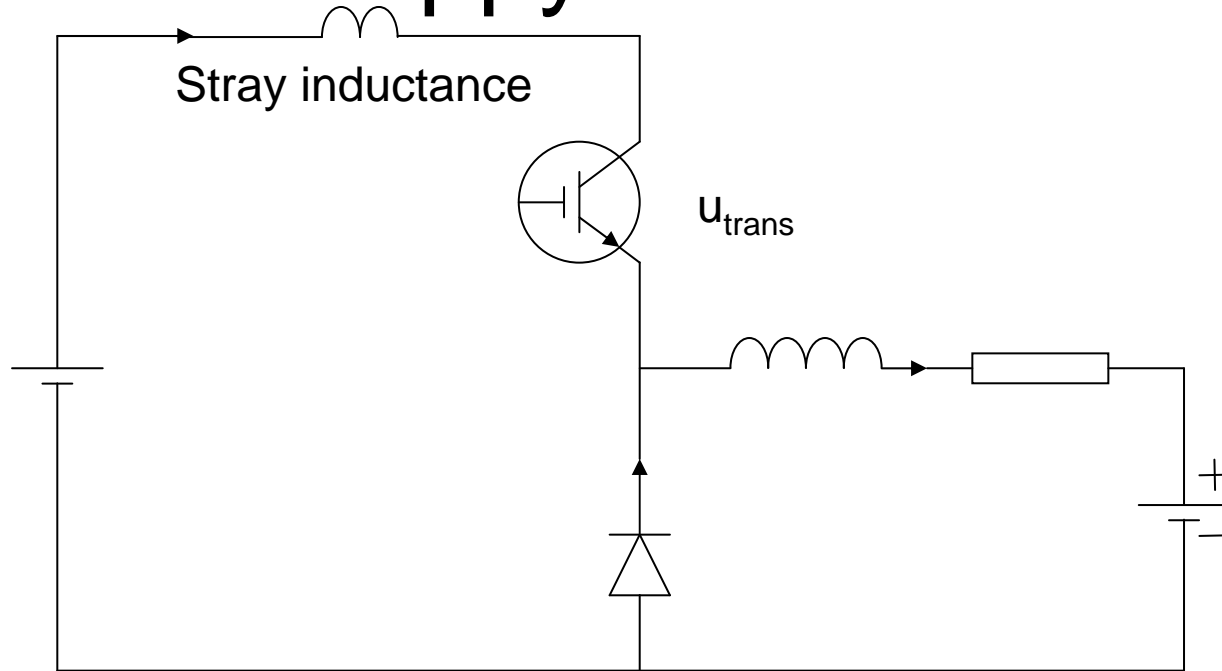
Transistor turn on. Reverse recovery 2, "snappy" diode



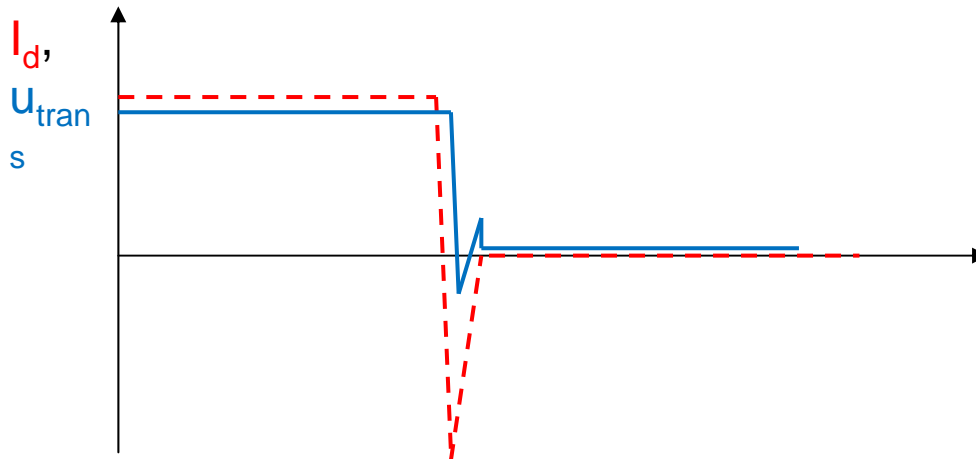
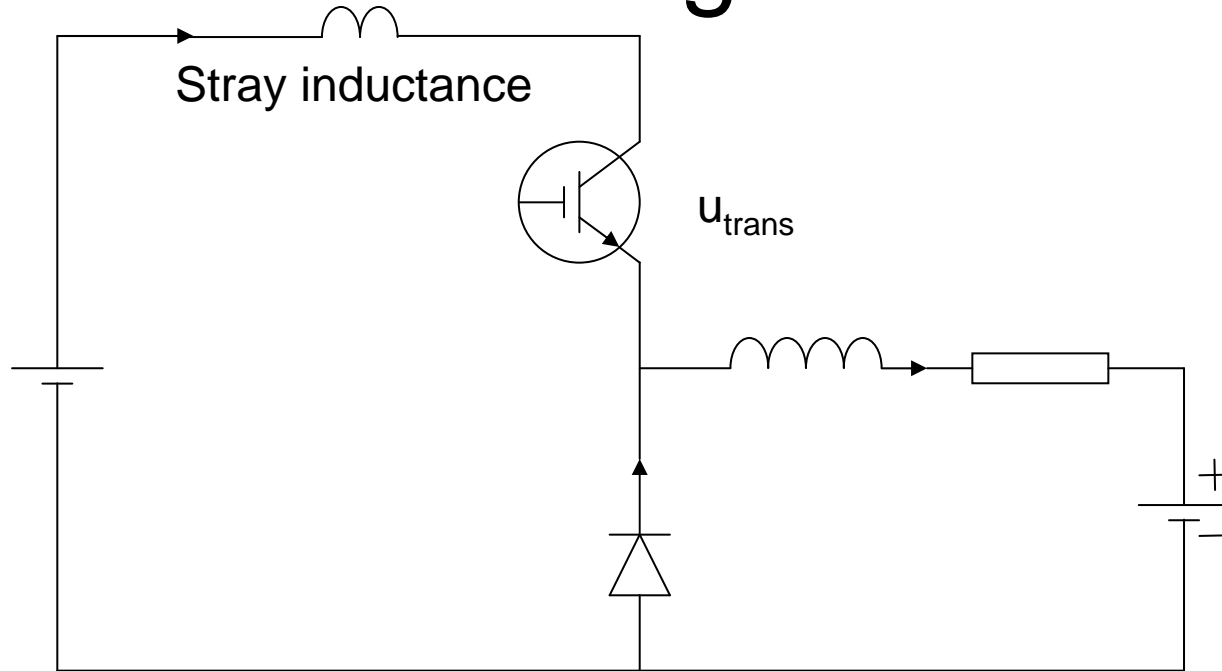
Transistor turn on. Reverse recovery 3, "soft switching" diode




Transistor turn off

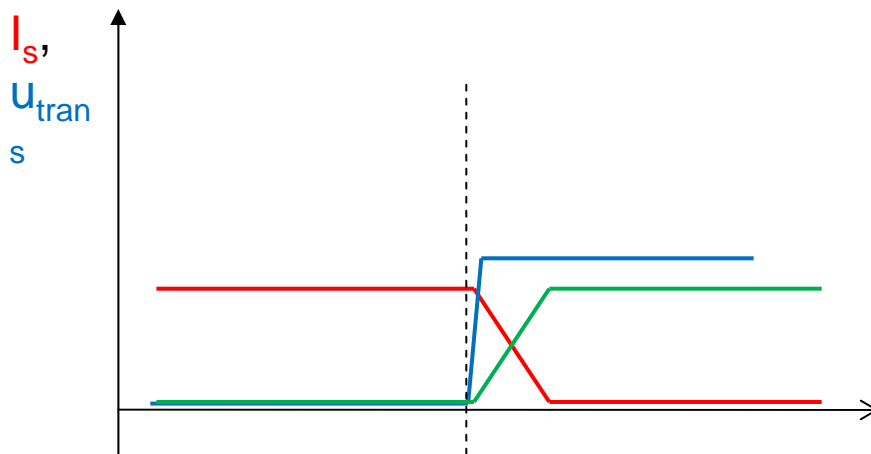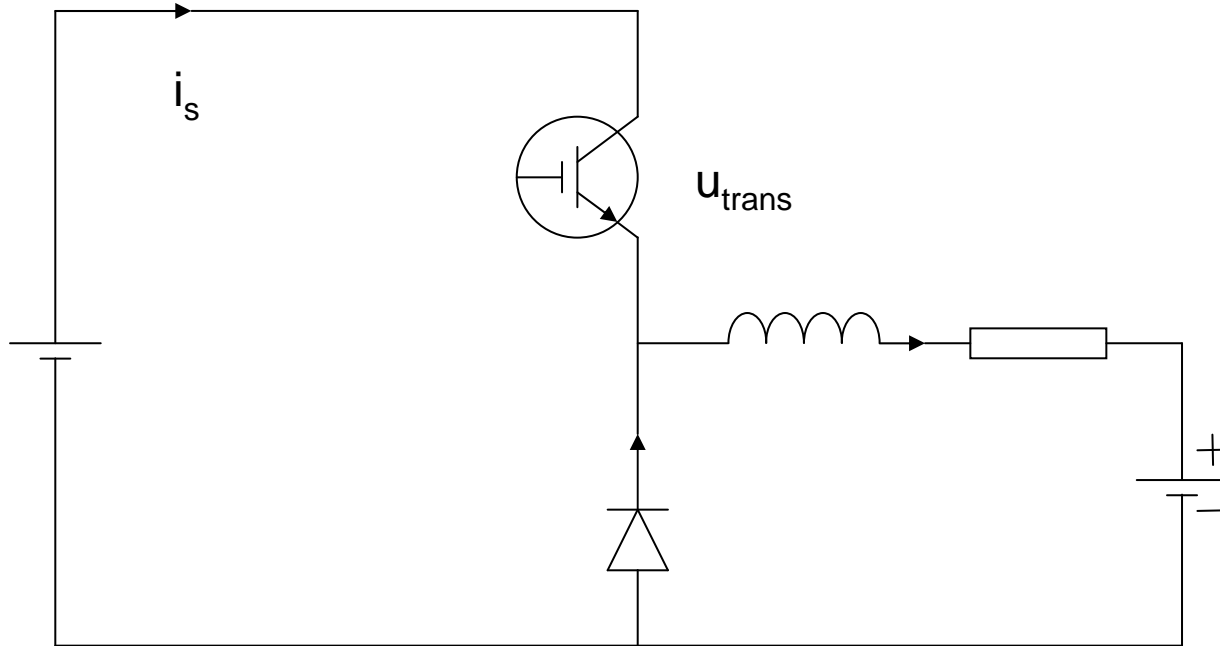



Transistor turn off 1. Fast

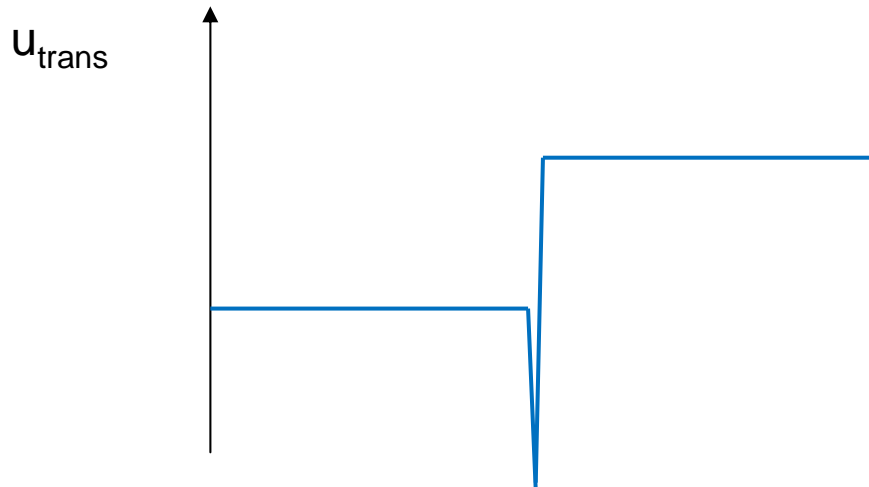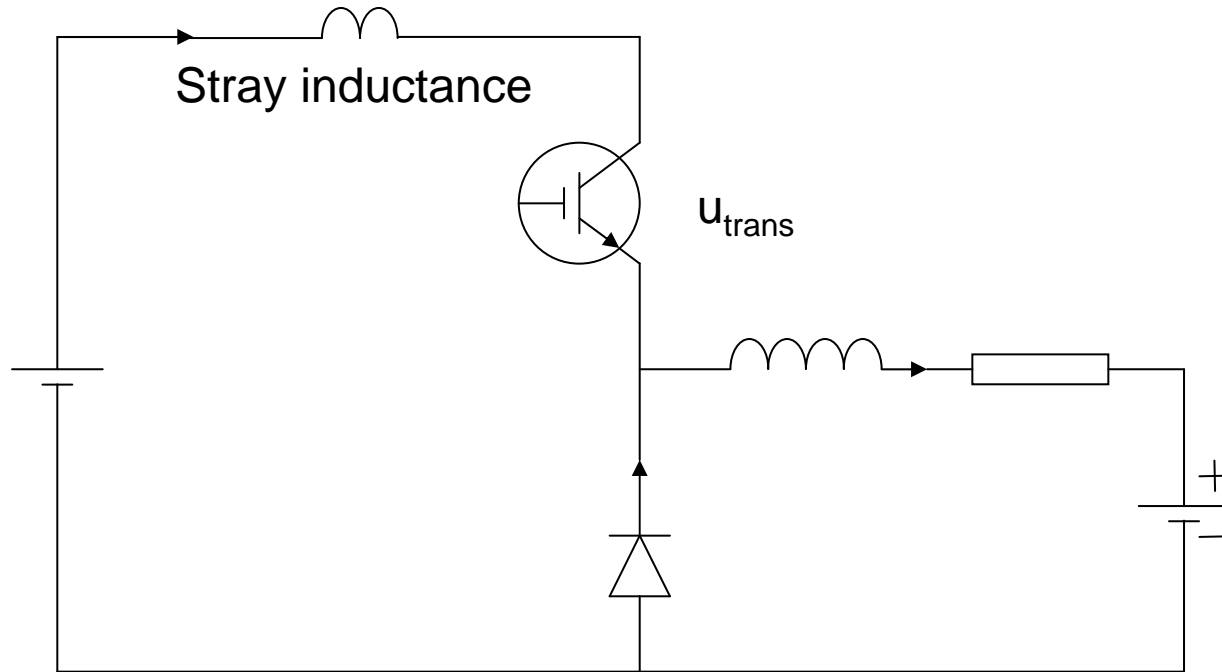


Transistor turn off 2. Slow

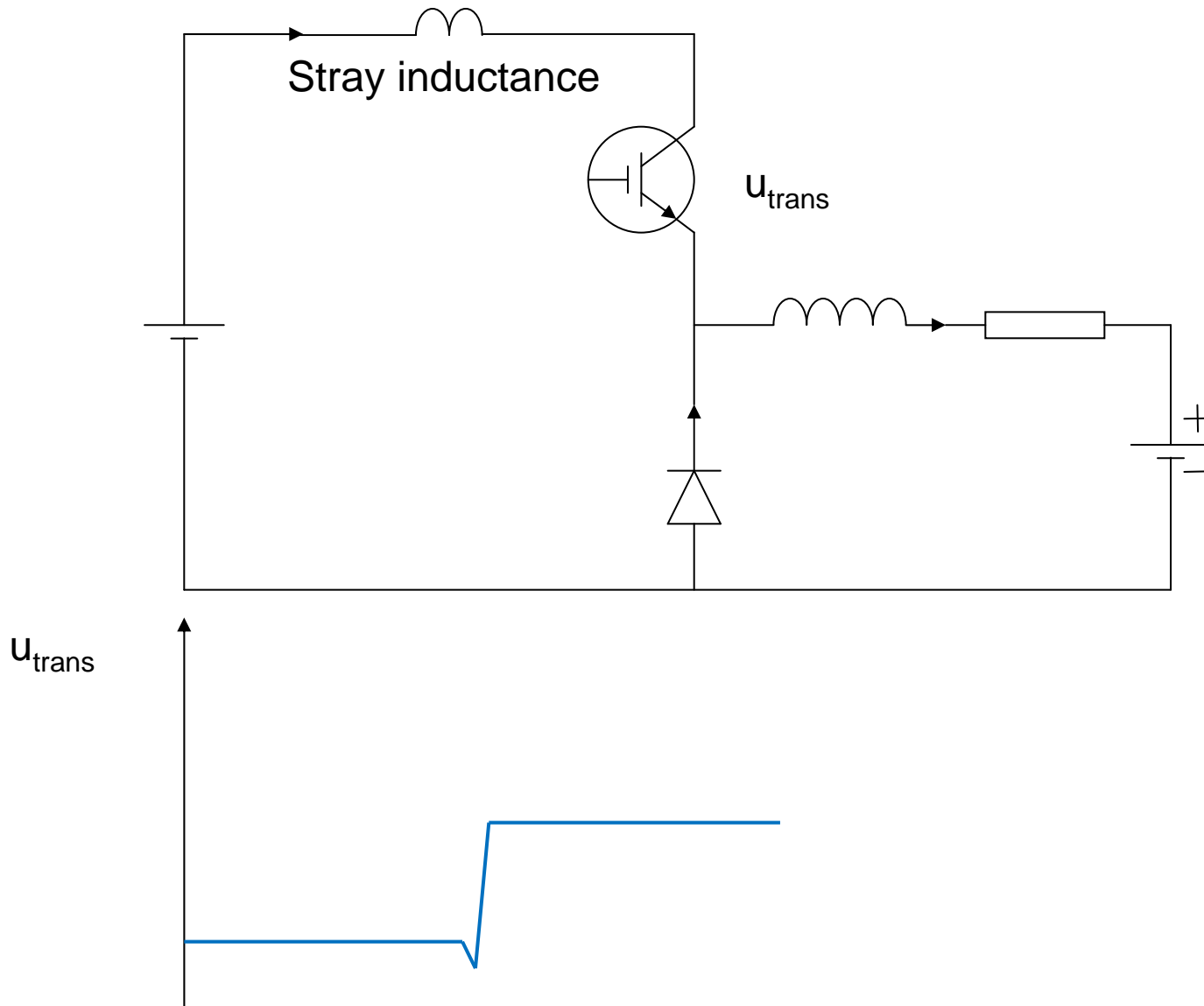

Transistor turn off. Forward recovery

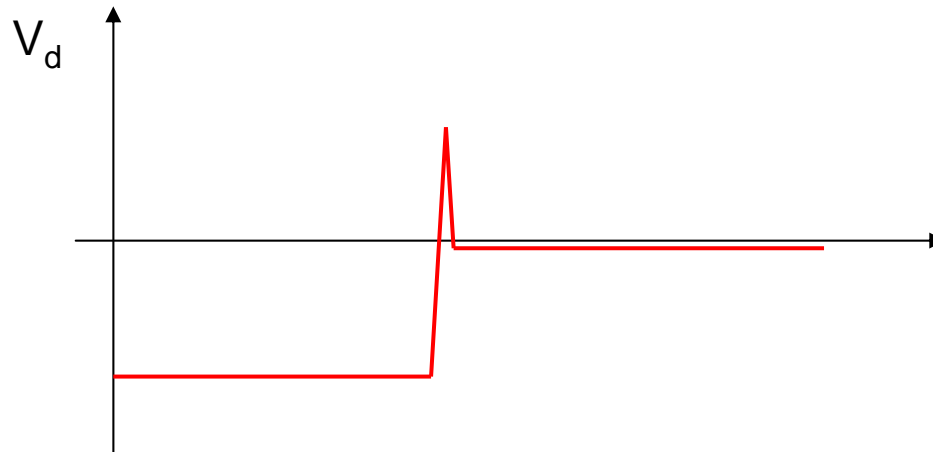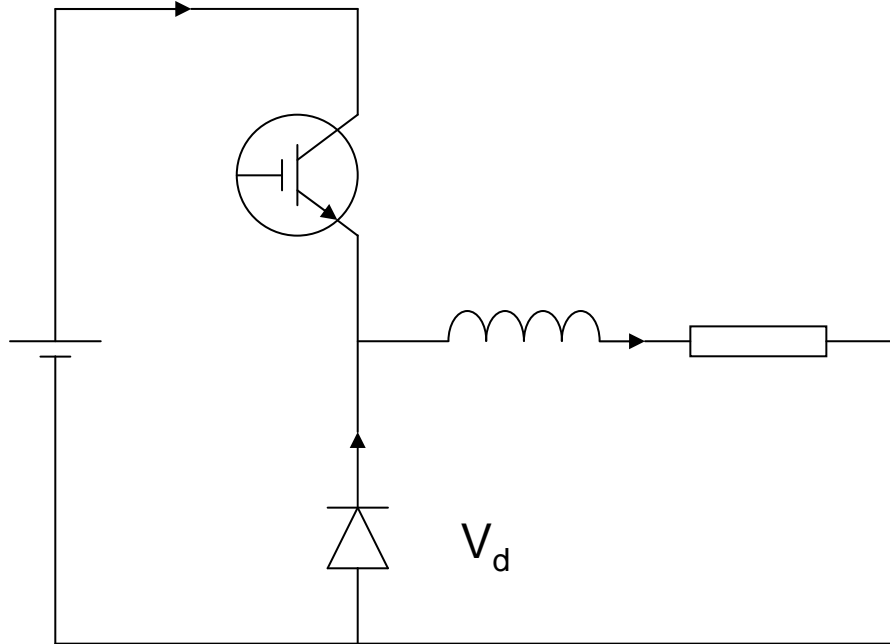

RCD snubber

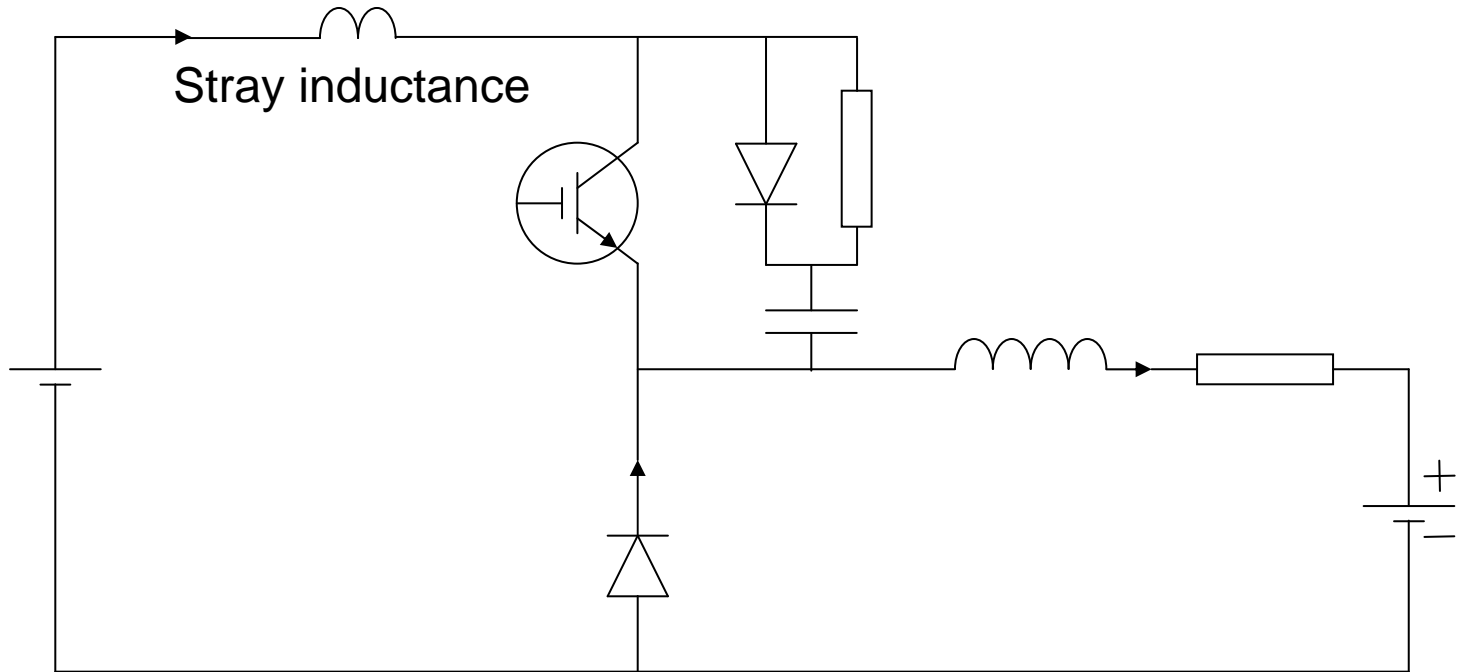

Exercise

Calculate the snubber capacitor for the commutation time 0.1 ms.
The load current is 10 A, assumed constant during the commutation.
The dclink voltage is 500 V. Low voltage is 250 V.

Calculate the snubber resistor so the discharge time (3 time constants)
of the snubber capacitor is less than the IGBT on state time.
The switch frequency is 1 kHz

$$i = C \cdot \frac{du}{dt} \Rightarrow C = \frac{i \cdot \Delta t}{\Delta u} = \frac{10 \cdot 0.1 \cdot 10^{-3}}{500} = \frac{10}{5} \cdot 10^{-3-1-2} = 2 \mu F$$

$$\text{Duty cycle is 50\%, turn on time} = 0.5 \text{ ms. Time const} = \frac{0.5 \text{ ms}}{3} = 0.17 \text{ ms}$$

$$R = \frac{0.17 \cdot 10^{-3}}{2 \cdot 10^{-6}} = 85 \Omega$$

Clamp snubber

