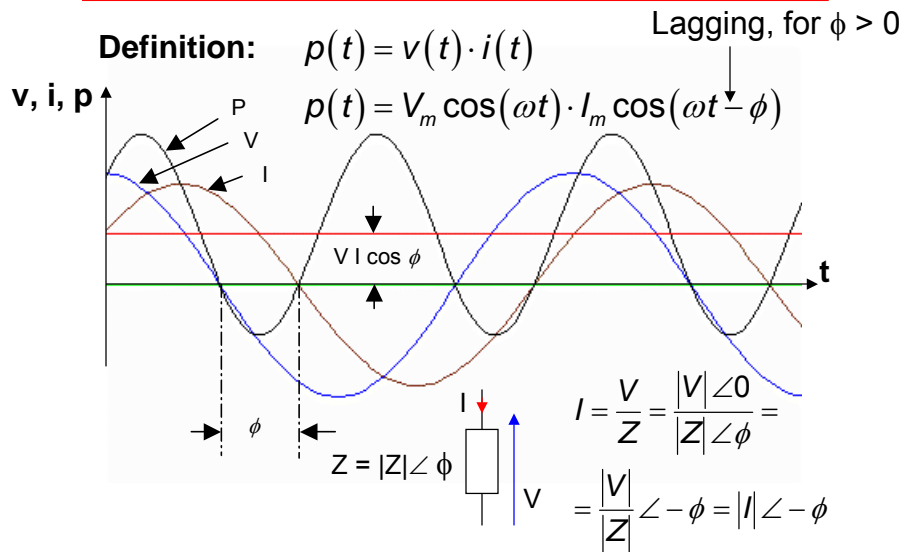


Electric Power

- **single-phase (1~) systems**
 - ◆ One source
 - ◆ Two energy-carrying wires
 - ◆ Pulsating instantaneous power (2f)
- **three-phase (3~) systems**
 - ◆ Three sources, 120° phase shifted

Single Phase Power



Instantaneous and Average Power

trigonometric identity:

$$\cos \alpha \cdot \cos \beta = \frac{1}{2} [\cos(\alpha - \beta) + \cos(\alpha + \beta)]$$

the instantaneous power equation:

$$p(t) = \frac{V_m I_m}{2} [\cos \phi + \cos(2\omega t - \phi)]$$

the average of $\cos(2\omega t - \phi)$ over a cycle is zero

the average power over one cycle: $P = \frac{1}{2} V_m I_m \cos(\phi)$

Average Power from RMS Values

$$V_{rms} = \frac{1}{T} \sqrt{\int_0^T v^2(t) dt} = \frac{1}{\sqrt{2}} V_m \quad \text{for } v(t) = V_m \sin(\omega t)$$

Root mean square (rms) of an arbitrarily (periodic) AC waveform delivers the same power to a resistor as the corresponding DC quantity.

The average power in terms of rms: $P = V_{rms} I_{rms} \cos(\phi)$


Notation convention (this lecture, not in general):

Voltage and currents given in rms if not stated otherwise.

e.g. 208 V \angle -30° means $V_m = \sqrt{2} \cdot 208 = 294 \text{ V}_{pk}$

Power Factor

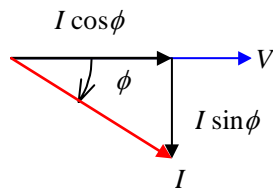
$$P = V_{rms} \underbrace{I_{rms} \cos(\phi)}_{\text{power factor}}$$



Lagging Power Factor

Load
behaves
like

$$R \parallel j\omega L$$

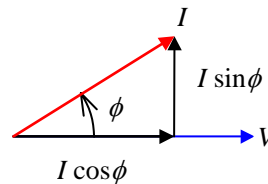

Leading Power Factor


$$R \parallel 1/j\omega C$$

Complex Power

General case:

$$V = |V| \angle \gamma$$

$$I = |I| \angle \gamma - \phi$$

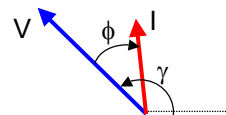

Complex or
Apparent Power:

$$S = V \cdot I^* = |V| \cdot |I| \angle \phi$$

$$S = |V| \cdot |I| \cos \phi + j|V| \cdot |I| \sin \phi$$

Real Power:

$$P = |V| \cdot |I| \cos(\phi) \quad (W)$$

Reactive Power:

$$Q = |V| \cdot |I| \sin(\phi) \quad (VA_r)$$


$$S = P + jQ \quad (VA)$$

Positive Angle ϕ : Lagging PF

Negative Angle ϕ : Leading PF

Power Triangle

$$\text{Power Factor: } \cos \phi = \cos \left[\arctan \left(\frac{Q}{P} \right) \right] = \frac{P}{\sqrt{P^2 + Q^2}} = \frac{P}{|S|}$$

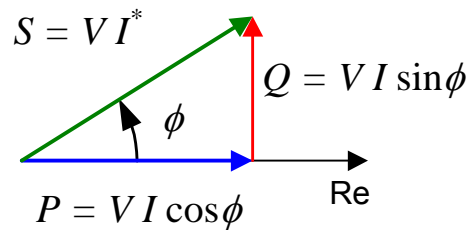

**+ Q = Lagging Power Factor
Inductive Load (Consuming)**

**- Q = Leading Power Factor
Capacitive Load (Consuming)**

Example: Power Factor

See Book, Problem 1-18, p. 54

Assume that the voltage applied to a load is $V = 208 \text{ V} \angle -30^\circ$ and the current flowing through the load is $I = 5 \text{ A} \angle 15^\circ$.

- Calculate the complex power S consumed by this load.
- Is this load inductive or capacitive?
- Calculate the power factor of this load?
- Calculate the reactive power consumed or supplied by this load. Does the load consume reactive power from the source or supply it to the source?

Example: Power Factor

- (a) The complex power S consumed by this load is


$$\mathbf{S} = \mathbf{V}\mathbf{I}^* = (208\angle -30^\circ \text{ V})(5\angle 15^\circ \text{ A})^* = (208\angle -30^\circ \text{ V})(5\angle -15^\circ \text{ A})$$

$$\mathbf{S} = 1040\angle -45^\circ \text{ VA}$$
- (b) This is a capacitive load.
- (c) The power factor of this load is

$$\text{PF} = \cos(-45^\circ) = 0.707 \text{ leading}$$
- (d) This load supplies reactive power to the source. The reactive power of the load is


$$Q = VI \sin \theta = (208 \text{ V})(5 \text{ A}) \sin(-45^\circ) = -735 \text{ var}$$

Wye (Y) Connected Systems

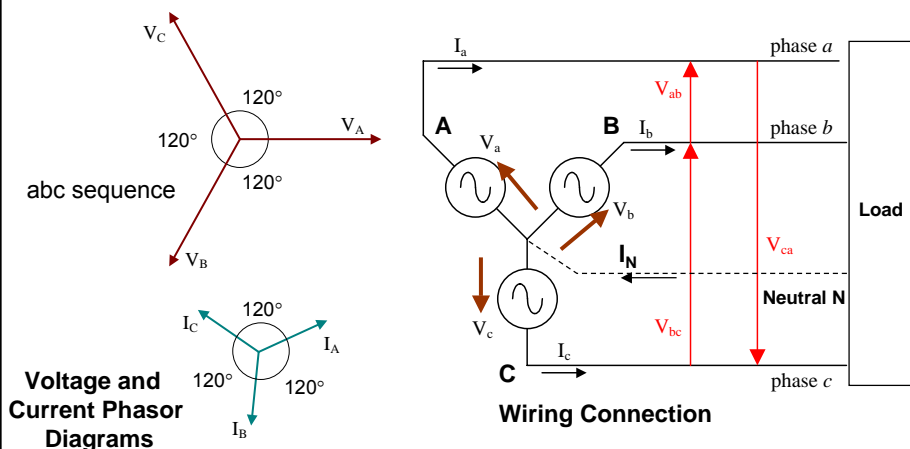

3-wire system: $I_N = 0$, Balanced system: $I_a = I_b = I_c$

Three Phase Time Domain Signals

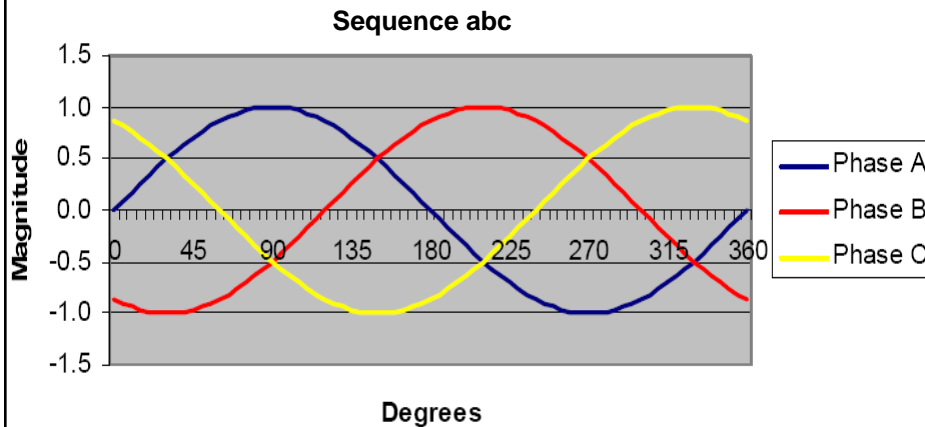

Three-Phase Power, Balanced System

$$\begin{aligned}
 V_a(t) &= \sqrt{2} \cdot V_p \sin(\omega t) & I_a(t) &= \sqrt{2} \cdot I_p \sin(\omega t - \phi) \\
 V_b(t) &= \sqrt{2} \cdot V_p \sin(\omega t - 120^\circ) & I_b(t) &= \sqrt{2} \cdot I_p \sin(\omega t - 120^\circ - \phi) \\
 V_c(t) &= \sqrt{2} \cdot V_p \sin(\omega t + 120^\circ) & I_c(t) &= \sqrt{2} \cdot I_p \sin(\omega t + 120^\circ - \phi)
 \end{aligned}$$

$$\begin{aligned}
 p_a(t) &= V_a(t) \cdot I_a(t) = 2V_p I_p \sin(\omega t) \sin(\omega t - \phi) \\
 p_b(t) &= V_b(t) \cdot I_b(t) = 2V_p I_p \sin(\omega t - 120^\circ) \sin(\omega t - 120^\circ - \phi) \\
 p_c(t) &= V_c(t) \cdot I_c(t) = 2V_p I_p \sin(\omega t + 120^\circ) \sin(\omega t + 120^\circ - \phi)
 \end{aligned}$$

Three-Phase Power, Balanced System

$$p_{3\phi}(t) = p_a(t) + p_b(t) + p_c(t)$$

$$\sin \alpha \cdot \sin \beta = \frac{1}{2} [\cos(\alpha - \beta) - \cos(\alpha + \beta)]$$

$$p_{3\phi}(t) = V_p I_p \left\{ 3 \cos \phi - \underbrace{[\cos(2\omega t - \phi) + \cos(2\omega t - 240 - \phi) + \cos(2\omega t + 240 - \phi)]}_{= 0} \right\}$$

$$p_{3\phi}(t) = 3 \cdot V_p I_p \cos(\phi) = P_{3\phi} = \text{const.}!$$

Complex Power, Balanced System

$$V_p = |V_p| \angle 0^\circ \quad I_p = |I_p| \angle -\phi$$

$$S_{3\phi} = 3 \cdot V_p \cdot I_p^* \quad \text{General Form of Complex Power}$$


$$= \sqrt{3} \cdot V_L \cdot I_L^*$$

$$S_{3\phi} = 3 |V_p| |I_p| \angle \phi \quad \text{Phasor Form}$$

$$S_{3\phi} = 3 |V_p| |I_p| (\cos \phi + j \sin \phi)$$

$$= P_{3\phi} + jQ_{3\phi}$$

Relations in the Wye Connection

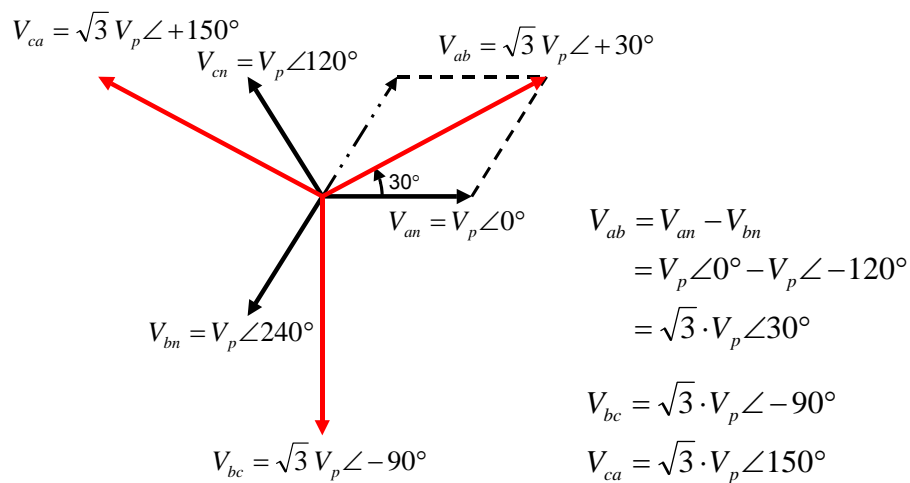

Relations in the Y Connection

voltage relationship

$$V_{Line} = \sqrt{3} \cdot V_{phase} \angle +30^\circ$$

current relationship

$$I_{Line} = I_{phase}$$

Three-Phase Power, Balanced System


$$P_{3\phi} = 3|V_p||I_p|\cos\phi = \sqrt{3}|V_L||I_L|\cos\phi \quad \text{Real Power}$$

$$Q_{3\phi} = 3|V_p||I_p|\sin\phi = \sqrt{3}|V_L||I_L|\sin\phi \quad \text{Reactive Power}$$


Electric Power

- **single-phase (1~) systems**
 - ◆ One source
 - ◆ Two energy-carrying wires
 - ◆ Pulsating instantaneous power (2f)
- **three-phase (3~) systems**
 - ◆ Three sources, 120° phase shifted
 - ◆ Requires only 3 energy-carrying wires to deliver 3 times the power of 1~ phase system
 - ◆ Balanced systems
 - Instantaneous power is **constant**
 - No torque pulsations in 3~ machines
 - ◆ Unbalanced systems
 - Instantaneous power is not constant
 - Analyze each phase individually as a 1~ system

Relations in the Delta Connection

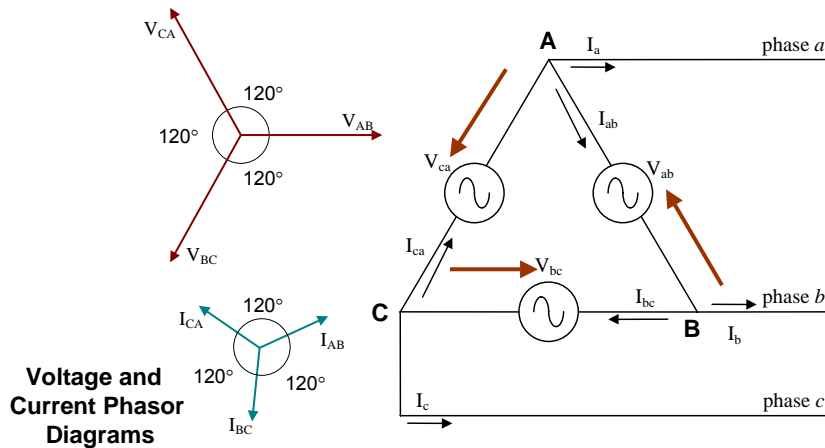

Relations in the Delta (Δ) Connection

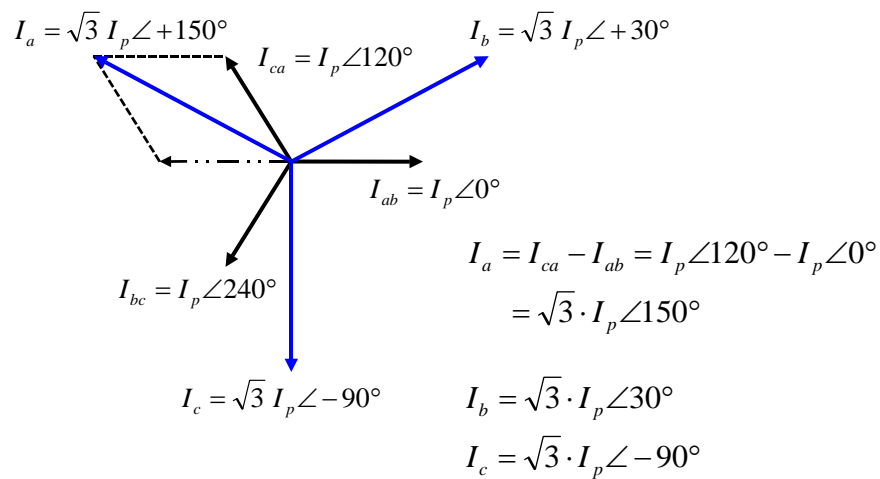

Relations in the Delta Connection

voltage relationship

$$V_{Line} = V_{phase}$$

current relationship

$$I_{Line} = \sqrt{3} \cdot I_{phase} \angle + 30^\circ$$

**See also Book,
Table 2-1**

Three-Phase Power, Balanced System

Wye Connection

$$I_p = I_L$$

$$V_p = V_L / \sqrt{3}$$


$$P_{3\phi} = 3 \cdot V_p I_p \cos(\phi)$$

Delta Connection

$$I_p = I_L / \sqrt{3}$$

$$V_p = V_L$$

$$P_{3\phi} = 3 \cdot V_p I_p \cos(\phi)$$

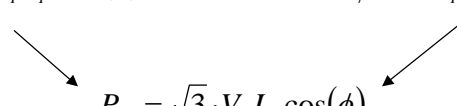
$$P_{3\phi} = \sqrt{3} \cdot V_L I_L \cos(\phi)$$

Homework 1

See web site

<http://www.eng.fsu.edu/~steuerer/eel3216.html>