

*Week 3: Diode Application Circuits*





# Topics to cover ...

- Voltage Regulation - Zener Diode
  - Rectifiers
  - DC-to-DC converters
  - Wave shaping circuits
  - Photodiode and LED
- 
- Reading Assignment:  
Chap 3.13-3.16, 3.18 of Jaeger & Blalock



# Breakdown Region Diode Model

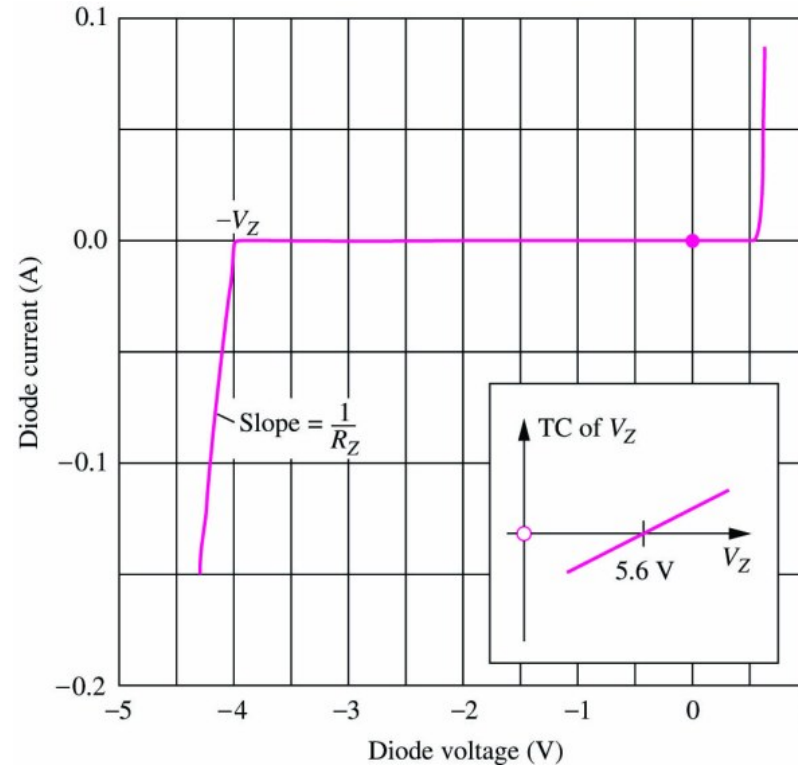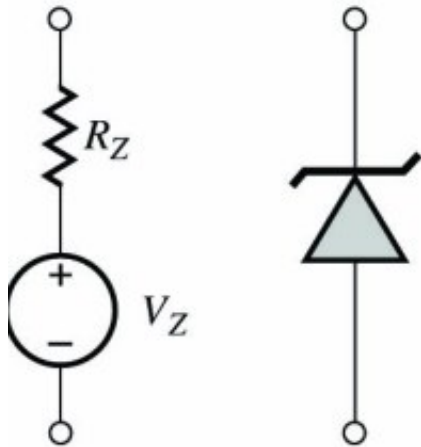


In breakdown, the diode is modeled with a DC voltage source,  $V_Z$ , and a series resistance,  $R_Z$ .  $R_Z$  models the slope of the  $i$ - $v$  characteristic.

Diodes designed to operate in reverse breakdown are called **Zener diodes** and use the indicated symbol



# Example 1 – Graphic Analysis

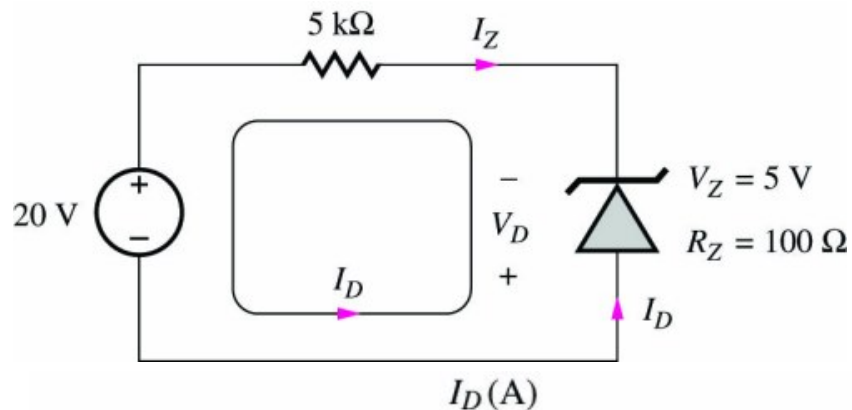


Load-line equation :  
(KVL along the loop)

$$V_D + 5000I_D + 20 = 0$$


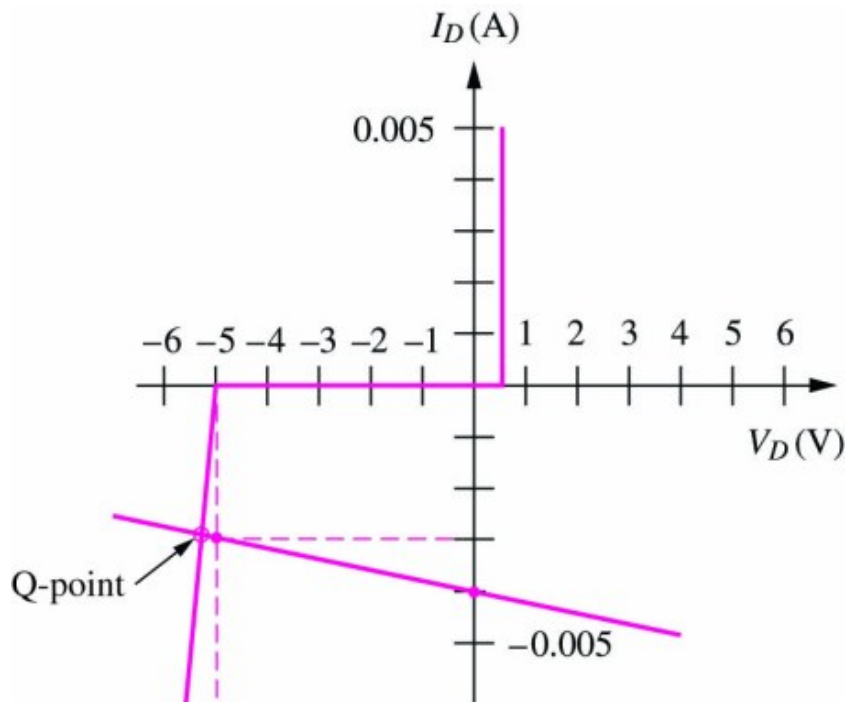
**Using graphic analysis:**

Choose 2 points (0V, -4mA) and (-5V, -3mA) to draw the load line.


It intersects with *i-v* characteristic at **Q-point (-2.9 mA, -5.2 V).**



# Example 2 – Piecewise Linear Model

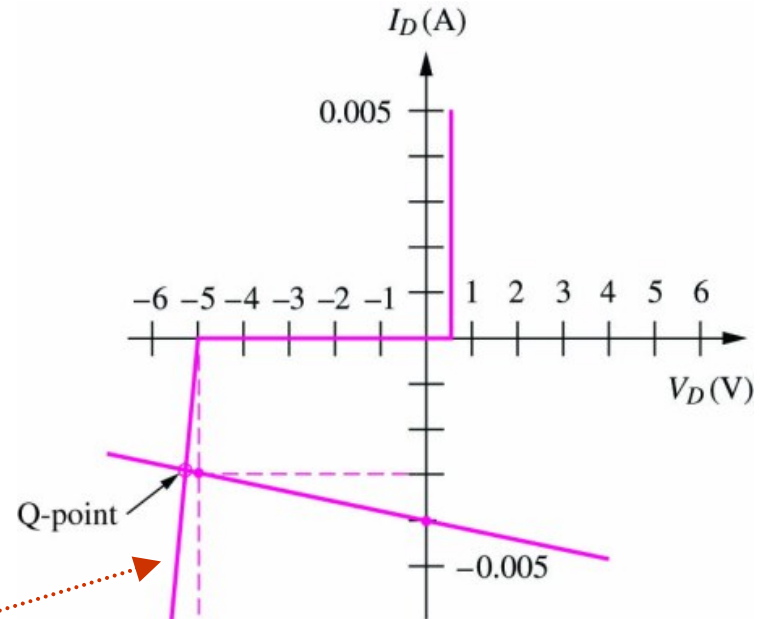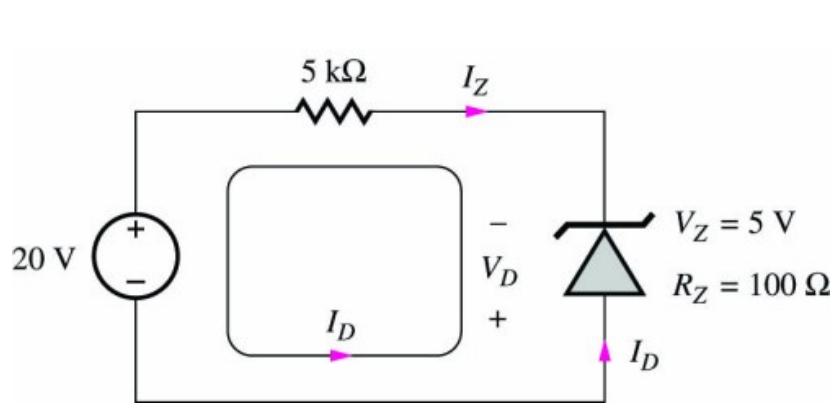

Using piecewise linear model:

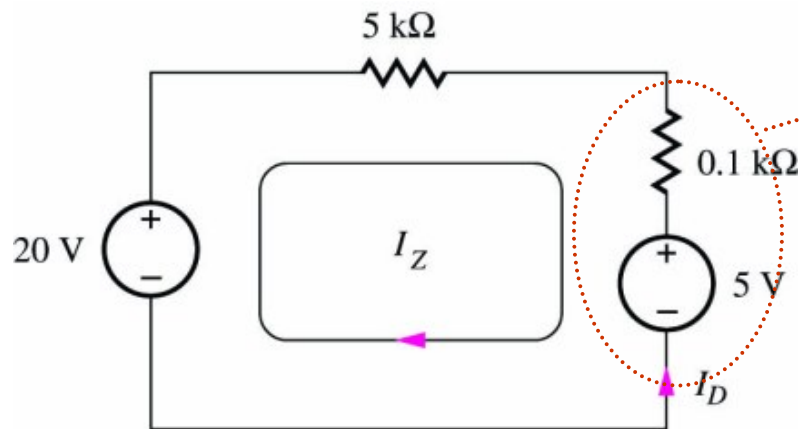

$$I_Z = -I_D > 0$$

Assume in breakdown region

$$-20 + 5100I_Z + 5 = 0$$


$$I_Z = \frac{(20 - 5)V}{5100\Omega} = 2.94\text{mA}$$

Since  $I_Z > 0$  ( $I_D < 0$ ), solution is consistent with Zener breakdown assumption.



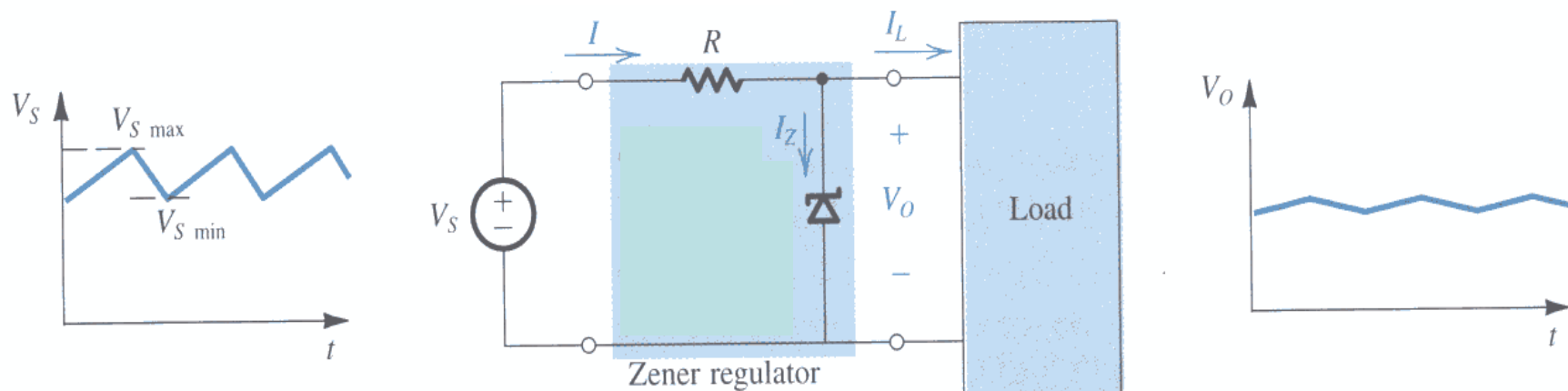
# Voltage Regulator

- Function: to maintain a constant voltage across the load when the source voltage or the load current vary.



# Voltage Regulator

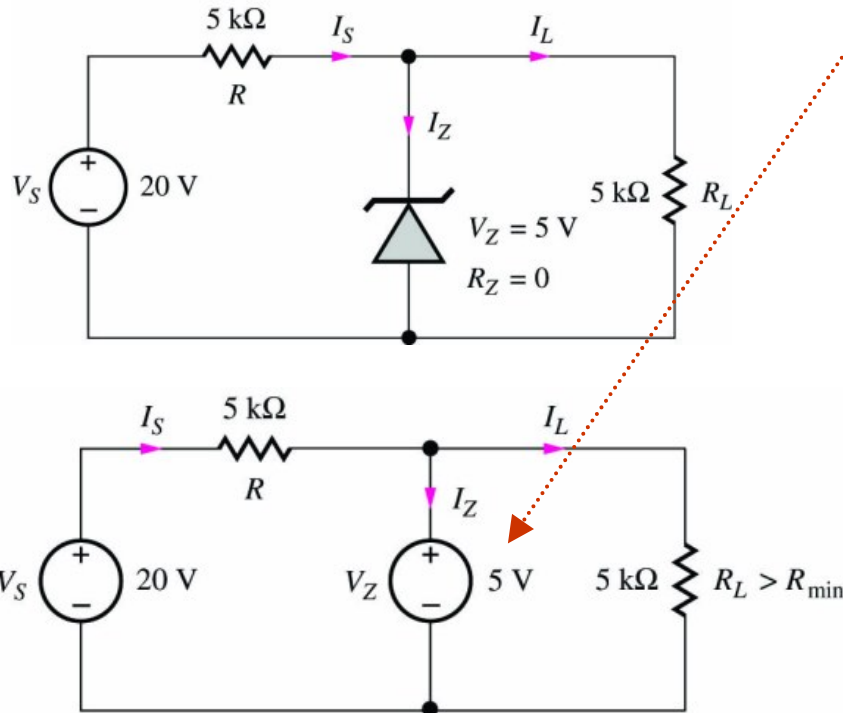

Use constant voltage drop model:

$$I_S = \frac{V_S - V_Z}{R} = \frac{(20 - 5)V}{5k\Omega} = 3\text{mA}$$

$$I_L = \frac{V_Z}{R_L} = \frac{5V}{5k\Omega} = 1\text{mA}$$

$$I_Z = I_S - I_L = 2\text{mA}$$

For proper regulation,  $I_Z > 0$ . If  $I_Z < 0$ , Zener diode no longer controls voltage across load resistor and the regulator is said to have “dropped out of regulation”.


Zener diode keeps voltage across load resistor constant

$$\therefore I_Z = \frac{V_S}{R} - V_Z \left( \frac{1}{R} + \frac{1}{R_L} \right) > 0 \quad R_L > \frac{R}{\left( \frac{V_S}{V_Z} - 1 \right)} = R_{\min}$$



# Example 3

Zener diode model

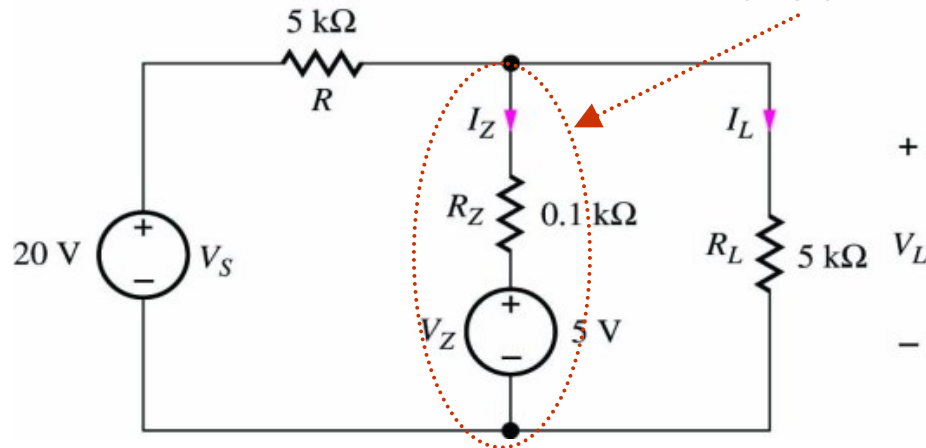

**Problem:** Find  $V_L$  and  $I_Z$  using the piece-wise linear model.

**Given data:**

$$V_S = 20 \text{ V}, R = 5 \text{ k}\Omega, \\ R_Z = 0.1 \text{ k}\Omega, V_Z = 5 \text{ V}$$

**Analysis:**

KCL at output node:

$$\frac{V_L - 20}{5000} + \frac{V_L - 5}{100} + \frac{V_L}{5000} = 0$$

$$\therefore V_L = 5.19 \text{ V}$$


$$I_Z = \frac{V_L - 5}{100} = \frac{5.19 - 5}{100} = 1.9 \text{ mA} > 0$$

Diode is actually operating in breakdown region as assumed.





# Line and Load Regulation

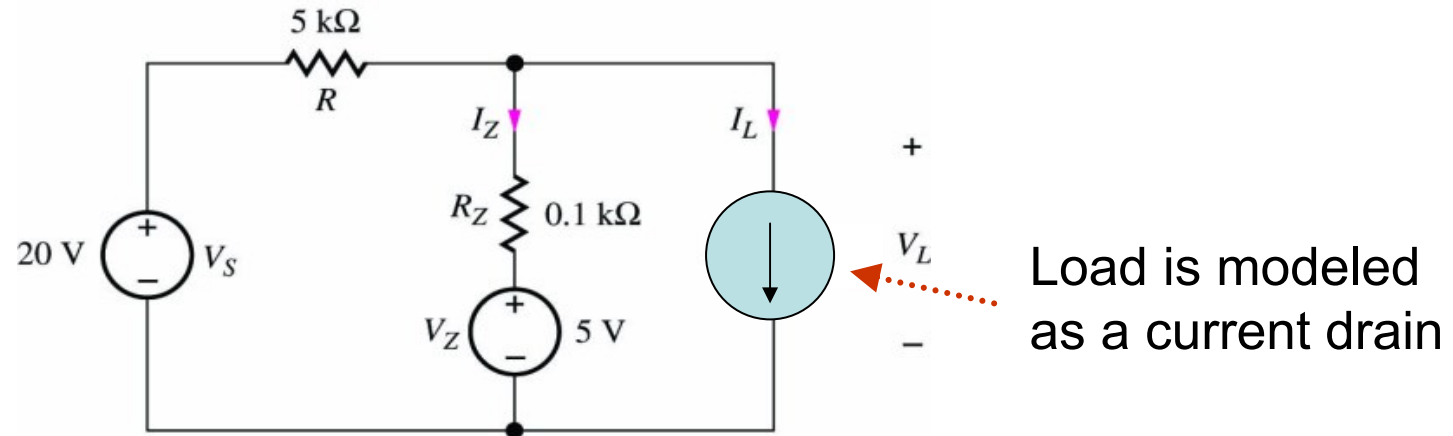

By superposition:

$$V_L = \frac{R}{R + R_z} V_Z + \frac{R_z}{R + R_z} V_S - (R_z // R) I_L$$

*Line regulation*  $\equiv \frac{\partial V_L}{\partial V_S} = \frac{R_z}{R + R_z}$  (characterizes how sensitive output voltage is to input voltage changes)

*Load regulation*  $\equiv \frac{\partial V_L}{\partial I_L} = -(R_z // R) [\Omega]$  (characterizes how sensitive output voltage is to load current changes)




# Topics to cover ...

- Voltage Regulation - Zener Diode
- **Rectifiers**
- DC-to-DC converters
- Wave shaping circuits
- Photodiode and LED





# AC-DC Converter

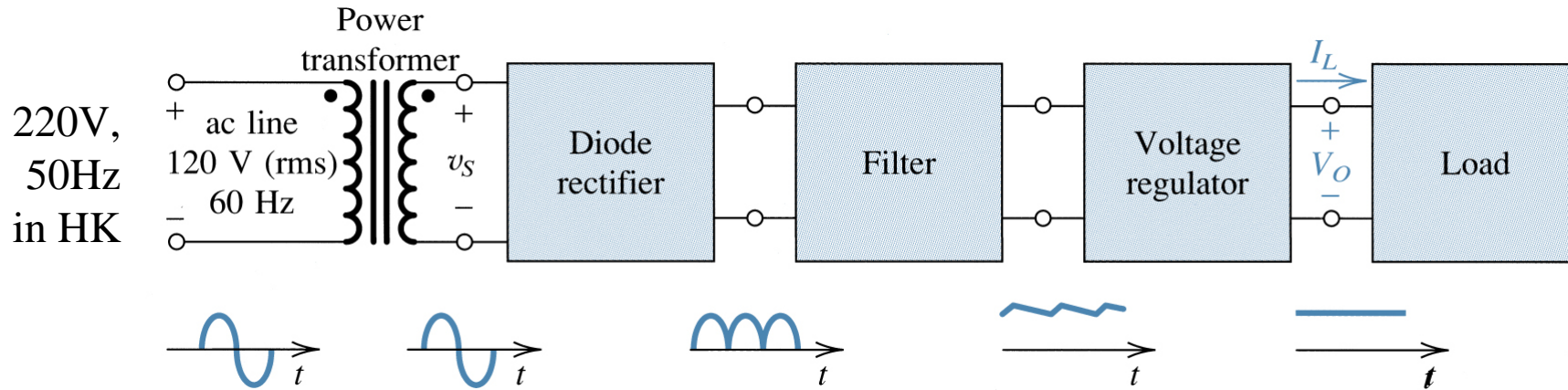



- Transformer:
  - step down AC voltage amplitude
  - Isolate equipment from power-line
- Rectifier:
  - converts an ac input to a unipolar output
- Filter:
  - convert the pulsating input to a nearly constant dc output
- Regulator:
  - Reduce the **ripple** of the dc voltage



# Half-Wave Rectifier

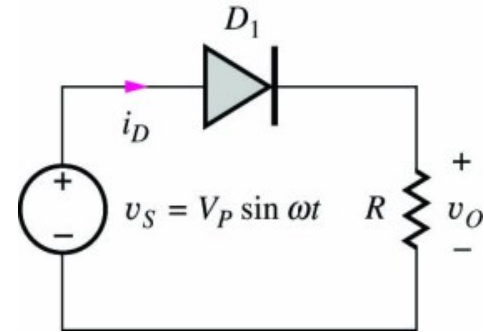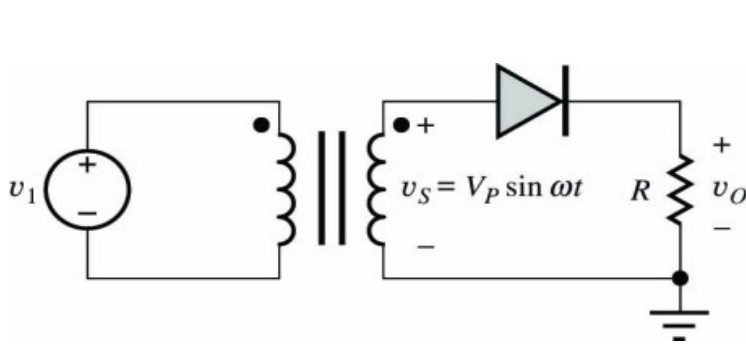


Using ideal Diode model:

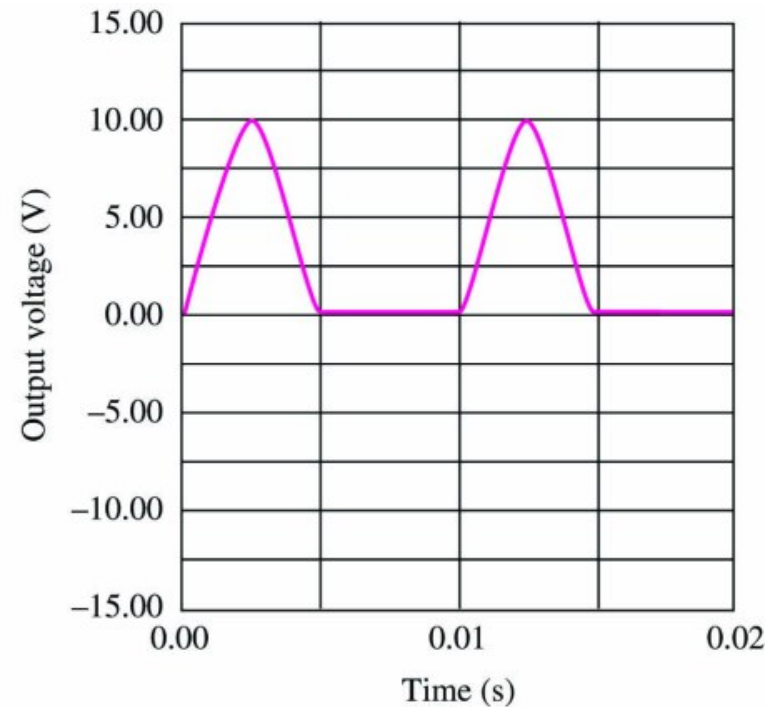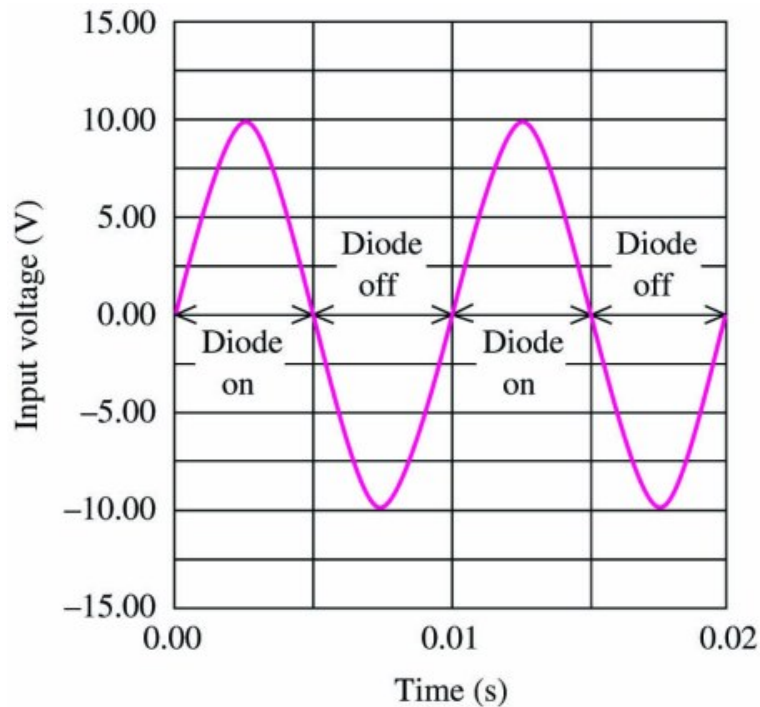

# Half-Wave Rectifier

Using Constant Voltage Drop model:

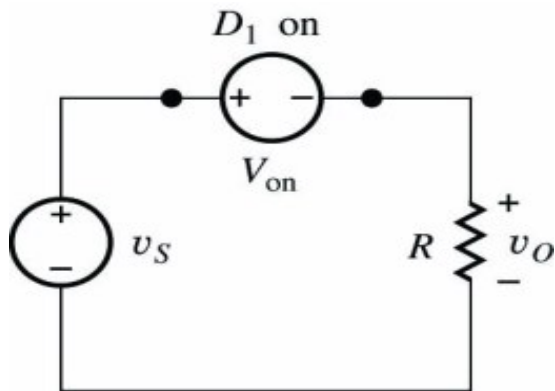


When diode is ON:

$$v_o = (V_P \sin \omega t) - V_{on}$$


When diode is OFF:

$$v_o = 0.$$

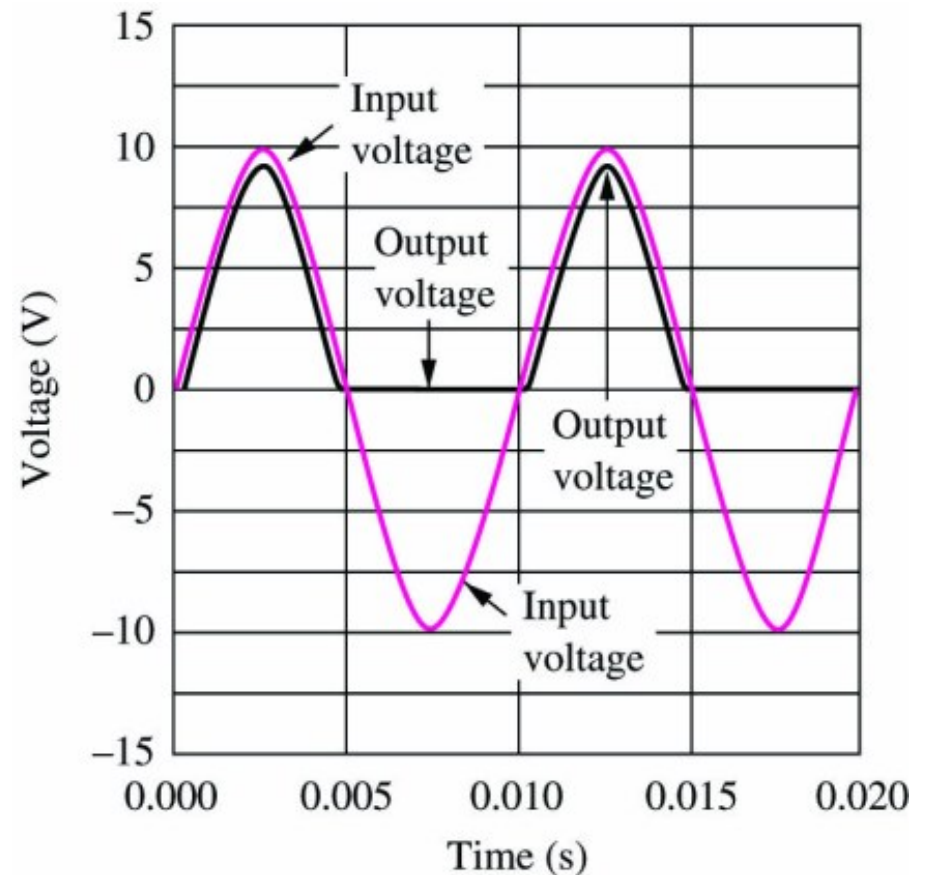Time-varying components in circuit output can be suppressed using a filter capacitor.




# Peak Detector Circuit

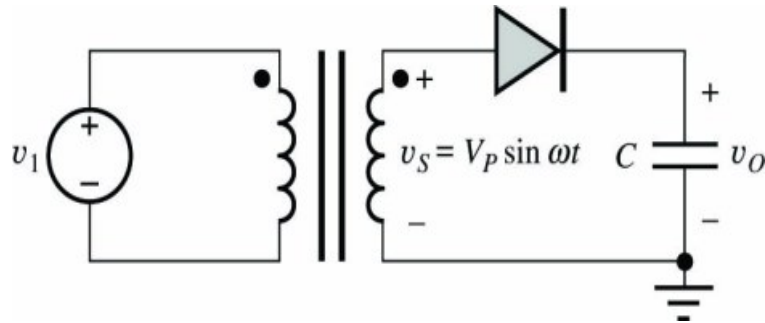

Replace R with C

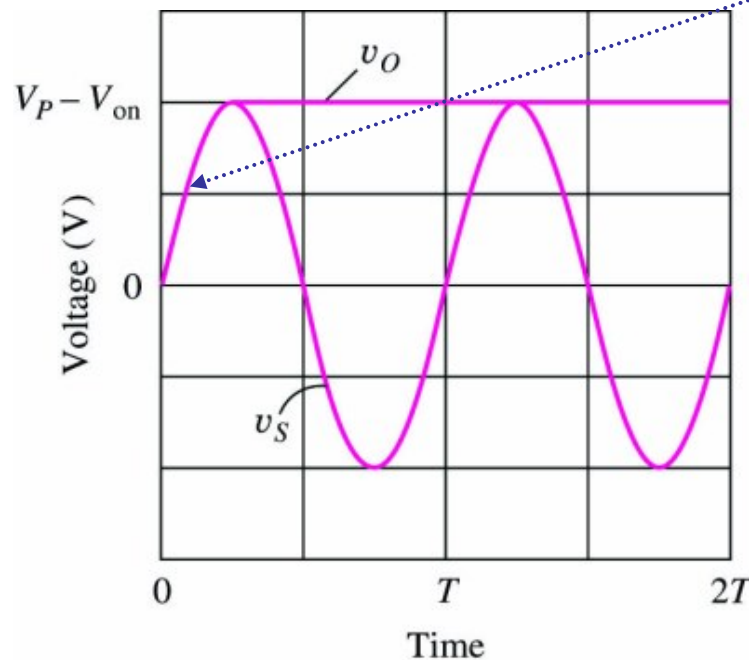As input voltage rises, diode is on and capacitor (initially discharged) charges up to  $V_S - V_{on}$





At the peak of input, diode current tries to reverse, diode cuts off, capacitor has no discharge path and retains constant, thereby providing a dc output voltage:

$$V_{dc} = V_P - V_{on}$$



# Half-Wave Rectifier with $RC$ Load

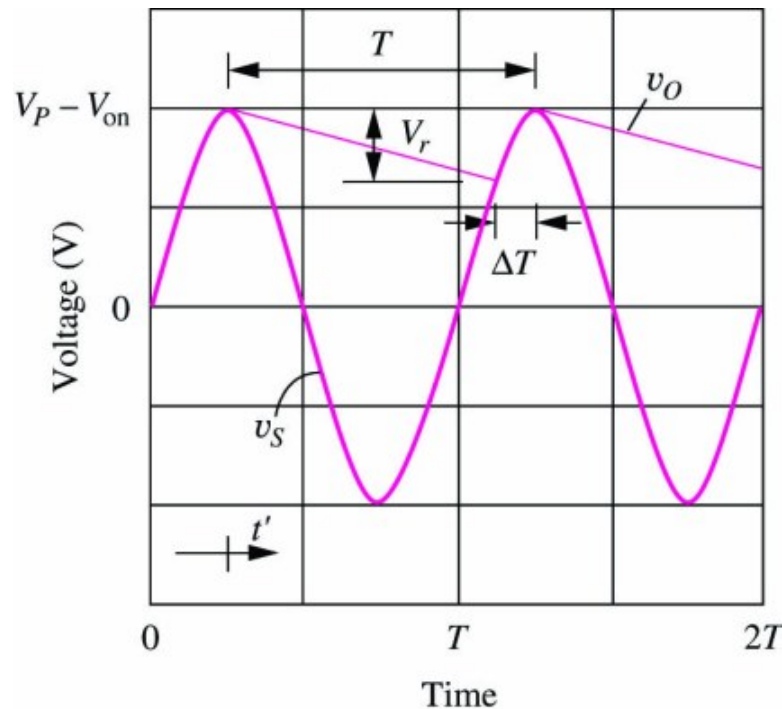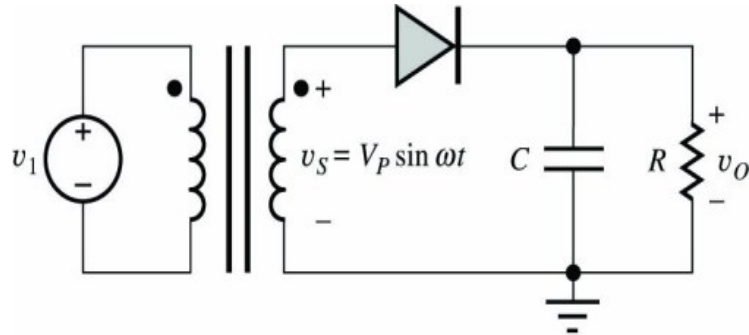

- As input voltage rises during first quarter cycle,
  - diode is on
  - capacitor charges up to peak value of input voltage
- After the peak of input,
  - Input voltage  $< V_P$
  - Diode cuts off
  - Capacitor discharges exponentially through  $R$
  - Discharge continues till input voltage exceeds output voltage which occurs near peak of next cycle.
- This process then repeats once every cycle



# Half-Wave Rectifier with $RC$ Load

Output voltage is not constant as in ideal peak detector, but has **ripple voltage**  $V_r$



Diode conducts for a short time  $\Delta T$  called **conduction interval** during each cycle and its angular equivalent is called **conduction angle**  $\theta_c$ .

During discharge period,

$$v_o(t) = (V_P - V_{on}) \exp(-t / RC)$$


$$\cong (V_P - V_{on})(1 - t / RC) \quad \text{for } t \ll RC$$
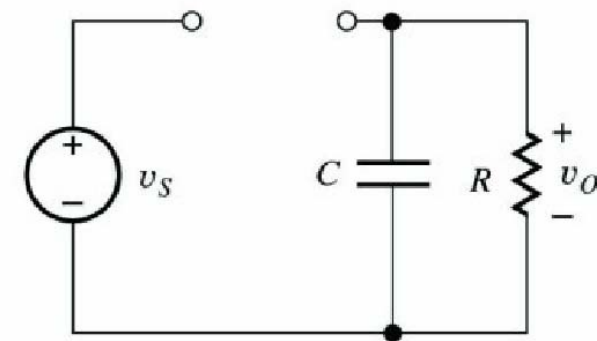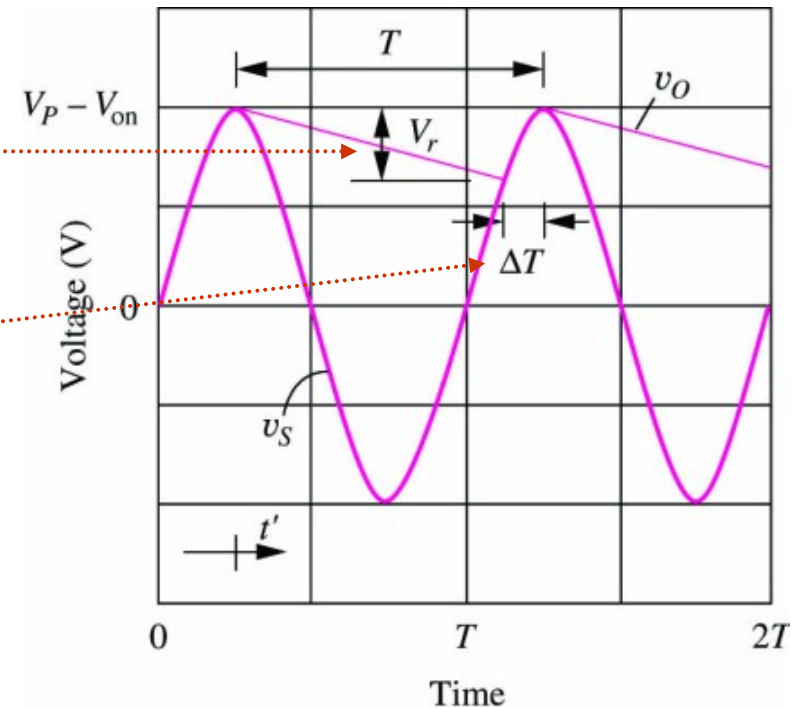
$$V_r \cong (V_P - V_{on}) \frac{T - \Delta T}{RC} \cong (V_P - V_{on}) \frac{T}{RC} \quad \text{for } \Delta T \ll T$$





# Half-Wave Rectifier with $RC$ Load

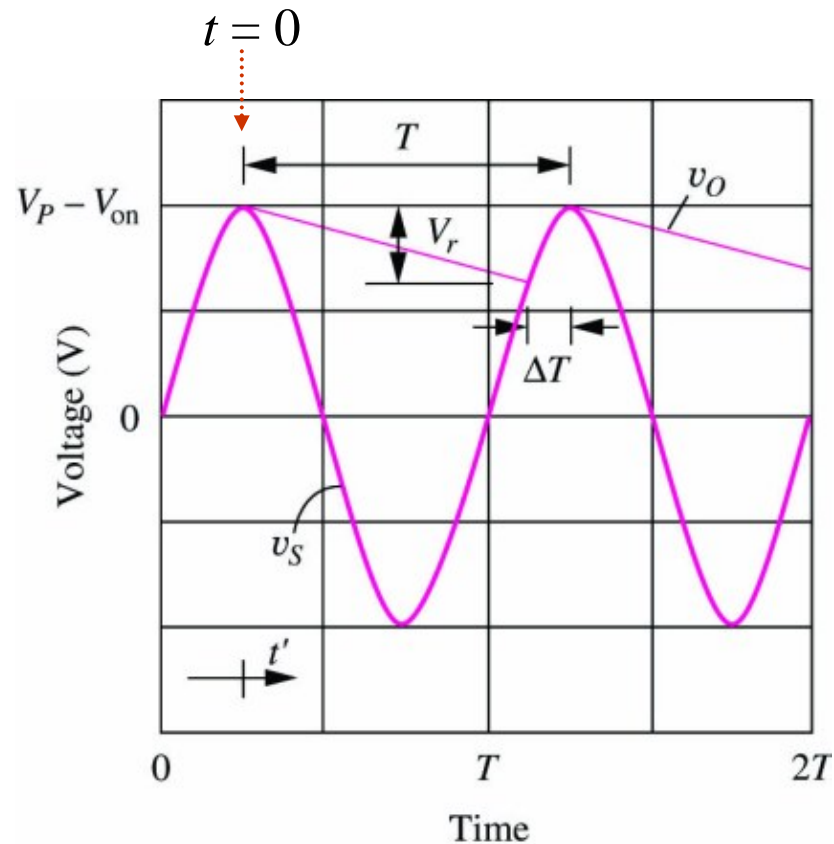

To find the conduction period,

$$(V_P - V_{on}) \exp\left(-\frac{T - \Delta T}{RC}\right) = V_P \cos \omega(T - \Delta T) - V_{on}$$

Assume  $\Delta T \ll T$ ,  
It can be solved that,

$$\Delta T \cong \frac{1}{\omega} \sqrt{\frac{2T}{RC} \frac{(V_P - V_{on})}{V_P}} = \frac{1}{\omega} \sqrt{\frac{2V_r}{V_P}}$$

$$\theta_c = \omega \Delta T = \sqrt{\frac{2V_r}{V_P}} \quad \text{where} \quad \omega = \frac{2\pi}{T}$$



# Example 4

**Problem:** Find dc output voltage, output current, ripple voltage, conduction interval, conduction angle of RC loaded half-wave rectifier.

**Given data:** secondary voltage  $V_{rms} = 12.6$  (60 Hz),  $R = 15 \Omega$ ,  $C = 25,000 \mu F$ ,  $V_{on} = 1 V$

**Analysis:**  $V_{dc} = V_P - V_{on} = (12.6\sqrt{2} - 1)V = 16.8V$

$$I_{dc} = \frac{V_P - V_{on}}{R} = \frac{16.8V}{15\Omega} = 1.12A$$

Using discharge interval  $T = 1/60$  s,

$$V_r \cong (V_P - V_{on}) \frac{T}{RC} = 0.747V$$

$$\theta_c = \sqrt{\frac{2V_r}{V_P}} = 0.290 \text{ rad or } 16.6^\circ$$

$$\Delta T = \frac{\theta_c}{\omega} = \frac{\theta_c}{2\pi f} = \frac{0.29}{120\pi} = 0.769ms$$

## Check of result:


The hidden assumptions are justified:

$$\Delta T \ll T = 1/60 = 16.7ms$$


$$T \ll RC = 375ms$$



# Peak Diode Current

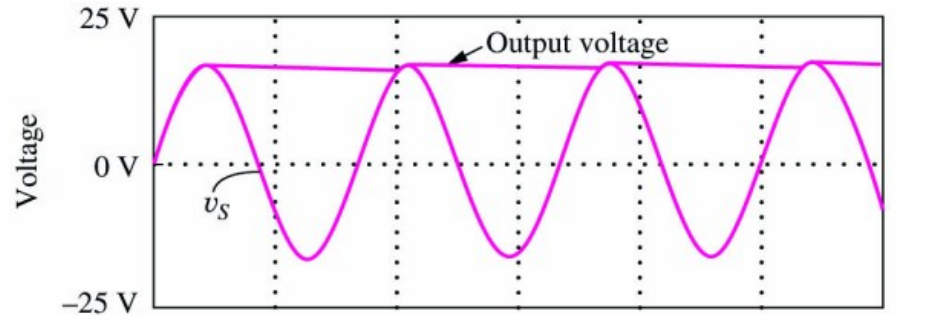

(a)

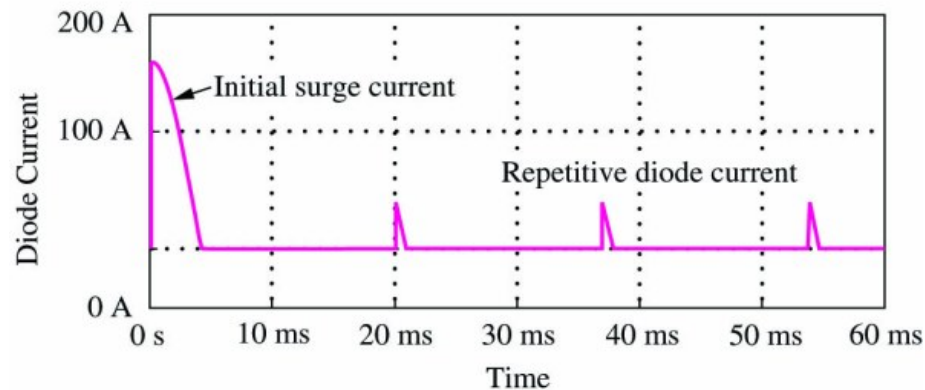


(b)

- Nonzero current exists in diode for only a very small fraction of period  $T$
- An almost constant dc current flows out of filter capacitor to load
- Total charge lost from capacitor in each cycle is re-supplied by diode during the conduction interval


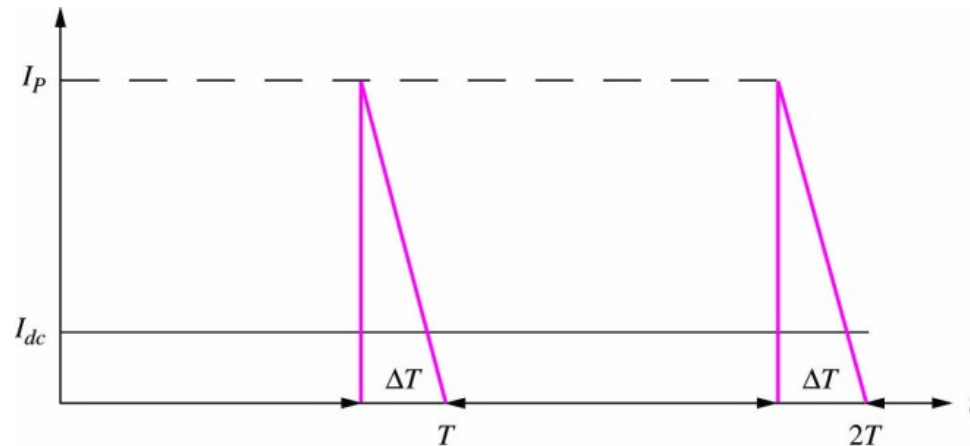
# Peak Diode Current

- Let's model the repetitive current pulse is modeled as triangle of height  $I_p$  and width  $\Delta T$ ,




Charge supplied during diode conduction:  $Q = I_p \frac{\Delta T}{2}$

Charge transferred to the load in each cycle:

$$Q \approx I_{dc} T \quad \therefore I_p = I_{dc} \frac{2T}{\Delta T} \quad \left( i \equiv \frac{dQ}{dt} \Rightarrow Q = \int i(t) dt \right)$$




# Surge Current

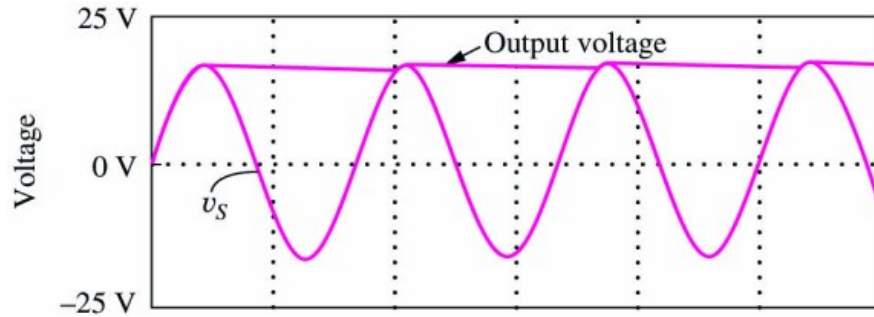

(a)

During first quarter cycle,
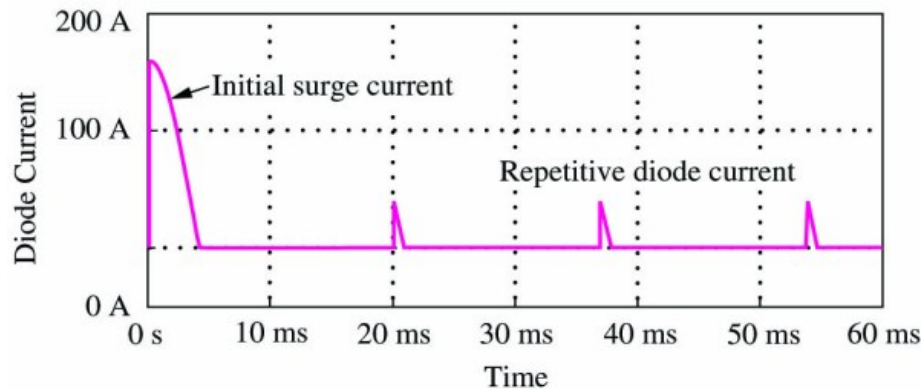
$$i_d(t) = i_c(t) \cong C \left( \frac{d}{dt} V_P \sin \omega t \right) \\ = \omega C V_P \cos \omega t$$




(b)

Peak values of this initial surge current occurs at  $t = 0^+$ :

$$I_{SC} = \omega C V_P$$




# Peak Inverse Voltage (PIV)

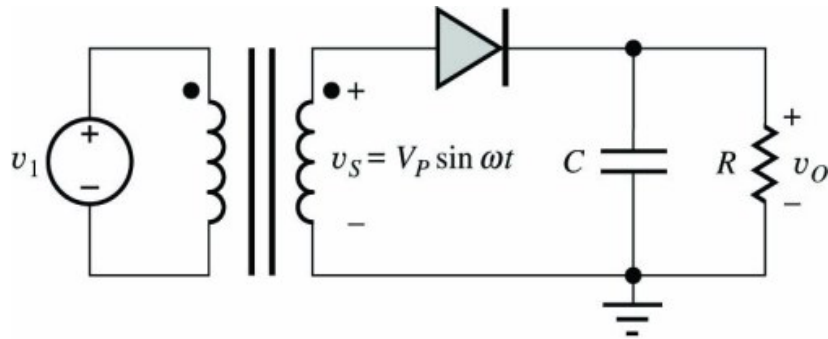

When diode is off, reverse-bias across diode is  $V_{dc} - v_s$ . When  $v_s$  reaches negative peak, the diode sees the **peak inverse voltage (PIV)**


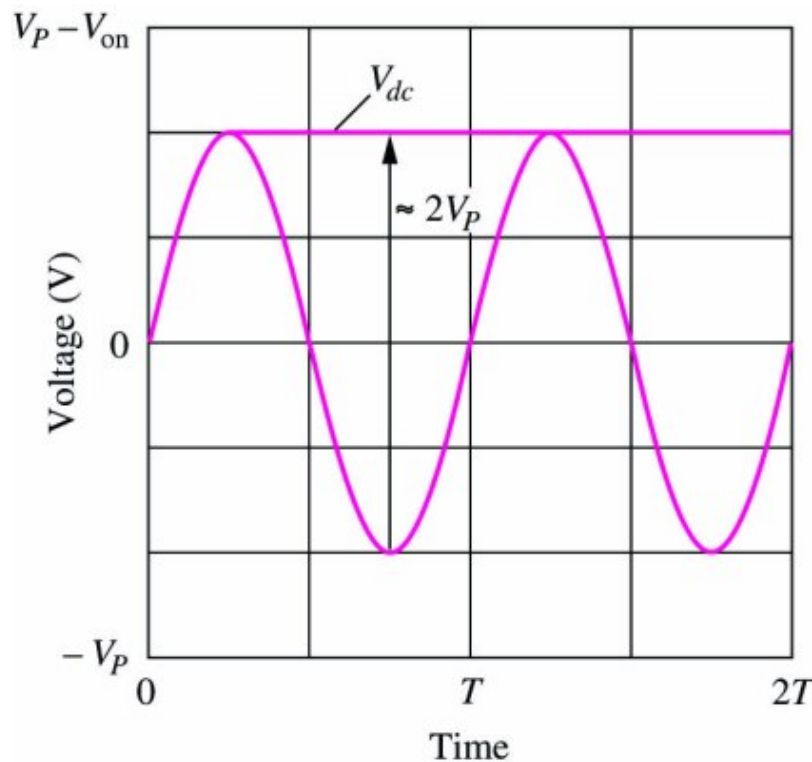
$$\text{PIV} \geq V_{dc} - v_s^{\min} = V_P - V_{on} - (-V_P) \cong 2V_P$$



The diode should have a breakdown voltage greater than the PIV in order to avoid entering breakdown region.



# Full-Wave Rectifier

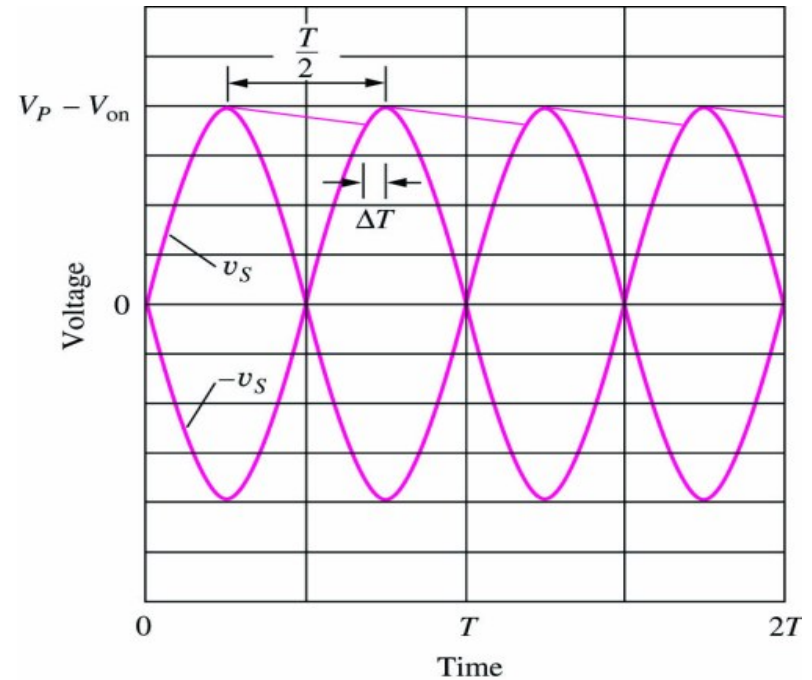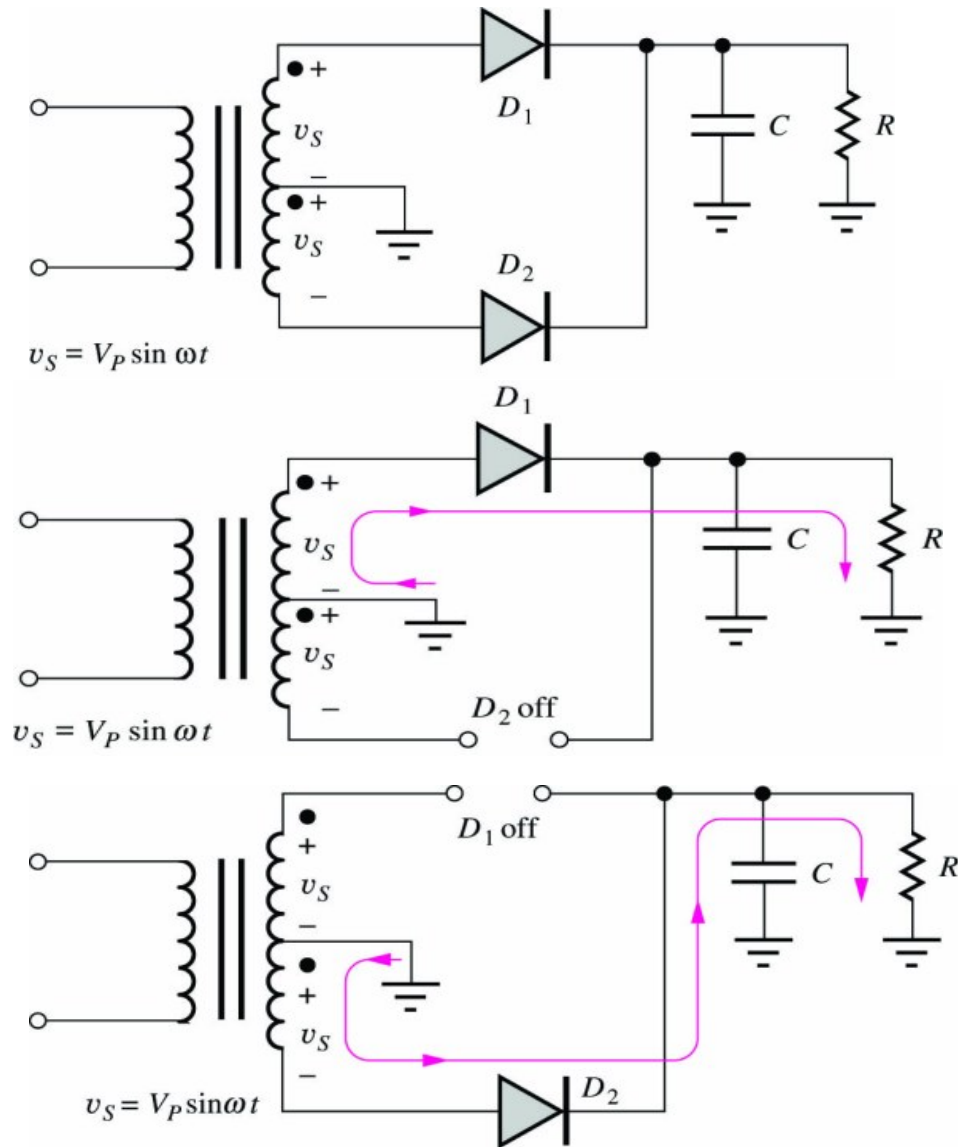

- Capacitor discharge time halved  $\rightarrow$  Require half the filter capacitance to achieve a given ripple voltage
- Output DC =  $V_P - V_{on}$
- PIV =  $2V_P - V_{on} \approx 2V_P$



# Capacitor Size




(b)

A 0.175F capacitor





# Full-Wave Bridge Rectifier

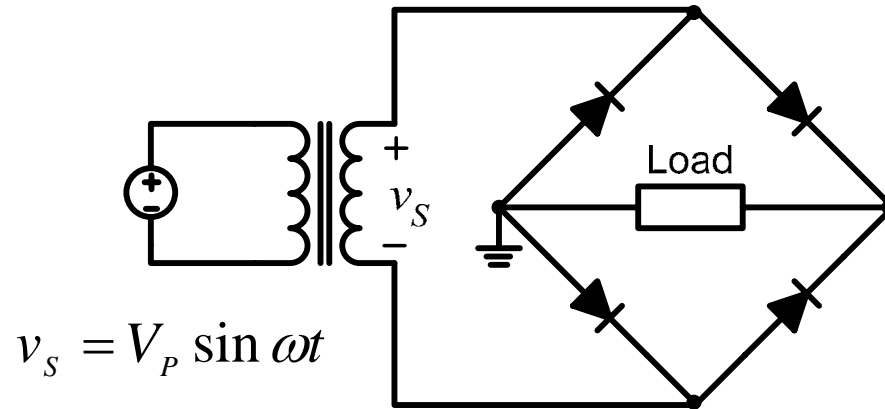


- Current always flows in one direction through the load regardless of whether  $v_S$  is positive or negative.
- Which direction?




# Full-Wave Bridge Rectifier


- $v_S$  positive:

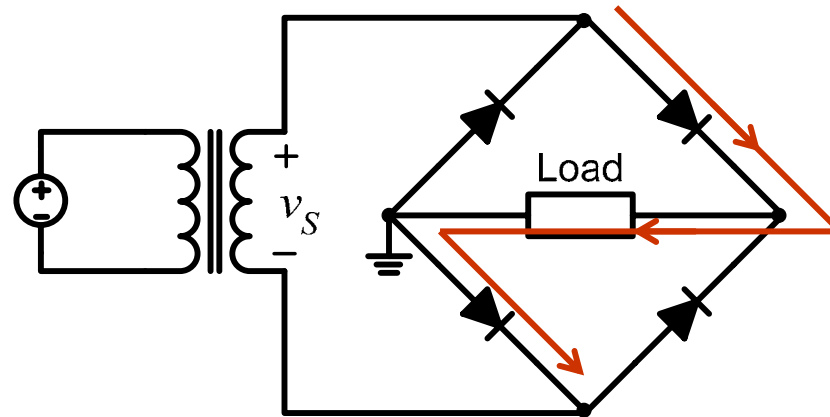

- $v_S$  negative:

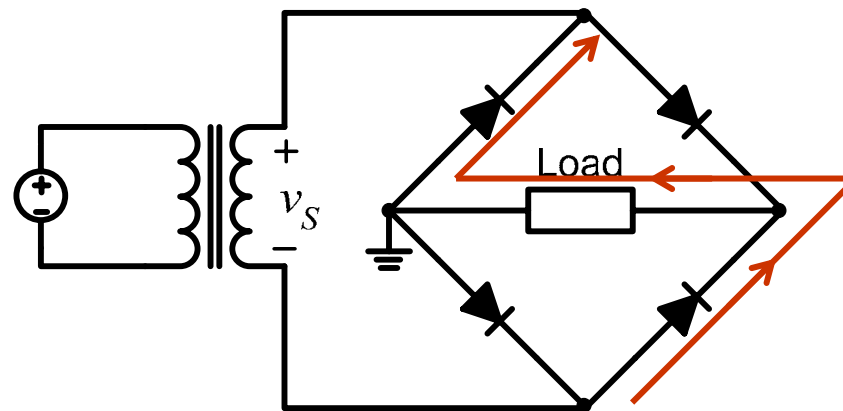


# Full-Wave Bridge Rectifier

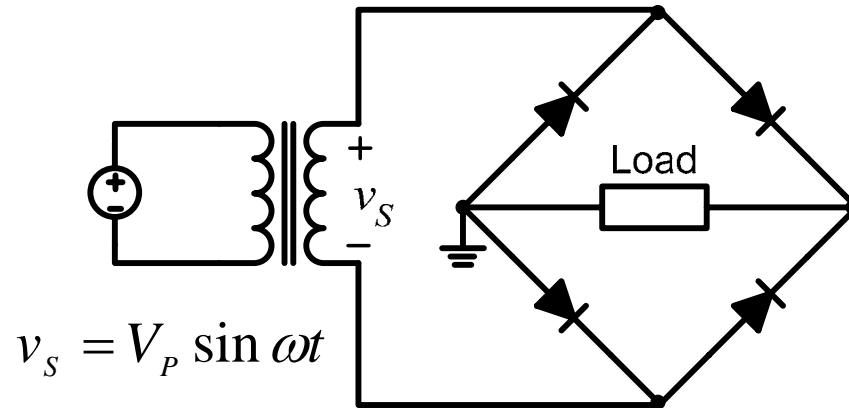

- Full wave rectification is achieved without center-tapped transformer by using two extra diodes
- Filter capacitance is halved compared to that of the half-wave rectifier
- Two diodes in either conduction path
- Output DC =  $V_P - 2V_{on}$



# Reduced Peak Inverse Voltage

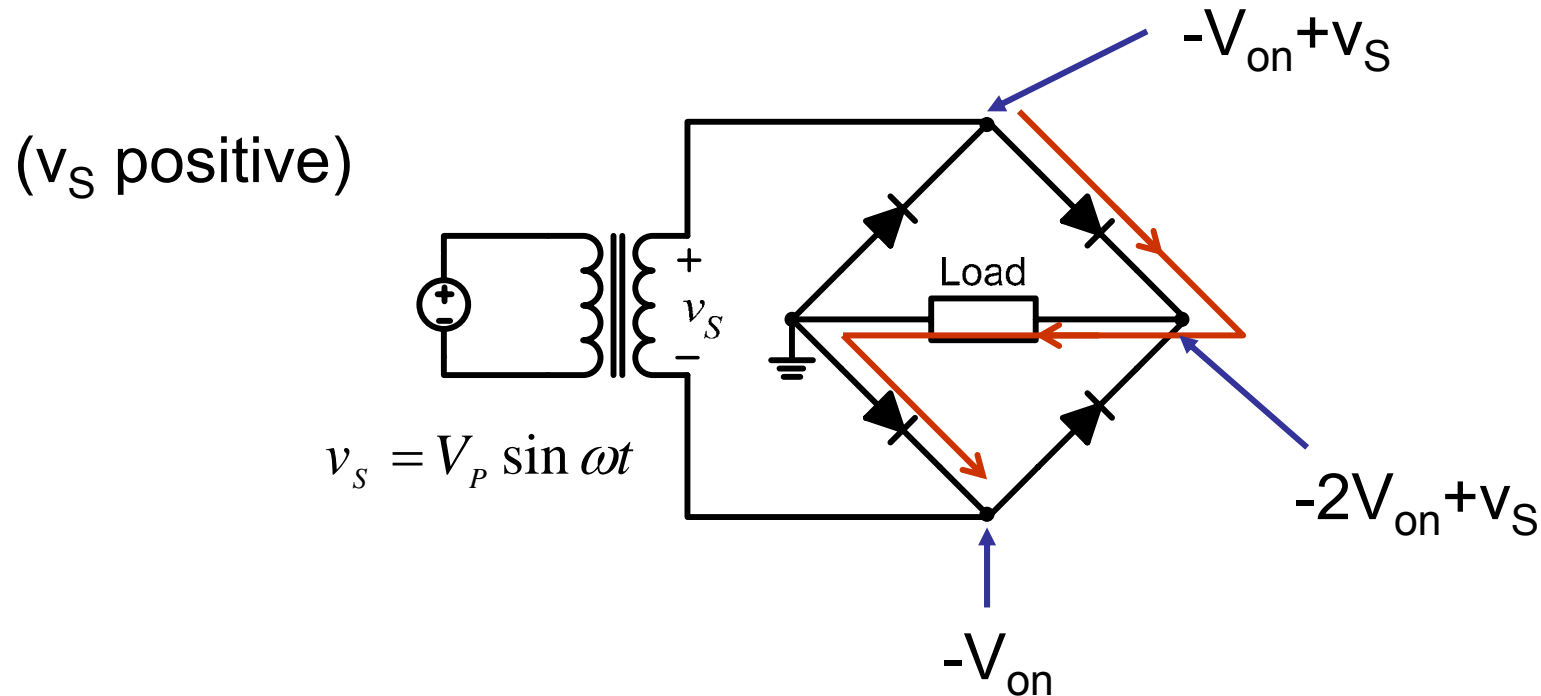

- $PIV = \text{Max}(-V_{on} + v_S) = V_p - V_{on} \approx V_P$
- So diodes with lower breakdown voltage can be used  
→ Cheaper



# Rectifier Topology Comparison

	Output DC Voltage	PIV	Filter capacitance for a same ripple
<b>Half-Wave</b>	$V_P - V_{ON}$	$2V_P - V_{ON}$	$C = \frac{(V_P - V_{on})T}{V_r R}$
<b>Center-Tapped Full-Wave</b>	$V_P - V_{ON}$	$2V_P - V_{ON}$	$C/2$
<b>Bridge Rectifier Full-Wave</b>	$V_P - 2V_{ON}$	$V_P - V_{ON}$	$C/2$

- Filter capacitor is a major factor in determining cost, size and weight in design of rectifiers.
- Low PIV is important in high-voltage circuits.



# Example 5

**Problem:** Design rectifier with given specifications.

**Specifications:**  $V_{dc} = 15 \text{ V}$ ,  $V_r < 0.15 \text{ V}$ ,  $I_{dc} = 2 \text{ A}$ ,

**Assumptions:**  $V_{on} = 1 \text{ V}$ , input freq = 50 Hz

**Analysis:** Use full-wave bridge rectifier

$$V_P = V_{dc} + 2V_{on} = 15 + 2 = 17 \text{ V} \quad (V_P \text{ of the transformer output})$$

$$C = \frac{(V_P - V_{on})}{V_r} \frac{T}{2R} = I_{dc} \left( \frac{T/2}{V_r} \right) = 2 \text{ A} \left( \frac{1}{100} \text{ s} \right) \left( \frac{1}{0.15 \text{ V}} \right) = 0.133 \text{ F}$$

$$\Delta T = \frac{1}{\omega} \sqrt{\frac{2V_r}{V_P}} = \frac{1}{50 \cdot 2\pi} \sqrt{\frac{2(0.15 \text{ V})}{17 \text{ V}}} = 0.423 \text{ ms}$$

$$I_P = I_{dc} \left( \frac{2}{\Delta T} \right) \left( \frac{T}{2} \right) = 2 \text{ A} \frac{(1/50) \text{ s}}{0.423 \text{ ms}} = 94.6 \text{ A} \quad \text{PIV} = V_P - V_{ON} = 16 \text{ V}$$




# Topics to cover ...


- Voltage Regulation - Zener Diode
- Rectifiers
- **DC-to-DC converters**
- Wave shaping circuits
- Photodiode and LED



# Boost Converter

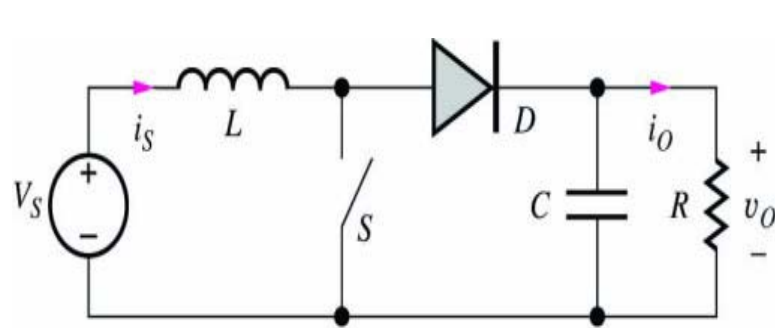


Switching

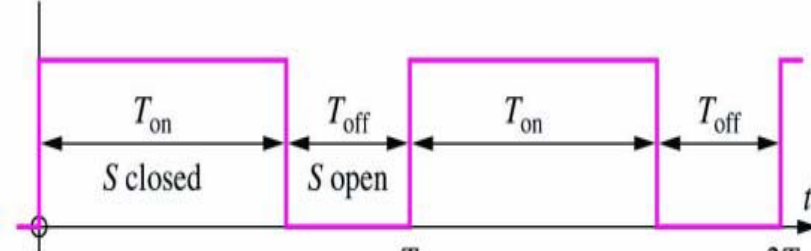

When switch is closed, diode is off.

At the end of  $T_{on}$ :
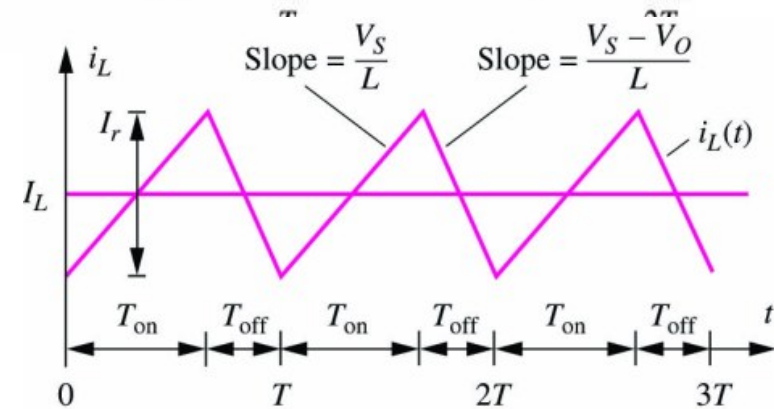
$$i_L(T_{on}) = i_L(0^+) + \frac{1}{L} \int_0^{T_{on}} V_S dt = i_L(0^+) + \frac{V_S}{L} T_{on}$$



When switch is open, diode is on.

Assuming constant  $v_O$ , at the end of  $T_{off}$ :

$$i_L(T) = i_L(0^+) + \frac{V_S}{L} T_{on} + \frac{V_S - V_O}{L} T_{off}$$

In steady state:

$$i_L(T) = i_L(0^+) \quad \therefore V_O = \frac{V_S}{1 - \delta}$$

where  $\delta = T_{on}/T$  is **duty cycle**.

Since  $0 < \delta < 1$ ,  $V_O > V_S$





# Boost Converter

Ripple current is given by  $I_r = \frac{V_S}{L} T_{on}$  or  $I_r = \frac{V_o - V_S}{L} T_{off}$


$$\therefore L = \frac{V_S}{I_r} T_{on} = \frac{V_S T}{I_r} \left( \frac{T_{on}}{T} \right) = \frac{V_S}{I_r f} \delta$$

In ideal converter, power delivered to input of converter is same as power delivered to load resistor.



$$V_S I_S = V_o I_o \quad \text{or} \quad I_S = I_o \frac{V_o}{V_S} = I_o \frac{T}{T_{off}} = \frac{I_o}{1 - \delta}$$

Ripple voltage is given as
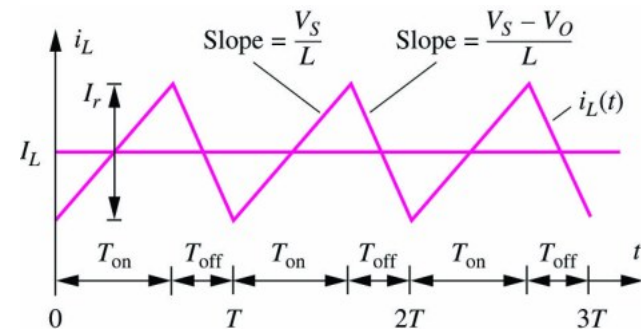
$$V_r \approx \frac{I_o}{C} T_{on} = \frac{V_o T_{on}}{RC} = \frac{V_o T}{RC} \left( \frac{T_{on}}{T} \right) = \frac{V_o T}{RC} \delta$$



# Buck Converter

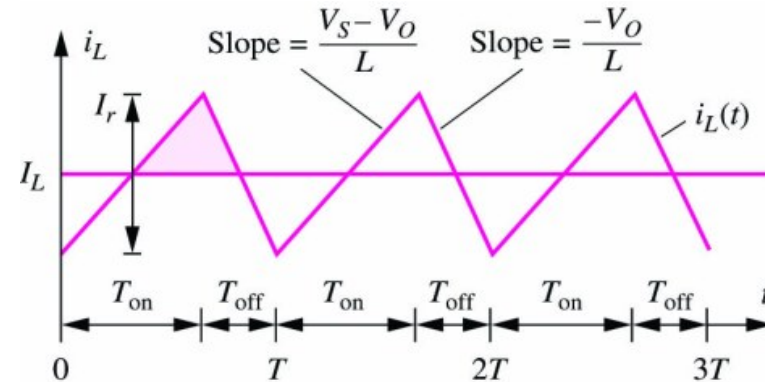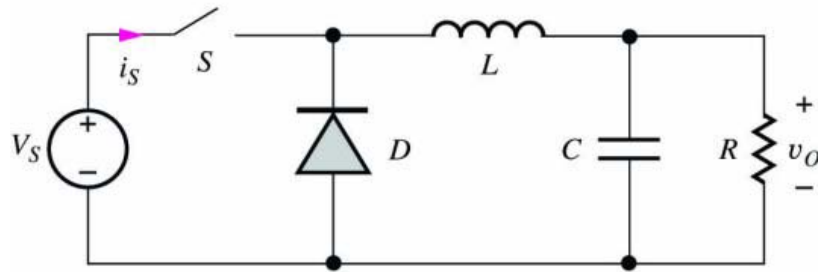

When switch is closed, diode is off:

$$i_L(T_{on}) = i_L(0^+) + \int_0^{T_{on}} \frac{V_S - V_O}{L} dt = i_L(0^+) + \frac{V_S - V_O}{L} T_{on}$$

$$i_L(T) = i_L(0^+)$$

When switch is open, diode is on:

$$\therefore V_O = V_S \frac{T_{on}}{T} = V_S \delta$$

$$i_L(T) = i_L(0^+) + \frac{V_S - V_O}{L} T_{on} - \frac{V_O}{L} T_{off}$$

where  $\delta$  is switch duty cycle.  
Since  $0 < \delta < 1$ ,  $V_O < V_S$ .



# Buck Converter

Ripple current is given by  $I_r = \frac{V_o T_{off}}{L}$  or  $I_r = \frac{V_S - V_o}{L} T_{on}$

$$\therefore L = \frac{V_o T_{off}}{I_r} = \frac{V_o T}{I_r} \left( \frac{T_{off}}{T} \right) = \frac{V_o}{I_r f} (1 - \delta)$$


In ideal converter, power delivered to input of converter is same as power delivered to load resistor.

$$\therefore I_S = I_o \frac{V_o}{V_S} = I_o \frac{T_{on}}{T} = I_o \delta$$


Ripple voltage is given as

$$V_r = \frac{1}{C} \int_{T_{on}/2}^{T_{on}+T_{off}/2} i_r dt = \frac{\Delta Q}{C}$$

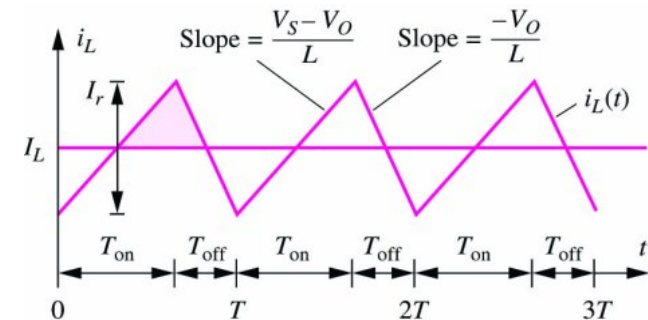
$$\Delta Q = \frac{1}{2} \frac{I_r T_{on}}{2} + \frac{T_{off}}{2} = \frac{I_r T}{8} \quad C = \frac{I_r T}{8 V_r} = \frac{V_o T^2}{V_r 8 L} (1 - \delta)$$




# A second analysis approach

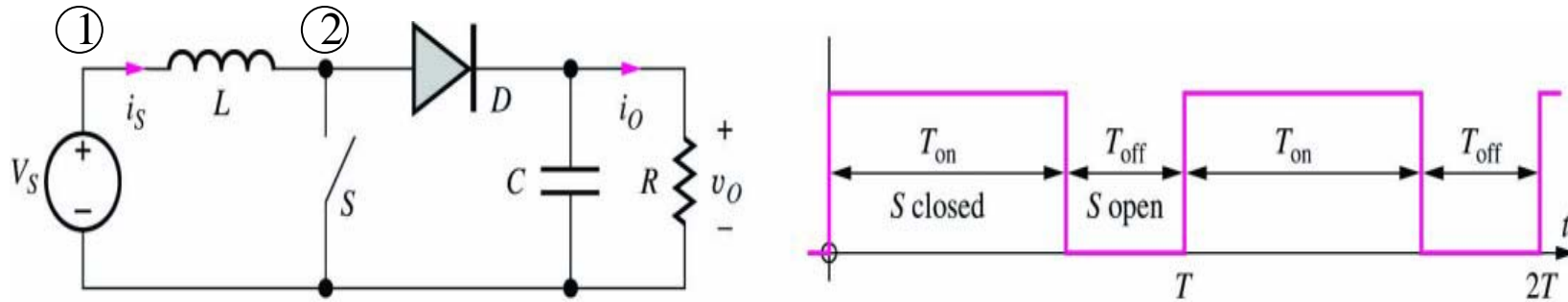

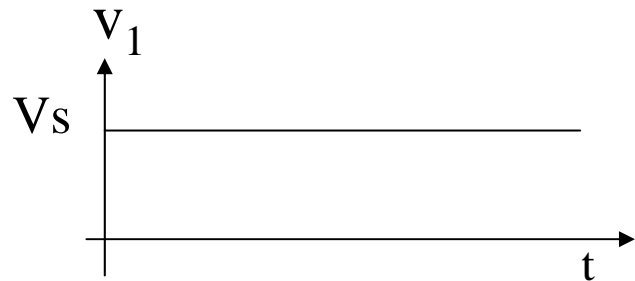In steady state, the average (dc) voltage across the L must be zero, otherwise the inductor current will approach + or - infinity as  $i_L$  takes integration of  $v_L$  over time.



$$\langle v_1 \rangle = V_S$$



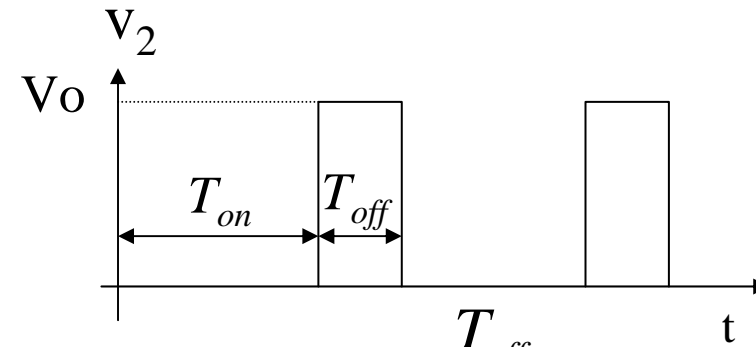


$$\langle v_2 \rangle = \frac{T_{off}}{T} V_O$$


$$\because \langle v_1 - v_2 \rangle = 0 \quad \therefore V_O = \frac{T}{T_{off}} V_S$$



# DC-DC Buck Converter

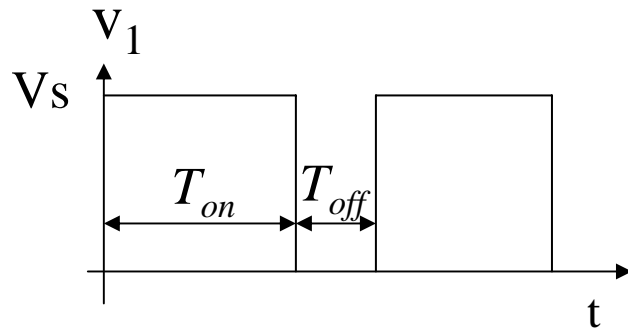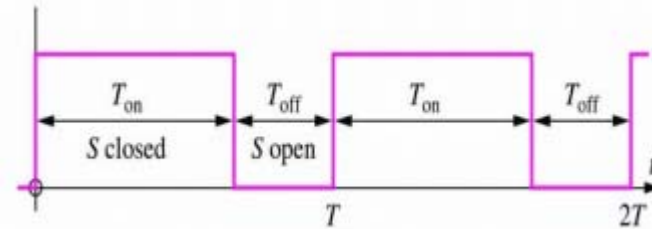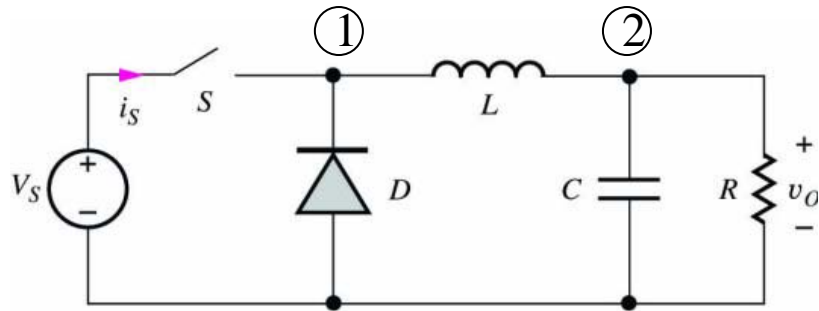
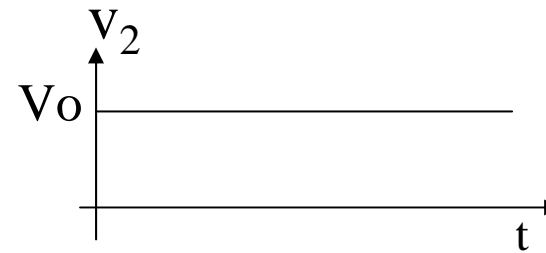
$$\langle v_1 \rangle = \frac{T_{on}}{T} V_S$$



$$\langle v_2 \rangle = V_O$$

$$\therefore V_O = \frac{T_{on}}{T} V_S$$






# Topics to cover ...

- Voltage Regulation - Zener Diode
- Rectifiers
- DC-to-DC converters
- Wave shaping circuits
- Photodiode and LED




# Clamping or DC-Restoring Circuit

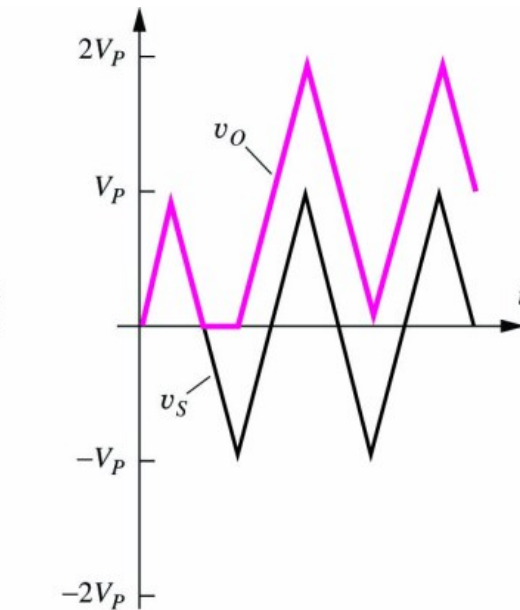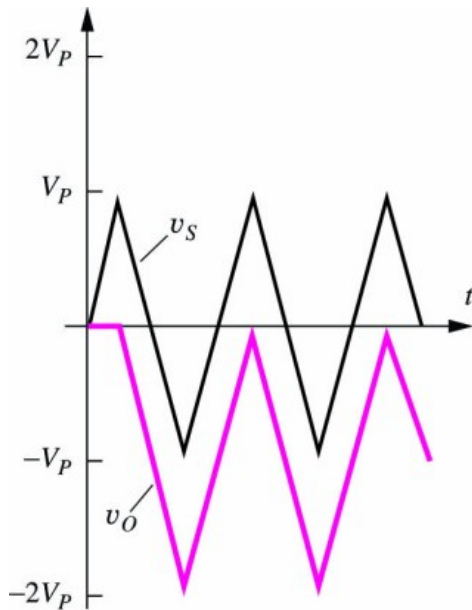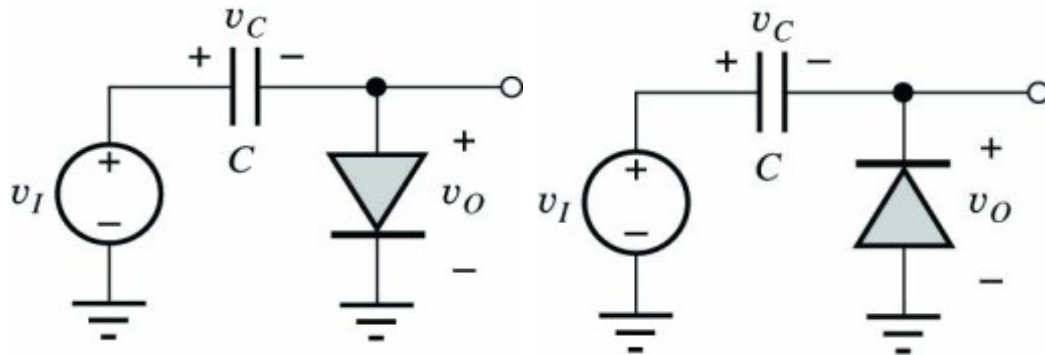


- No DC path between i/p and o/p
- After the initial transient lasting less than one cycle in both circuits, output waveform is an undistorted replica of input
- Both waveforms are clamped to zero
  - Their dc levels are said to be restored
- Clamping level can also be shifted away from zero by adding a voltage source in series with diode



# Clipping or Limiting Circuits

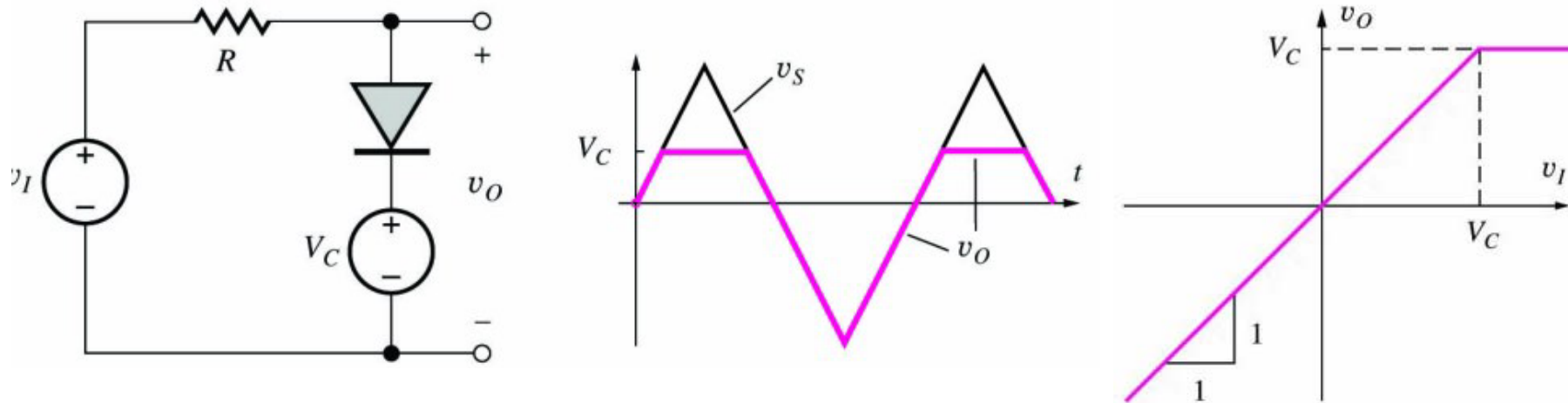

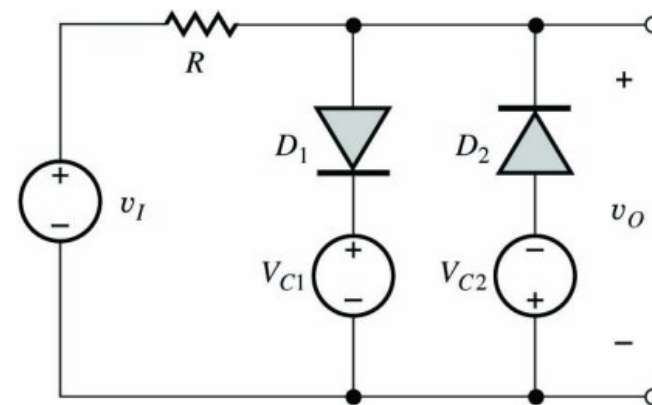- Have DC path between i/p and o/p
- O/p voltage cannot exceed the clipping level




Dual clipping levels






# Photodiodes

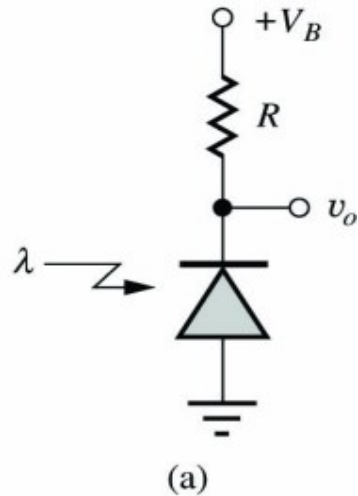

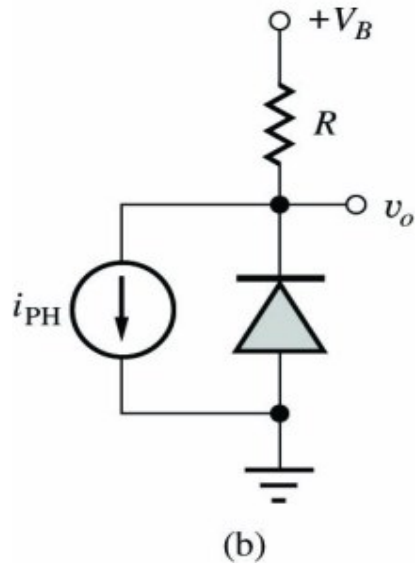- If depletion region of pn junction diode is illuminated with light with sufficiently high frequency, photons can provide enough energy to cause electrons to jump the semiconductor bandgap to generate electron-hole pairs.



- Photodetector: convert light signal into electrical form. Usually reverse biased to increase the depletion layer width.
- Solar cell: convert solar energy into electrical form.



# Light Emitting Diode (LED)

- When electrons and holes recombine, they release energy
- This energy is often released as heat into the lattice, but in some materials, known as *direct bandgap materials*, they release light
- Engineering LEDs can be difficult, but has been done over a wide range of wavelengths

