

*Week 6: Small Signal Analysis for
Single Stage BJT amplifiers*



Topics to cover ...


- Family of single-stage BJT amplifiers
- Small signal analysis
 - Common-Emitter Amplifier
- Common-Emitter Amplifier with Emitter R
- Common-Base Amplifier

Reading Assignment:

Chap 14.1 – 14.5 of Jaeger and Blalock , or
Chap 5.7 of Sedra & Smith



Signal Injection

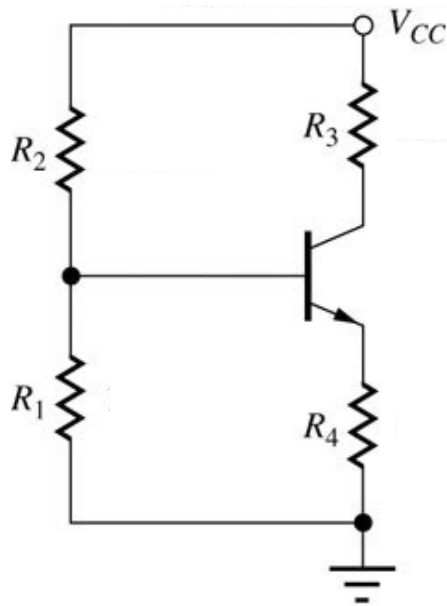


- Transistor is a VCCS:
$$i_C = I_S \exp\left(\frac{v_{BE}}{V_T}\right)$$
- To cause changes in current, v_{BE} must be changed
 - **Base or emitter** terminals can be used as i/p terminal
 - Collector is not used as an i/p terminal because even if Early voltage is considered, collector voltage has negligible effect on terminal currents



Signal Extraction

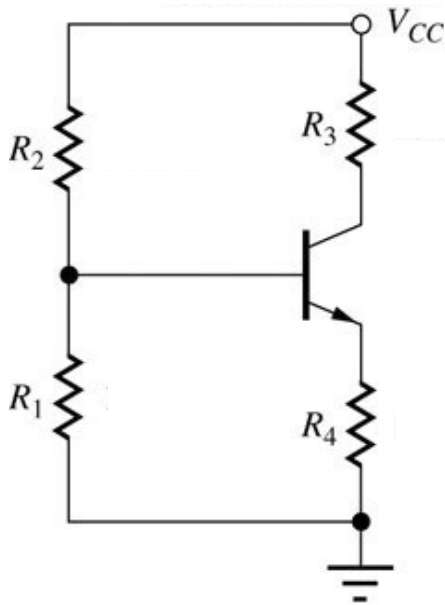- Large changes in i_C or i_E create large voltage drops across collector and emitter resistors
 - **Collector or emitter** can be used as o/p terminal
 - Base terminal is not used as o/p terminal due to small i_B



BJT Amplifier Family

- Constraints for signal injection and extraction yield three families of amplifiers

	<u>Input</u>	<u>Output</u>
– Common-Emitter (C-E):	Base	Collector
– Common-Base (C-B):	Emitter	Collector
– Common-Collector (C-C):	Base	Emitter

- All circuit examples in the following slides use the four-resistor bias circuits to establish Q-point for the various amplifiers.



Topics to cover ...

- Family of single-stage BJT amplifiers
- Small signal analysis
 - Common-Emitter Amplifier
- Common-Emitter Amplifier with Emitter R
- Common-Base Amplifier




Using Small Signal Models in BJT ckt Analysis

Steps for using small-signal models:

- Determine the DC operating point of the BJT
 - in particular, the collector current
- Calculate small-signal model parameters g_m , r_π , & r_e for this DC operating point
- Eliminate DC sources
 - Replace DC voltage sources with short circuits
 - Replace DC current sources with open circuits
- Replace BJT with an equivalent small-signal model
 - Choose most convenient one depending on surrounding circuitry
- Analyze




Common Emitter Amplifier

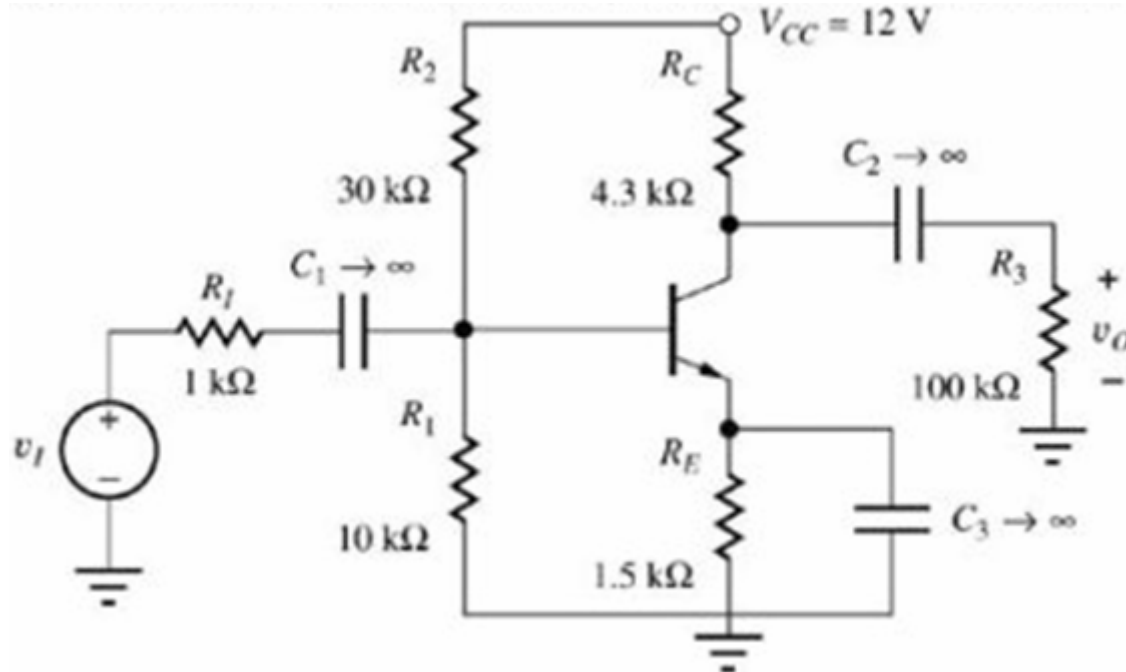

- Biased using the four-resistor network
- AC input is injected to base through a coupling capacitor
- AC output is taken from collector
- Emitter is ac-grounded





DC operating point

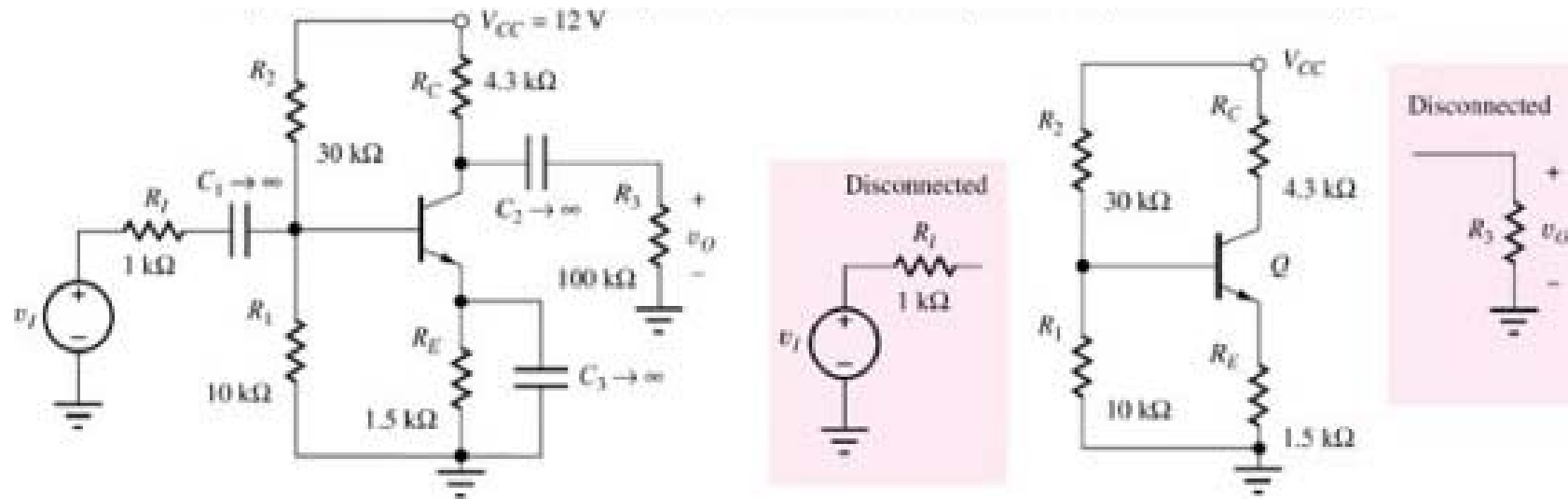

- All capacitors in original amplifier circuits are replaced by open circuits, disconnecting v_I , R_I , and R_3 from circuit
- Q-point can be found from dc equivalent circuit by using DC model for BJT






AC Equivalent

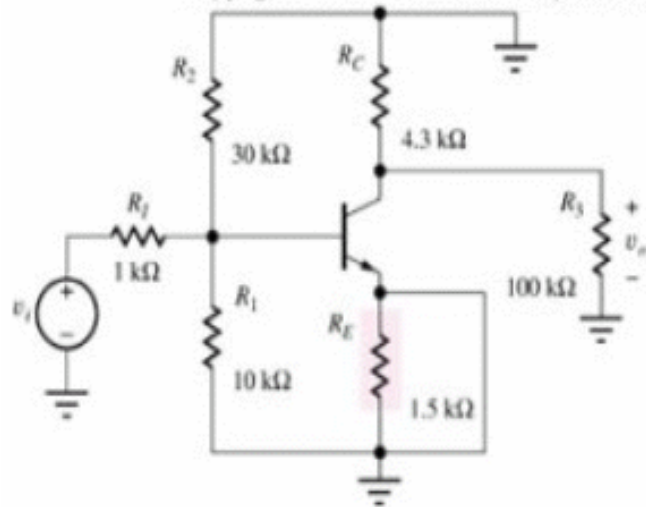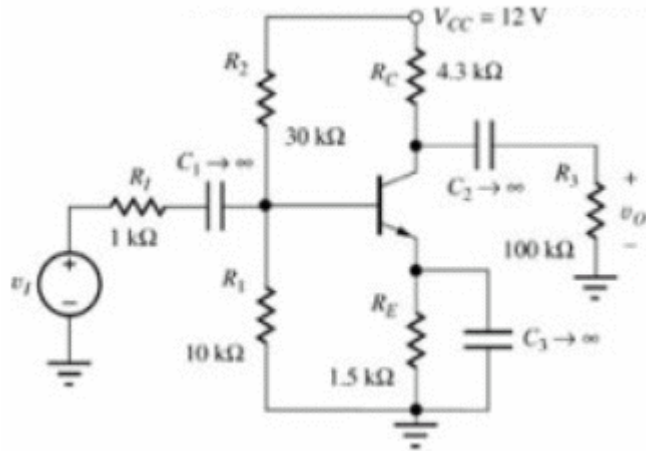

- Replace all ∞ capacitors by short circuits, ∞ inductors by open circuits
- Set all independent DC sources to 0, i.e., replace DC voltage sources by short circuits and DC current sources by open circuits
- Replace transistor by small-signal model
- Use small-signal AC equivalent to analyze AC characteristics of amplifier



Simplified AC Equivalent

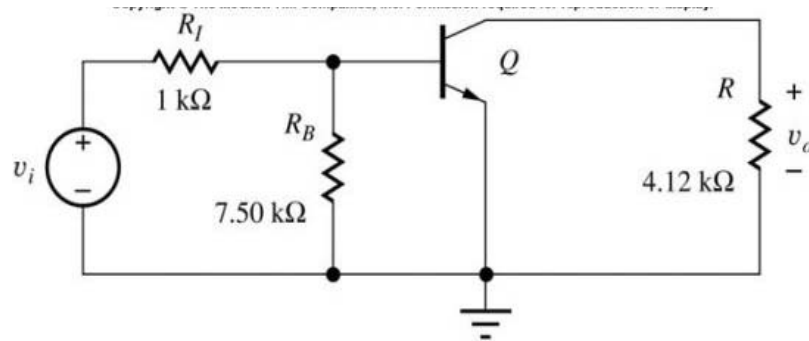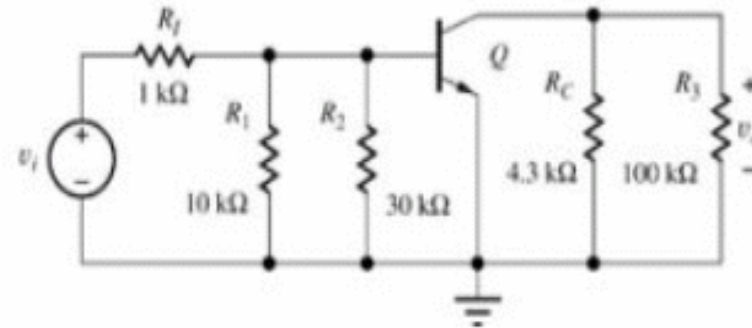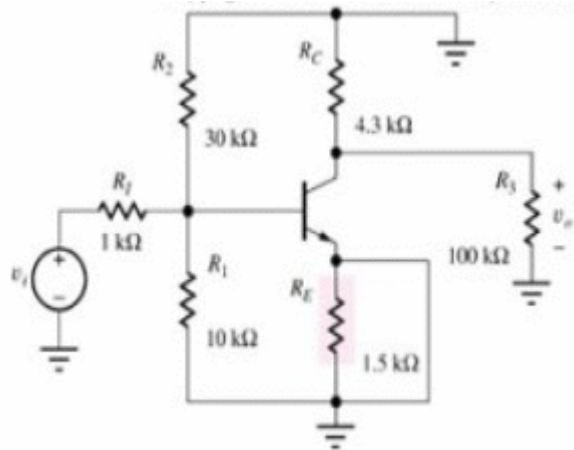

$$R_B = R_1 \parallel R_2 = 10 \text{ k}\Omega \parallel 30 \text{ k}\Omega$$

$$R = R_C \parallel R_3 = 4.3 \text{ k}\Omega \parallel 100 \text{ k}\Omega$$



Small Signal Performance Parameters

In AC analysis, we are interested to find


- Voltage gain
- Input resistance
- Output resistance

and sometimes

- Current gain
- Input signal range



Voltage Gain

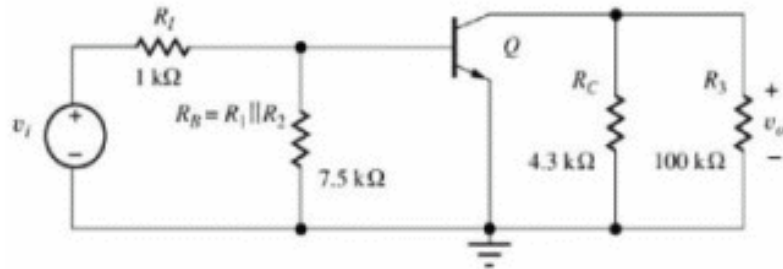


Terminal voltage gain


between base and collector is:

$$A_{vt} = \frac{v_c}{v_b} = \frac{v_o}{v_{be}} = -g_m R_L$$

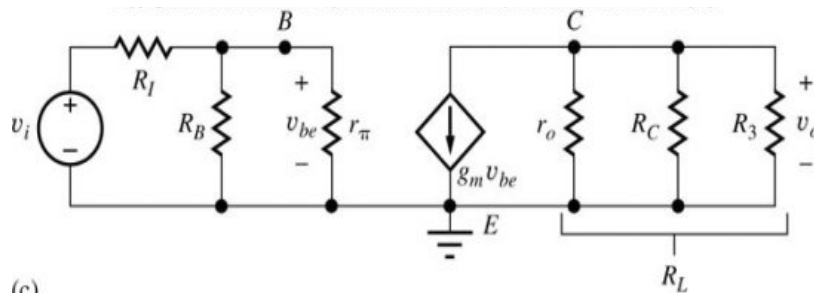Overall voltage gain from source v_i to output voltage across R_3 is:



(c)

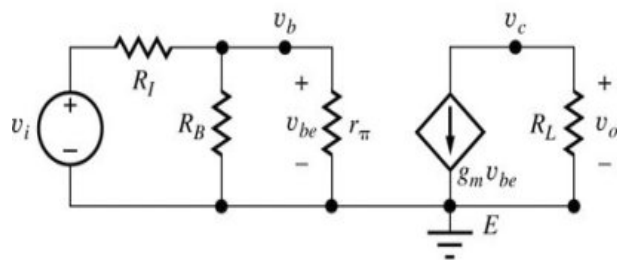



$$R_L = r_o \parallel R_C \parallel R_3$$

$$A_v = \frac{v_o}{v_i} = \left(\frac{v_o}{v_{be}} \right) \left(\frac{v_{be}}{v_i} \right) = A_{vt} \left(\frac{v_{be}}{v_i} \right)$$


$$\therefore A_v = -g_m R_L \left[\frac{R_B \parallel r_\pi}{R_I + (R_B \parallel r_\pi)} \right]$$



Input Resistance

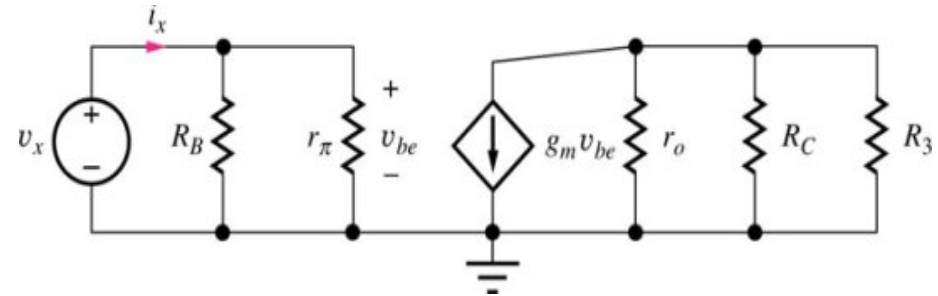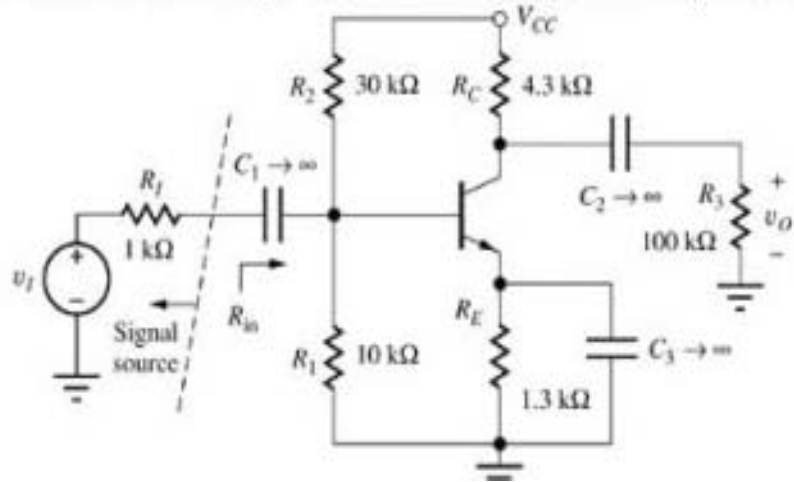

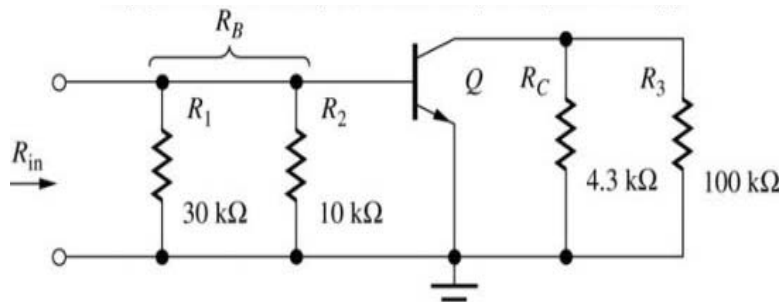- The total resistance looking into the amplifier at coupling capacitor C_1 represents total resistance of the amplifier presented to signal source





$$v_x = i_x (R_B \parallel r_\pi)$$


$$R_{in} = \frac{v_x}{i_x} = R_B \parallel r_\pi = R_1 \parallel R_2 \parallel r_\pi$$



Output Resistance

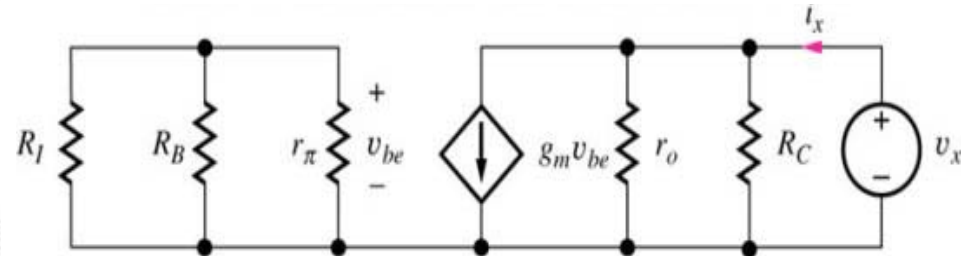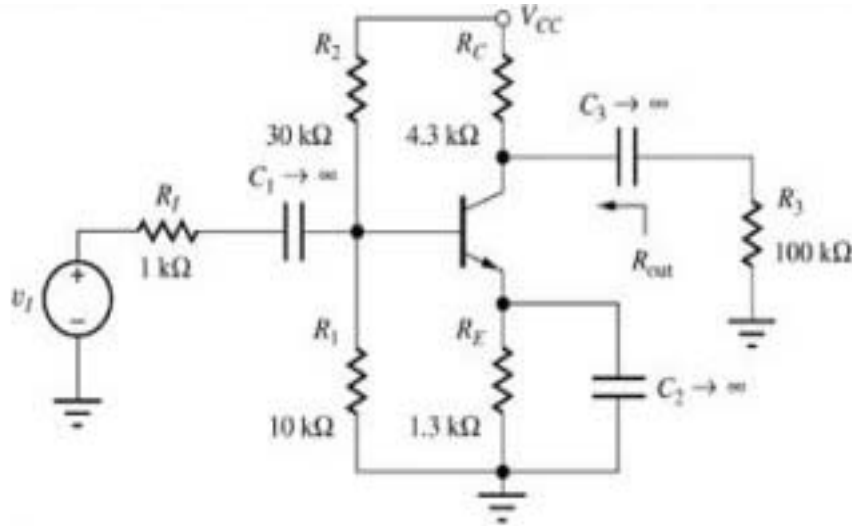

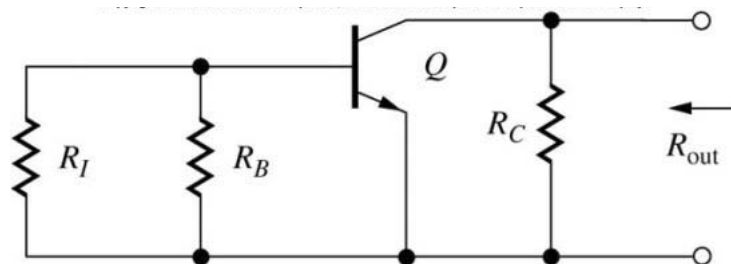- Output resistance is the total equivalent resistance looking into the output of the amplifier at coupling capacitor C_3




- To find R_{out} , input source is set to 0 and test source is applied at output

$$i_x = \frac{v_x}{R_C} + \frac{v_x}{r_o} + g_m v_{be} \quad \text{But } v_{be}=0.$$

$$\therefore R_{out} = \frac{v_x}{i_x} = R_C \parallel r_o \cong R_C \quad \text{As } r_o \gg R_C.$$




Example 1

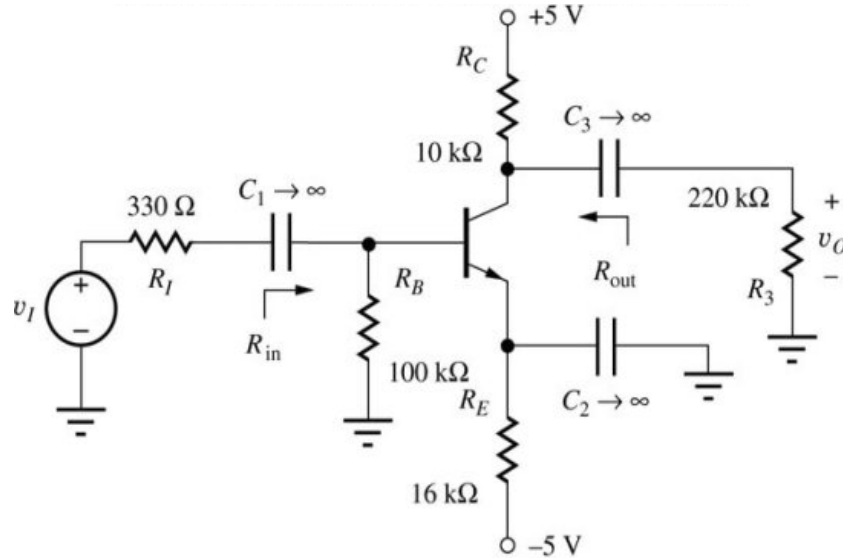

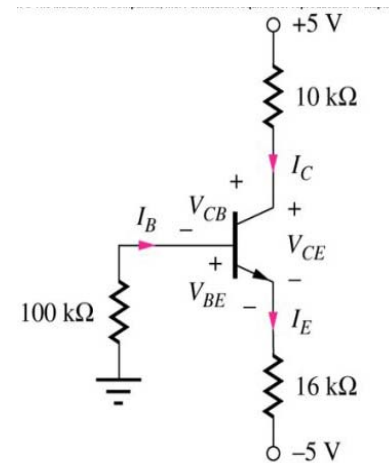- **Problem:** Find voltage gain, input and output resistances.
- **Given data:** $\beta = 65$, $V_A = 50$ V
- **Assumptions:** Active-region operation, $V_{BE} = 0.7$ V, small signal operating conditions.

Analysis: To find the Q-point, dc equivalent circuit is constructed.

$$10^5 I_B + V_{BE} + (\beta + 1) I_B (1.6 \times 10^4) = 5$$



$$\therefore I_B = 3.71 \mu\text{A}$$

$$I_C = 65 I_B = 241 \mu\text{A}$$

$$I_E = 66 I_B = 245 \mu\text{A}$$

$$5 - 10^4 I_C - V_{CE} - (1.6 \times 10^4) I_E - (-5) = 0$$


$$\therefore V_{CE} = 3.67 \text{ V}$$

Active region of operation is correct.



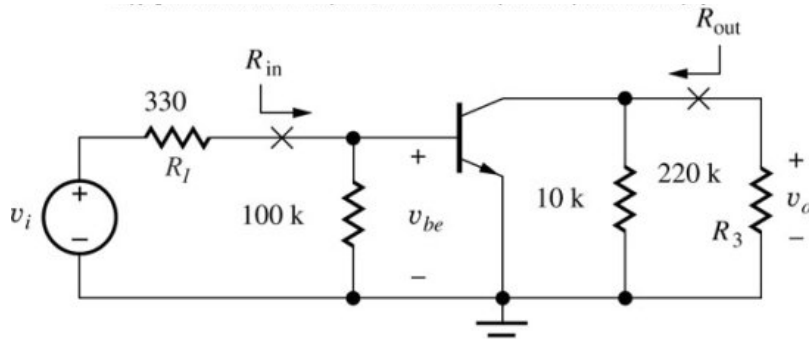Example 1 (Cont.)


Next we construct the ac equivalent and simplify it




$$g_m = \frac{I_C}{V_T} = 9.64 \times 10^{-3} \text{ S}$$

$$r_\pi = \frac{\beta V_T}{I_C} = 6.64 \text{ k}\Omega$$
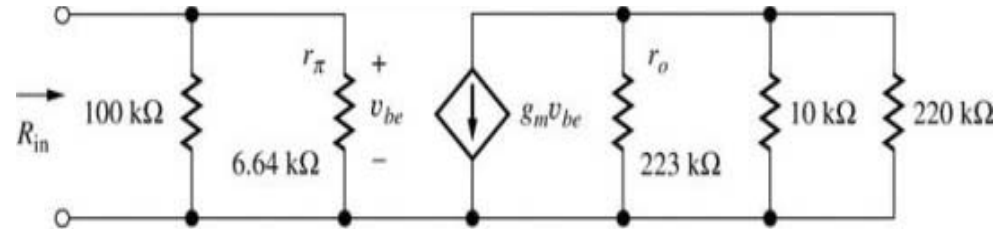
$$r_o = \frac{V_A + V_{CE}}{I_C} = 223 \text{ k}\Omega$$


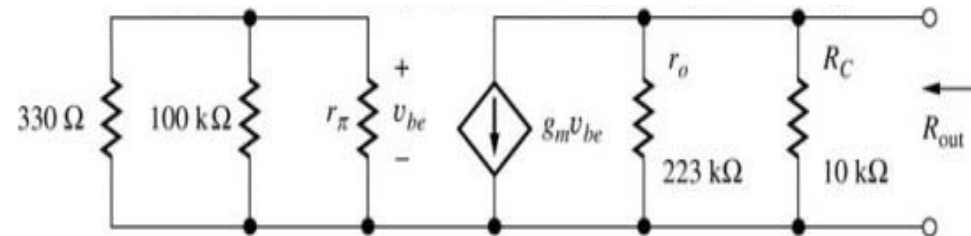
$$R_{in} = R_B \parallel r_\pi = 6.23 \text{ k}\Omega$$



$$R_{out} = R_C \parallel r_o = 9.57 \text{ k}\Omega$$

$$A_v = \frac{v_o}{v_i} = -g_m (R_{out} \parallel R_3) \left[\frac{R_{in}}{R_I + R_{in}} \right] = -84.0$$




Topics to cover ...


- Family of single-stage BJT amplifiers
- Small signal analysis
 - Common-Emitter Amplifier
- **Common-Emitter Amplifier with Emitter R**
- Common-Base Amplifier



Common-Emitter Amplifier with Emitter R

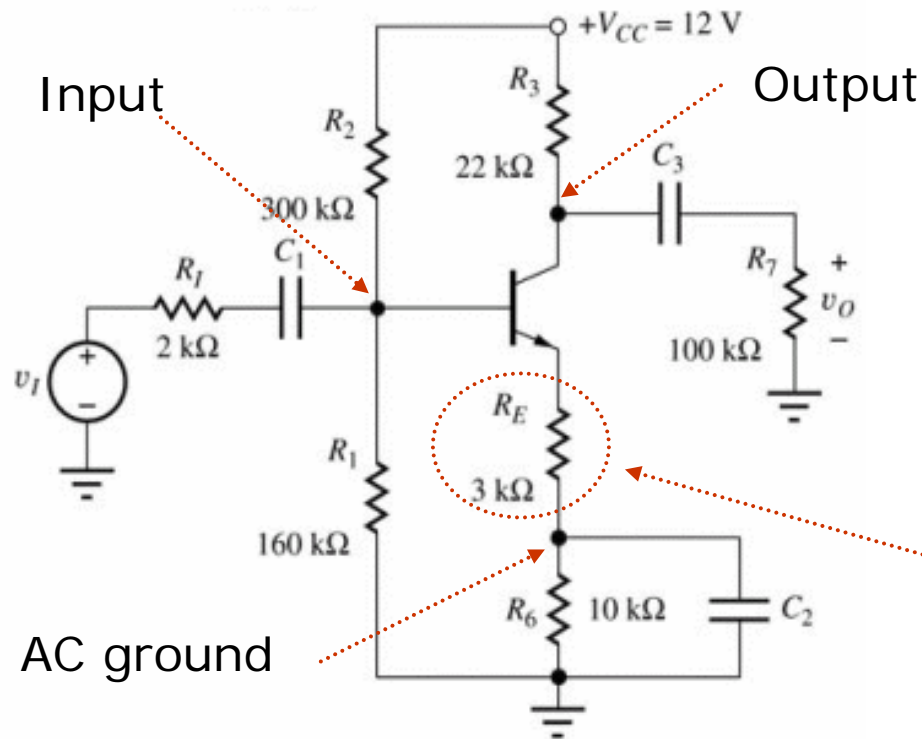

AC equivalent:

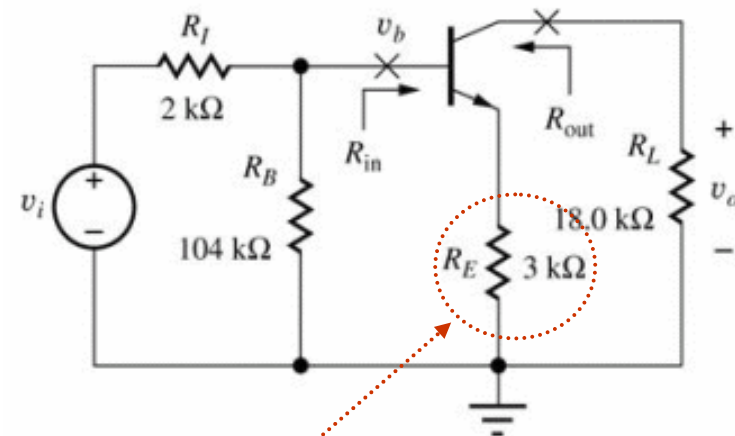


A resistor exists at the emitter of the ac equivalent circuit

Also called ***emitter degenerated*** CE amplifier

R_E provides negative feedback




Negative Feedback due to R_E

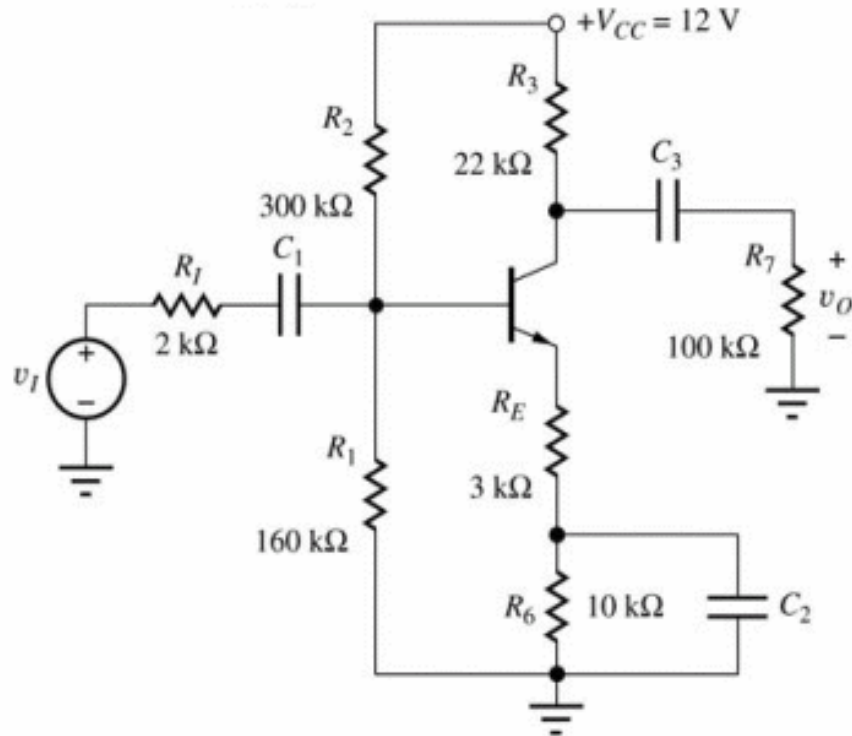

- Assume $i_C \uparrow$ for any reason
 - $i_E (=i_C/\alpha) \uparrow$
 - $V_E \uparrow$
 - $V_{BE} \downarrow$
 - $i_C \downarrow$: counter act the original change
-
- More discussion on negative feedback later in the course



Overall Voltage Gain

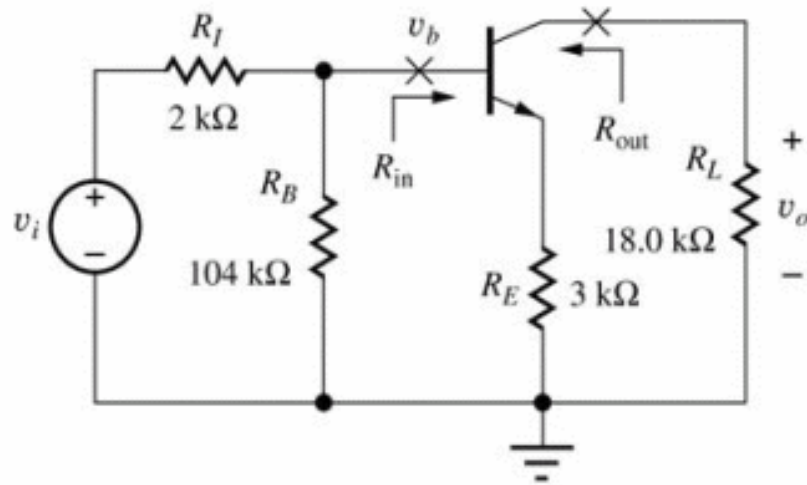

Overall voltage gain from v_i to v_o can be expressed as:

$$A_v \equiv \frac{v_o}{v_i} = \left(\frac{v_o}{v_b} \right) \left(\frac{v_b}{v_i} \right)$$

Define **terminal voltage gain** as:

$$A_{vt} \equiv \frac{v_o}{v_b}$$

And it can be observed that:

$$\frac{v_b}{v_i} = \frac{R_B \parallel R_{in}}{R_I + (R_B \parallel R_{in})}$$


Thus, the task breaks down into two steps:

- Find the terminal voltage gain
- Find the input resistance R_{in} .



Terminal Voltage Gain

Use hybrid- π model (neglecting r_o):

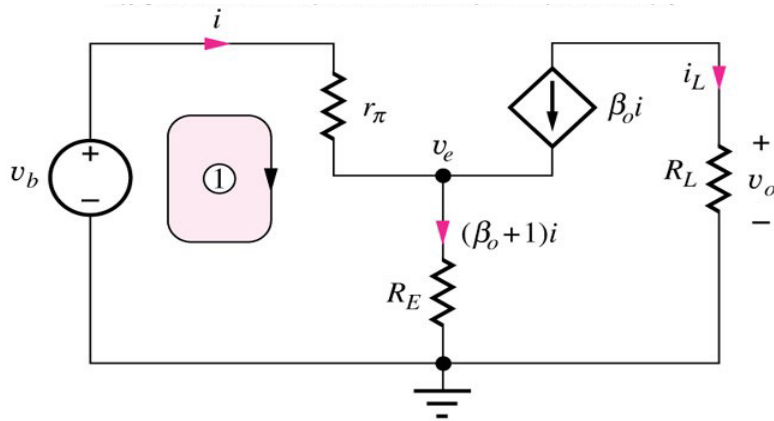

Using $r_{\pi}g_m = \beta$, we have

$$A_{vt} = -\frac{g_m r_{\pi} R_L}{r_{\pi} + (g_m r_{\pi} + 1)R_E} \cong -\frac{g_m R_L}{1 + g_m R_E}$$

for $g_m r_{\pi} = \beta \gg 1$

$$\begin{aligned} v_b &= i r_{\pi} + (\beta + 1) i R_E \\ &= i (r_{\pi} + (\beta + 1) R_E) \end{aligned}$$

$$v_o = -\beta i R_L$$

$$A_{vt} \equiv \frac{v_o}{v_b} = -\frac{\beta R_L}{r_{\pi} + (\beta + 1) R_E}$$

Effect of R_E :


- For $R_E = 0$, $A_{vt} \cong -g_m R_L$
– Upper limit of A_{vt}
- For $g_m R_E \gg 1$, $A_{vt} = -R_L / R_E$
– A_{vt} becomes less dependent on g_m which varies widely
- Increasing R_E decreases voltage gain!



Input Resistance

To find $R_{in} \rightarrow$ to find V_b/i :

$$v_b = i(r_\pi + (\beta + 1)R_E)$$

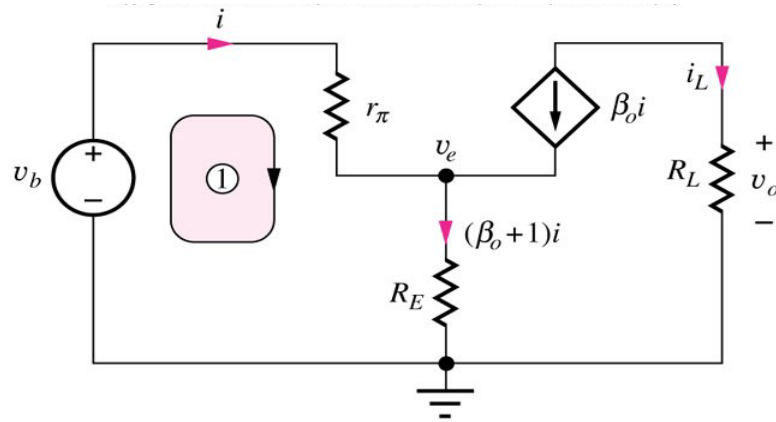

$$\begin{aligned} R_{in} &= \frac{v_b}{i} = r_\pi + (\beta + 1)R_E \\ &= r_\pi + (g_m r_\pi + 1)R_E \\ &\cong r_\pi (1 + g_m R_E) \end{aligned}$$

for $g_m r_\pi = \beta \gg 1$

- Increasing R_E increases input resistance!



Output Resistance

To find R_{out} :

- Set v_i to zero
- Apply a test source at output
- $R_{out} = v_x / i_x$

$$v_e = (\beta + 1)iR_E$$


KVL at left mesh:

$$i(R_{th} + r_\pi) + v_e = 0$$


$$\frac{v_e}{(\beta + 1)R_E} (R_{th} + r_\pi) + v_e = 0$$

$$\Rightarrow v_e = 0$$
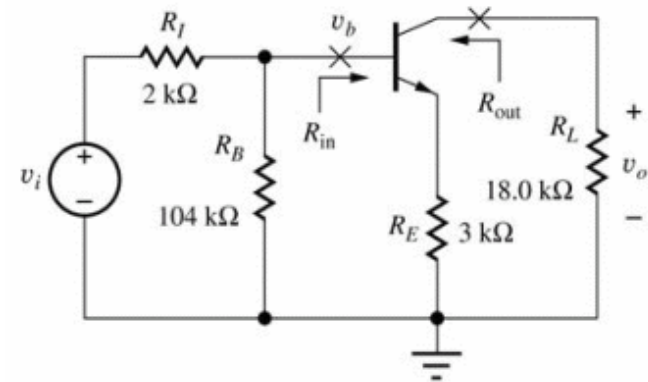
$$\therefore i = 0 \Rightarrow i_x = \beta i = 0 \quad \therefore R_{out} = \frac{v_x}{i_x} = \infty$$




$$R_{th} = R_I // R_B$$

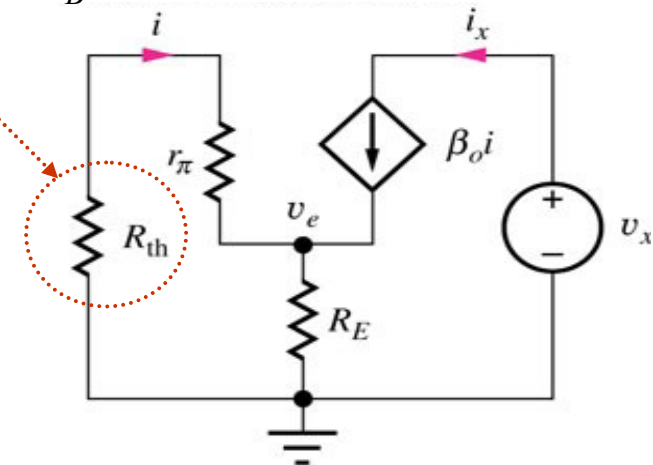

Output Resistance

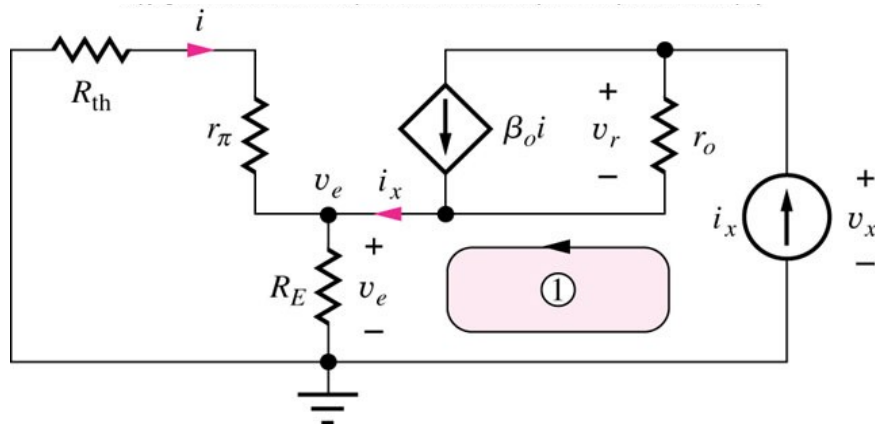Now, we also include r_o in our analysis:



KVL along loop 1:

$$v_x = v_r + v_e = (i_x - \beta i)r_o + v_e$$

Voltage at E:

$$v_e = i_x \left(\left(R_{th} + r_{\pi} \right) // R_E \right)$$

Current division at Emitter:

$$i = -i_x \frac{R_E}{R_E + R_{th} + r_{\pi}}$$

Put 2nd and 3rd equations into 1st equation:

$$\therefore v_x = r_o \left(i_x + \beta i_x \frac{R_E}{R_E + R_{th} + r_{\pi}} \right) + i_x \left(\left(R_{th} + r_{\pi} \right) // R_E \right)$$

$$\therefore R_{out} \equiv \frac{v_x}{i_x} \cong r_o \left(1 + \frac{\beta R_E}{R_E + R_{th} + r_{\pi}} \right) \quad \text{for large value of } r_o$$



Output Resistance

$$R_{\text{out}} \cong r_o \left(1 + \frac{\beta R_E}{R_E + R_{th} + r_\pi} \right)$$

Assuming $(r_\pi + R_E) \gg R_{th}$ and $r_o \gg R_E$, with $\beta = g_m r_\pi$


$$R_{\text{out}} \cong r_o \left(1 + \frac{g_m r_\pi R_E}{R_E + r_\pi} \right) = r_o (1 + g_m (r_\pi \parallel R_E))$$

Effect of R_E :


- For $R_E = 0$, $R_{\text{out}} = r_o$
- For $R_E = \infty$, upper limit of R_{out} is obtained:

$$R_{\text{out}} = (\beta + 1)r_o$$

- Increasing R_E increases R_{out} !

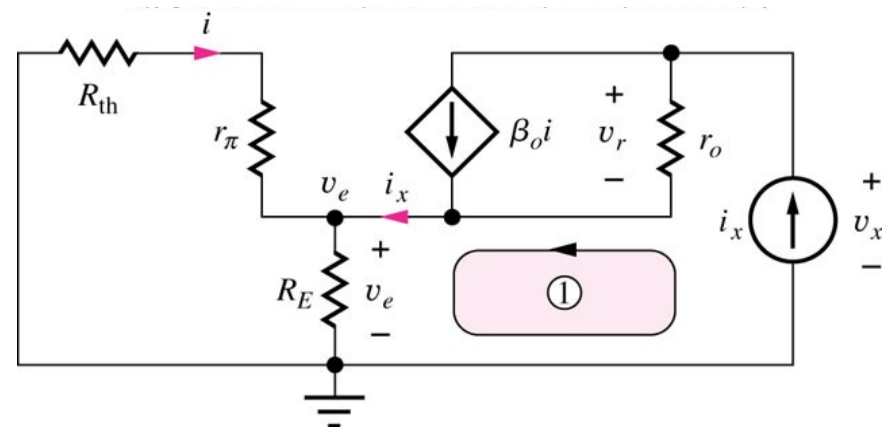

Current Gain

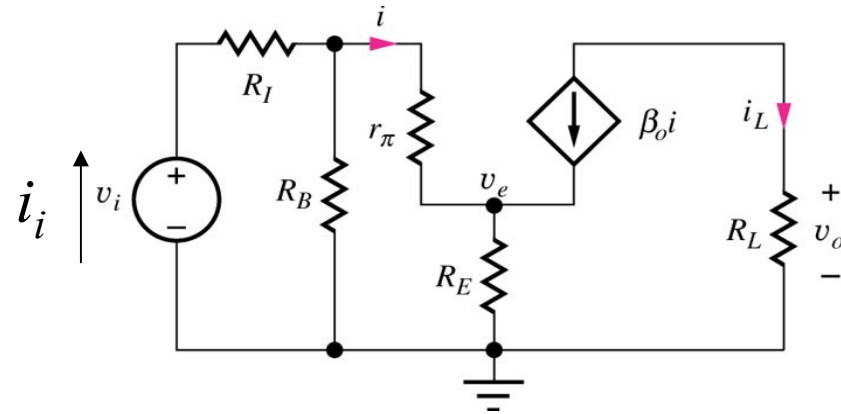

- Terminal current gain: $A_{it} \equiv \frac{i_L}{i} = -\beta$

- Overall current gain: $A_i \equiv \frac{i_L}{i_s} = \frac{i_L}{i} \frac{i}{i_s} = A_{it} \frac{R_B}{R_B + R_{in}}$



Input Signal Range


Remember, in deriving the linear small signal model, we assumed $v_{be} \ll V_T$:

$$\begin{aligned} i_C &= I_C e^{v_{be}/V_T} \cong I_C (1 + v_{be}/V_T) \\ &= \underbrace{I_C}_{DC} + \underbrace{\frac{I_C}{V_T} v_{be}}_{AC} \end{aligned}$$

Typically, v_{be} is required to be less than 5mV!



Input Signal Range

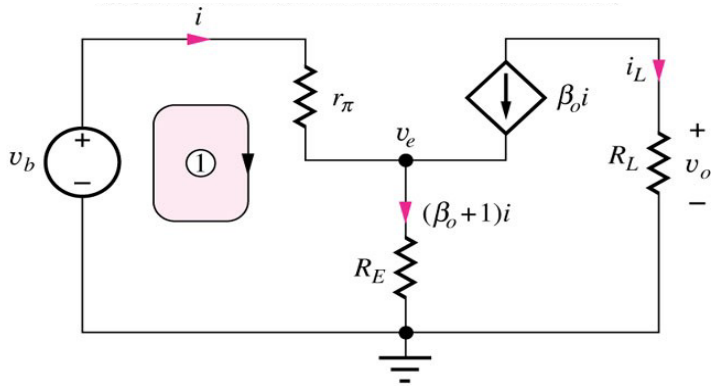

$$v_b = i(r_\pi + (\beta + 1)R_E)$$

$$v_{be} = ir_\pi = r_\pi \frac{v_b}{r_\pi + (\beta + 1)R_E} = \frac{v_b}{1 + g_m R_E + R_E / r_\pi}$$

$$|v_b| \leq 0.005 \left(1 + g_m \left(R_E + \frac{R_E}{\beta} \right) \right) \approx 0.005(1 + g_m R_E) \text{ V}$$

If $g_m R_E \gg 1$, v_b can be increased beyond 5 mV limit.

- Condition for $g_m R_E \gg 1$:
$$g_m R_E = \frac{I_C R_E}{V_T} \approx \frac{I_E R_E}{V_T} \gg 1$$

$$\therefore I_E R_E \gg V_T = 0.025 \text{ V}$$

- Increasing R_E increases input signal range!



Summary of Emitter Degenerated Common-Emitter Amplifier

- *Terminal voltage gain*: Inverting and Large $-\frac{g_m R_L}{1+g_m R_E}$
- *Overall voltage gain*: Inverting and Large $-\frac{g_m R_L}{1+g_m R_E} \left[\frac{R_B // R_{in}}{R_I + R_B // R_{in}} \right]$
- *Input resistance*: Large $r_\pi(1+g_m R_E)$
- *Output resistance*: Large $r_o \left(1+g_m(r_\pi \parallel R_E) \right)$
- *Terminal Current gain*: Large $-\beta$
- *Effects of the resistor at Emitter*:
 - Voltage gain decreased, but more stabilized (less sensitive to g_m)
 - Input signal range increased
 - Input and output resistance increased




Topics to cover ...


- Family of single-stage BJT amplifiers
- Small signal analysis
 - Common-Emitter Amplifier
- Common-Emitter Amplifier with Emitter R
- **Common-Base Amplifier**



Common-Base Circuits

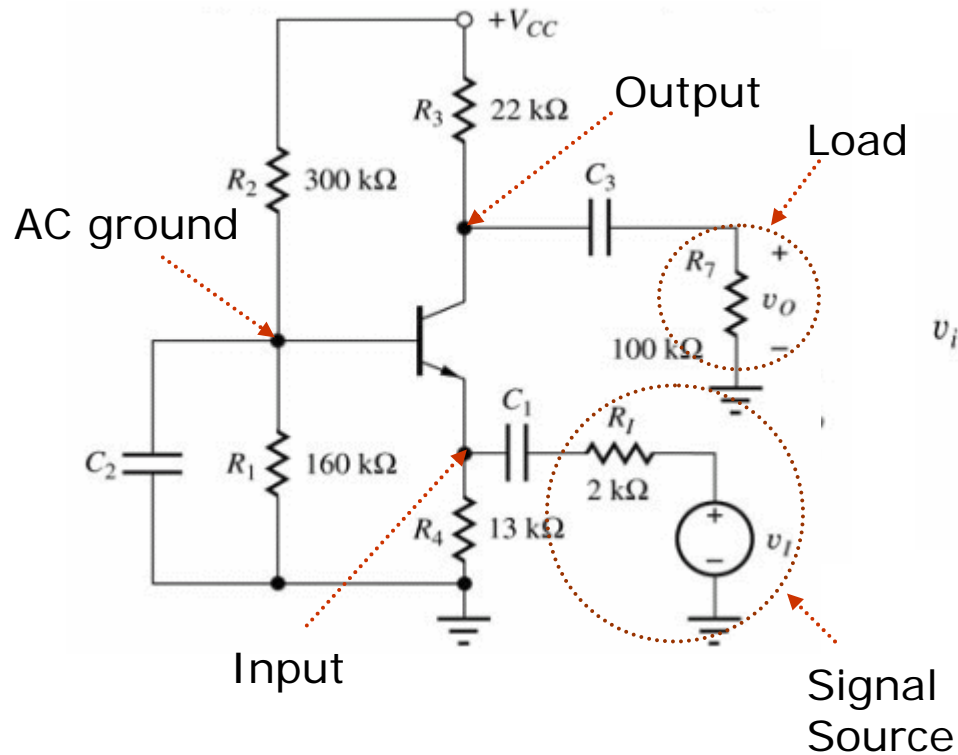


AC/Small-signal equivalent:

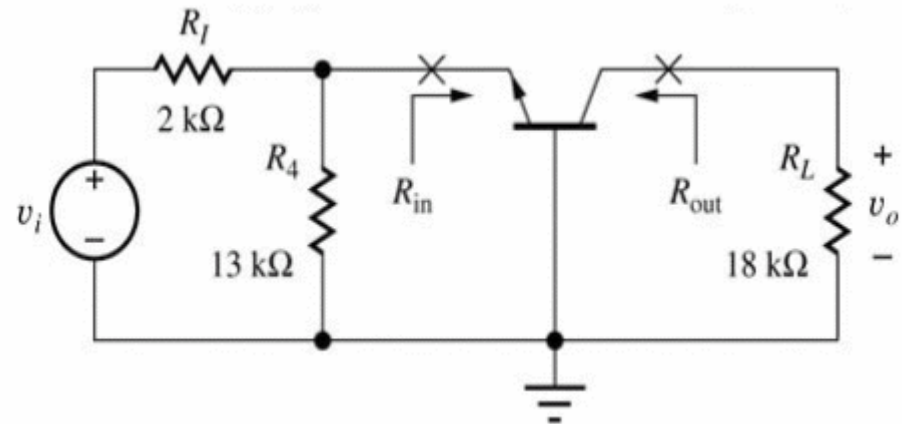

$$R_L = R_3 \parallel R_7$$




Terminal Voltage Gain

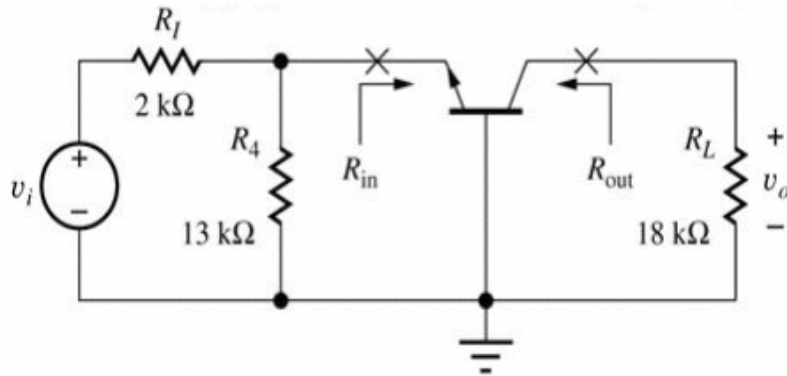



$$A_{vt}^{CB} \equiv \frac{v_o}{v_e} = +g_m R_L$$

Apply test source to input (E)
And use BJT small signal model:

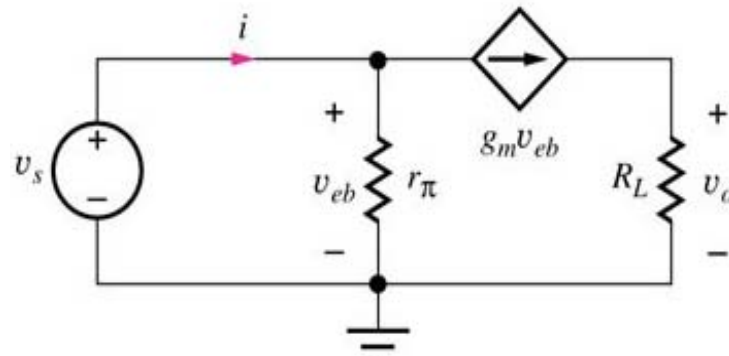- Non-inverting!
- Magnitude same as the CE amplifier with $R_E=0$.



Input Resistance

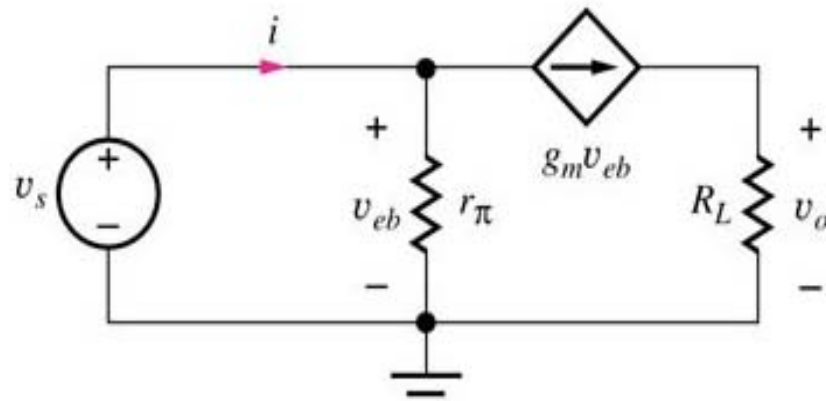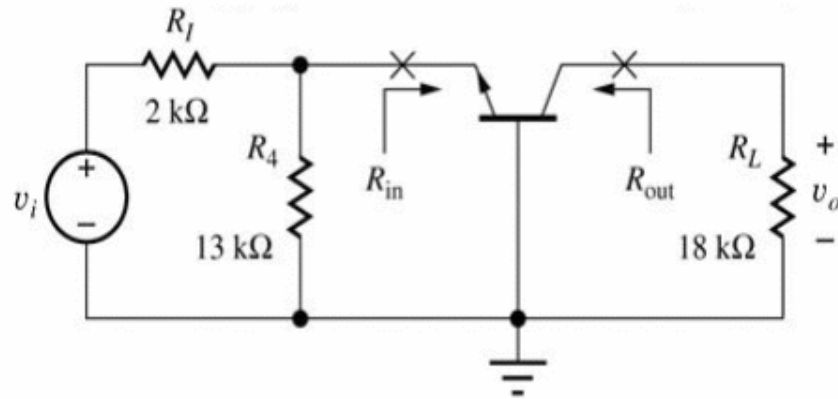

KCL at emitter:

$$i = \frac{v_e}{r_\pi} + g_m v_e$$


$$R_{in}^{CB} = \frac{v_e}{i} = \frac{r_\pi}{r_\pi g_m + 1} = r_\pi \parallel \left(\frac{1}{g_m} \right) \cong \frac{1}{g_m}$$

- R_{in} is small (as g_m is usually large)!

$$(g_m = I_C / V_T)$$



Overall Voltage Gain

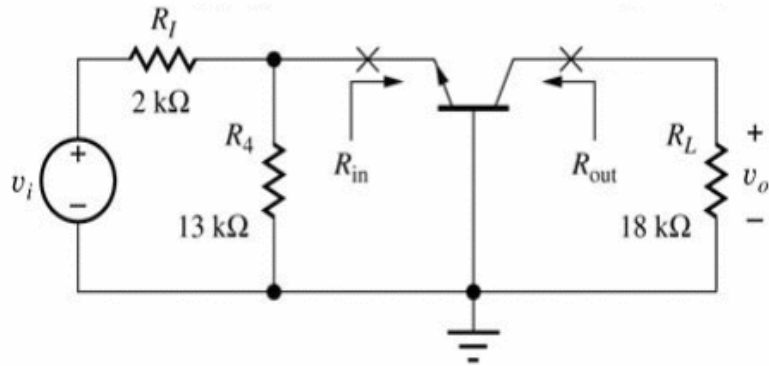

Overall voltage gain is

$$\begin{aligned}
 A_v^{CB} &= \frac{v_o}{v_i} = \left(\frac{v_o}{v_e} \right) \left(\frac{v_e}{v_i} \right) = A_{vt} \left[\frac{R_4 \parallel R_{in}}{R_I + (R_4 \parallel R_{in})} \right] \\
 &= \frac{g_m R_L}{1 + g_m (R_4 \parallel R_I)} \left(\frac{R_4}{R_I + R_4} \right) \\
 &\approx \frac{g_m R_L}{1 + g_m R_I} \quad \text{for } R_4 \gg R_I
 \end{aligned}$$

For $g_m R_I \ll 1$,

$$A_v^{CB} = +g_m R_L$$

This is the upper bound.

For $g_m R_I \gg 1$,

$$A_v^{CB} = +\frac{R_L}{R_I}$$

- For large voltage gain, a very small R_I is required!
- Not a good candidate for voltage amplifier



Example


- **Problem:** Find overall voltage gain.
- **Given data:** $\beta=100$, Q-point values: $I_C=245\mu\text{A}$, $V_{CE}=3.64\text{V}$, $g_m=9.8\text{mS}$, $r_\pi=10.2\text{k}\Omega$, $r_o=219\text{k}\Omega$.
- **Assumptions:** Small-signal operating conditions.
- **Analysis:**

$$R_{in}^{CB} \cong 1/g_m = 102\Omega$$


$$R_L = R_3 \parallel R_7 = 18\text{k}\Omega$$

$$A_{vt}^{CB} = +g_m R_L = 176$$
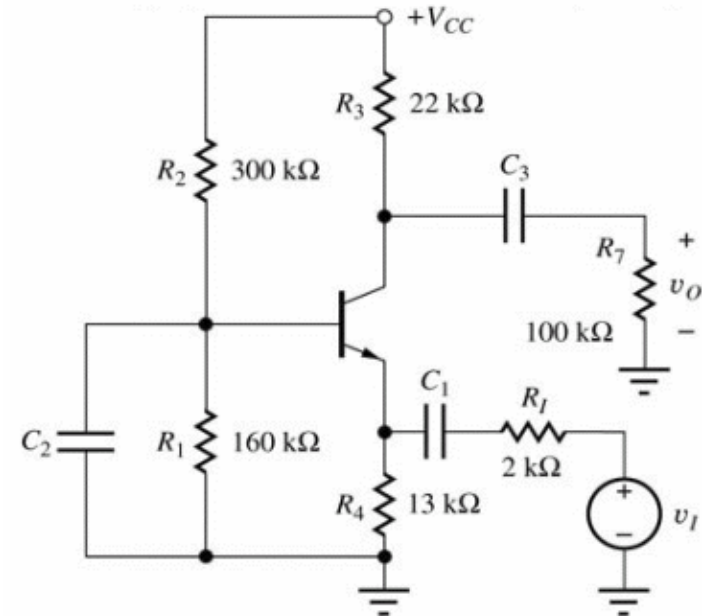
$$A_v^{CB} = \frac{A_{vt}^{CB}}{1 + g_m (R_I \parallel R_4)} \left(\frac{R_4}{R_I + R_4} \right) = +8.59$$



Input Signal Range

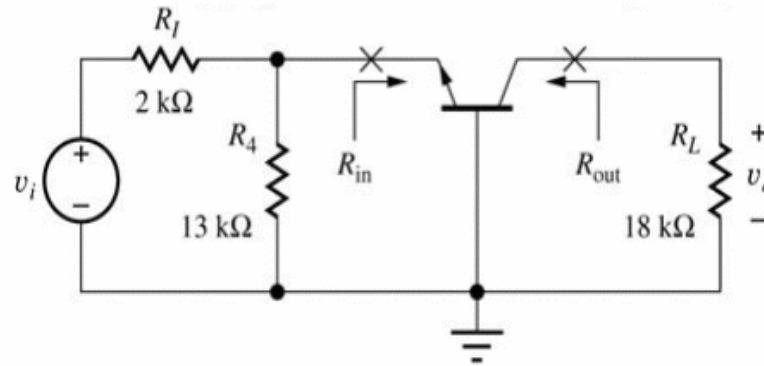

$$v_{eb} = v_i \frac{R_4 // R_{in}}{R_I + R_4 // R_{in}} = \frac{v_i}{1 + g_m (R_I // R_4)} \left(\frac{R_4}{R_I + R_4} \right)$$



$$v_i \cong v_{eb} (1 + g_m R_I) \quad \text{for } R_4 \gg R_I.$$

For small-signal operation, $|v_b| \leq 0.005(1 + g_m R_I) \text{V}$

Relative size of g_m and R_I determine signal-handling limit.



Output Resistance

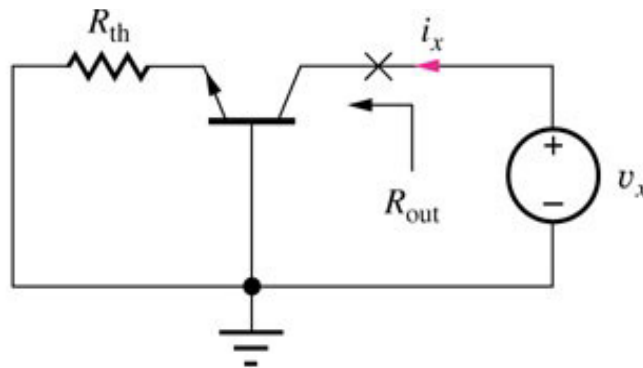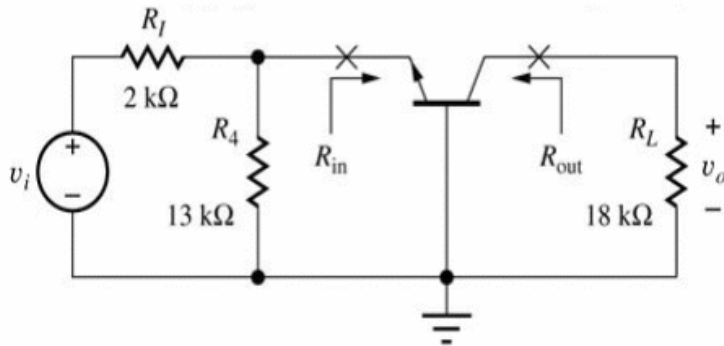


- R_{out} here is equivalent to the R_{out} of CE amplifier with $R_E = R_{th}$ and resistance at base equal to zero.

$$\therefore R_{out}^{CB} = r_o \left(1 + \frac{\beta R_{th}}{R_{th} + r_{\pi}} \right)$$

Using $\beta = g_m r_{\pi}$

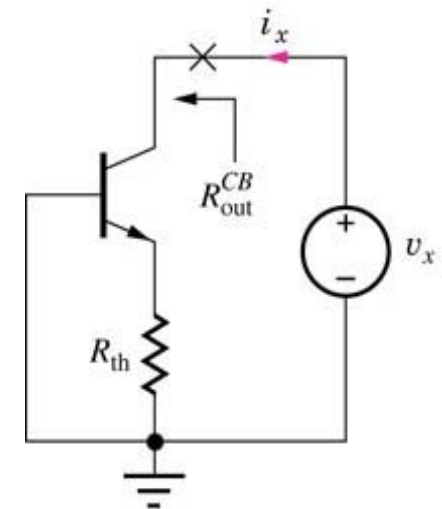
$$R_{out}^{CB} \cong r_o \left(1 + g_m (r_{\pi} // R_{th}) \right)$$



- R_{out} is large.



Current Gain

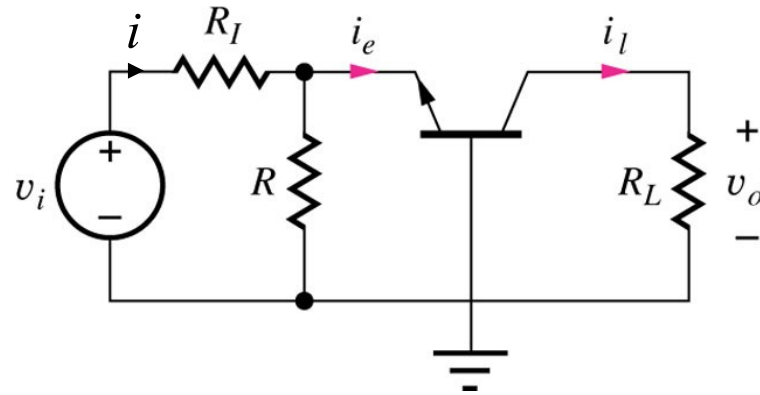

- Terminal current gain: $A_{it}^{CB} = \frac{i_l}{i_e} = \alpha \cong +1$
- Current gain from source to load:

$$A_i^{CB} = \frac{i_l}{i} = \left(\frac{i_l}{i_e} \right) \left(\frac{i_e}{i} \right) = A_{it} \frac{R}{R_{in} + R} \cong A_{it} = 1 \text{ for } R \gg R_{in}$$




Summary of Common Base Amplifier

- *Terminal voltage gain*: Non-inverting and Large
- *Input resistance*: Low
- *Output resistance*: High
- *Current gain*: close to Unity
- *Input range*: determined by $g_m R_{th}$

- Excellent for use as a current buffer




Current Buffer

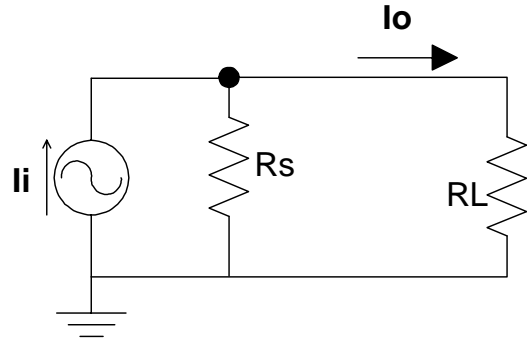

- Without a buffer:

$$I_o = \frac{R_s}{R_s + R_L} I_i \ll I_i \text{ for } R_L \gg R_s$$

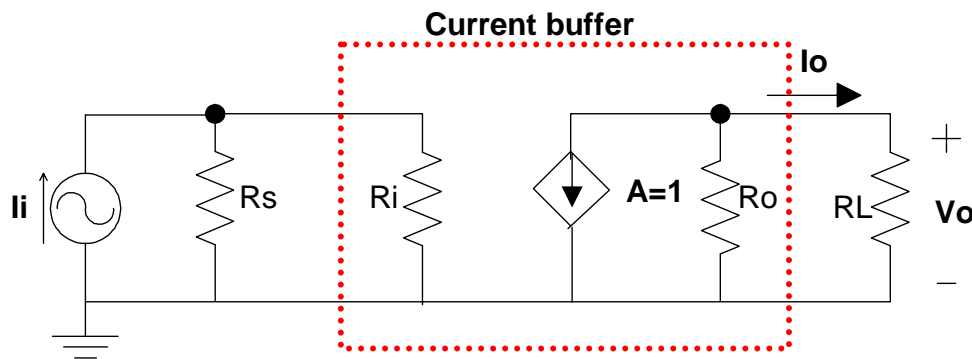Only a small portion of source current is delivered to load!



- With a buffer:

$$I_o = \left(\frac{R_s}{R_s + R_i} I_i \right) A \frac{R_o}{R_L + R_o}$$

$$\cong A I_i = I_i \text{ for } R_i \ll R_s \text{ and } R_o \gg R_L$$

- Requirement of a current buffer:
 - Low input resistance
 - High output resistance
 - Unity current gain

