

First Course on Power Systems

Module 5: Transformers in Power Systems


By
Ned Mohan
Professor of ECE
University of Minnesota

Reference Textbook:
First Course on Power Systems by Ned Mohan,
www.mnpere.com

Module 5: Transformers in Power Systems

Chapter 6 TRANSFORMERS IN POWER SYSTEMS	6-1
6-1 INTRODUCTION	6-1
6-2 BASIC PRINCIPLES OF TRANSFORMER OPERATION	6-1
6-3 SIMPLIFIED TRANSFORMER MODEL	6-7
6-4 PER-UNIT REPRESENTATION	6-8
6-5 TRANSFORMER EFFICIENCIES AND LEAKAGE REACTANCES	6-10
6-6 REGULATION IN TRANSFORMERS	6-11
6-7 AUTO-TRANSFORMERS	6-11
6-8 PHASE-SHIFT INTRODUCED BY TRANSFORMERS	6-13
6-9 THREE-WINDING TRANSFORMERS	6-14
6-10 THREE-PHASE TRANSFORMERS	6-15
6-11 REPRESENTING TRANSFORMERS WITH OFF-NOMINAL TURNS RATIOS, TAPS AND PHASE-SHIFT	6-16
REFERENCES	6-18
PROBLEMS	6-18

Need for transformers?

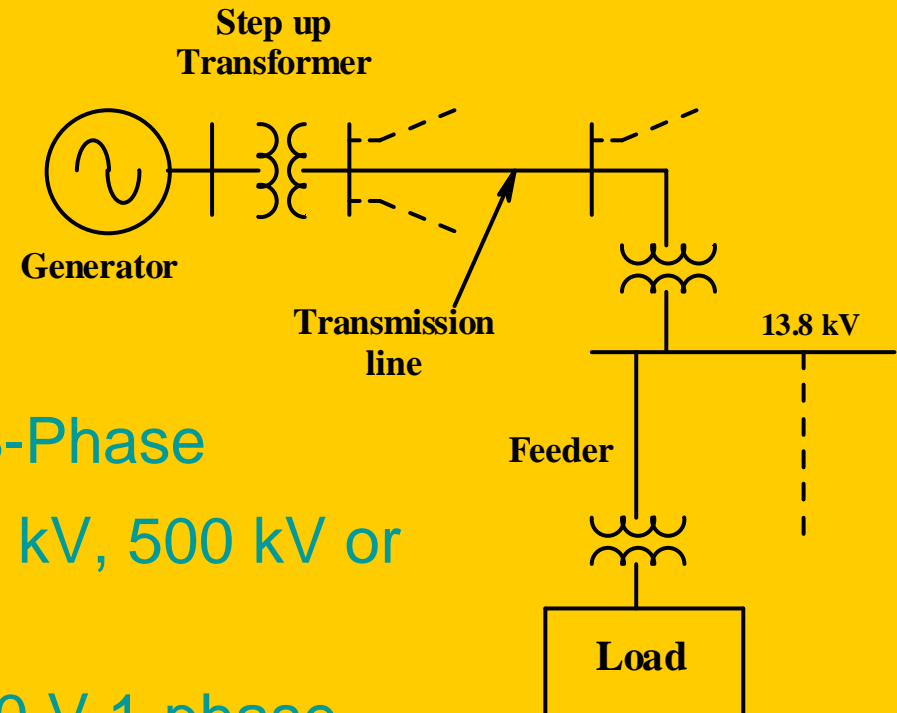

- Generation at 20-kV Level, 3-Phase
- Transmission at 230 kV, 345 kV, 500 kV or 765 kV
- Residential Usage at 120/240 V 1-phase
- Typically, voltage gets transformed 5 times
- Electrical Isolation for safety

Transformer Principle: Generation of Flux


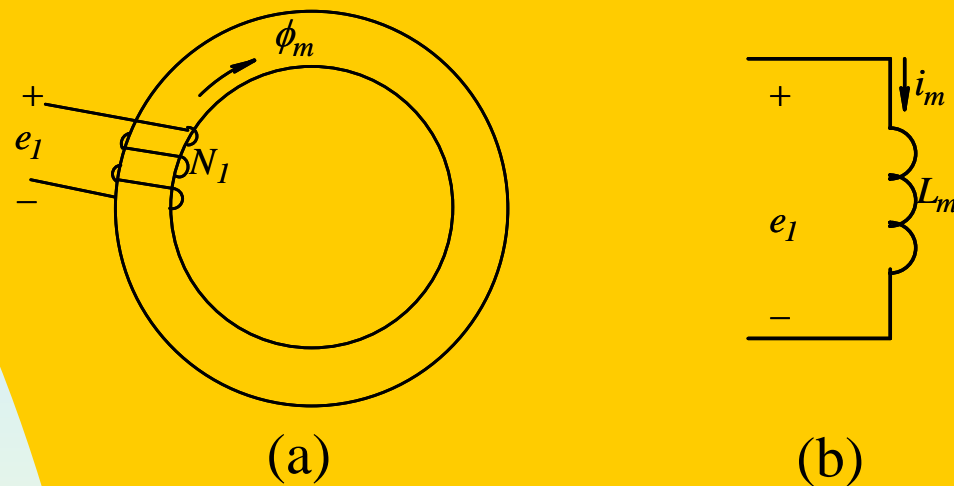
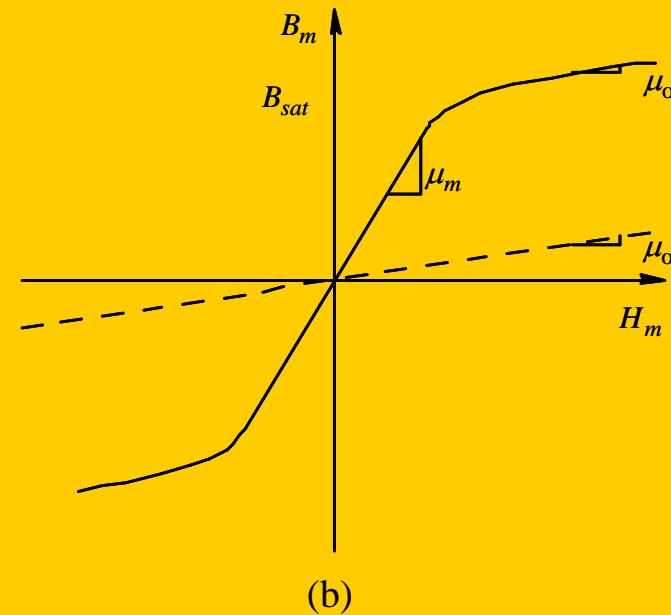


Fig. 6-1 Principle of transformers, beginning with just one coil.

$$e_1(t) = N_1 \frac{d\phi_m}{dt}$$



$$\phi_m(t) = \frac{1}{N_1} \int_0^t e_1(\tau) \cdot d\tau$$

Transformer Exciting Current:

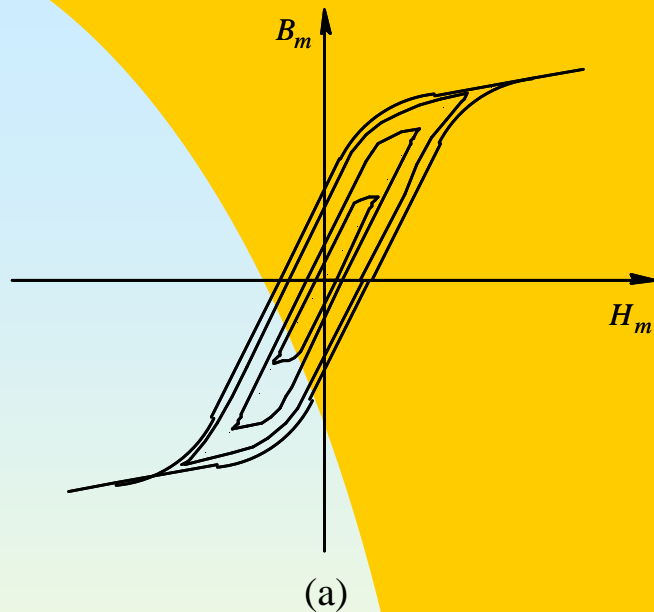


- Core of Ferromagnetic Material such as Silicone Steel
- Hysteresis Loss
- Saturation beyond the “knee”; incremental permeability of air
- Operated at 1.6 T to 1.8 T

Magnetizing Current:

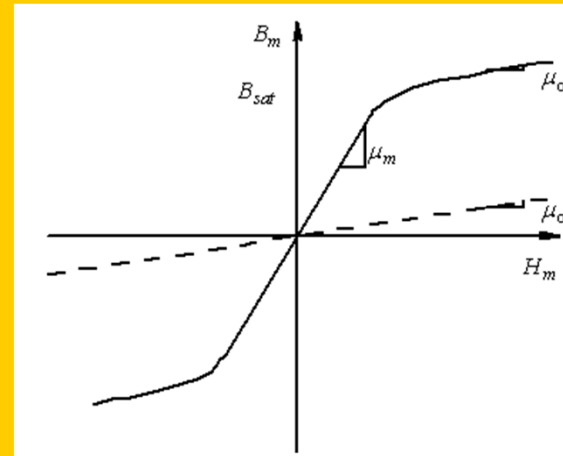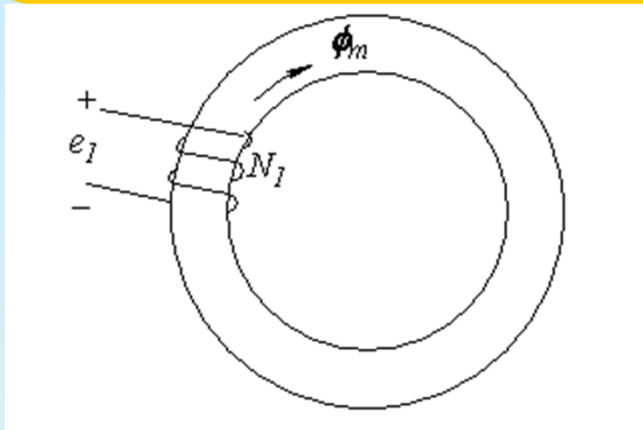

$$L_m = \frac{\lambda_m}{i_m}$$

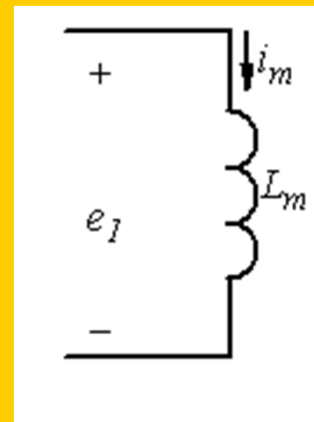

Magnetizing Flux

$$e_1 = \sqrt{2}E_1(\text{rms}) \cos \omega t$$

$$\phi_m(t) = \frac{1}{N_1} \int_0^t e_1(\tau) \cdot d\tau$$


$$\phi_m = \hat{\phi}_m \sin \omega t$$

$$\sqrt{2}E_1(\text{rms}) = (2\pi f) N_1 \hat{\phi}_m$$


$$\hat{\phi}_m \approx \frac{E_1(\text{rms})}{4.44 N_1 f}$$

- Exceeding the rated voltage causes saturation
- Modern Power Transformer: Magnetizing Current < 0.2% rated

Voltage Transformation

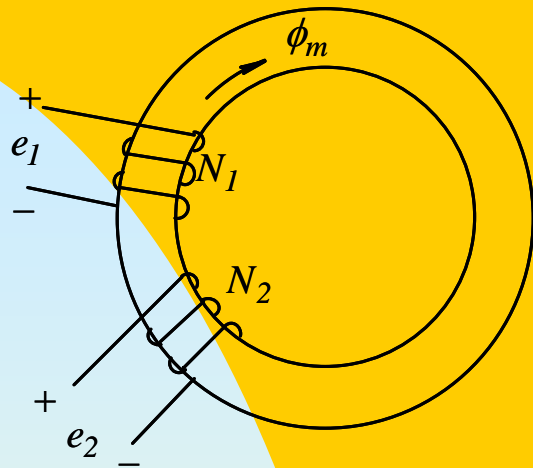

(a)

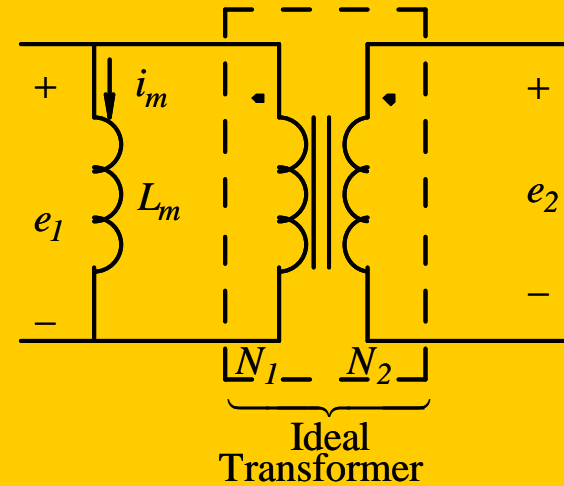

(b)

$$e_1(t) = N_1 \frac{d\phi_m}{dt}$$


$$e_2(t) = N_2 \frac{d\phi_m}{dt}$$

$$\frac{e_1(t)}{N_1} = \frac{e_2(t)}{N_2}$$


$$\frac{e_1(t)}{e_2(t)} = \frac{N_1}{N_2}$$

$$\frac{\bar{E}_1}{\bar{E}_2} = \frac{N_1}{N_2}$$

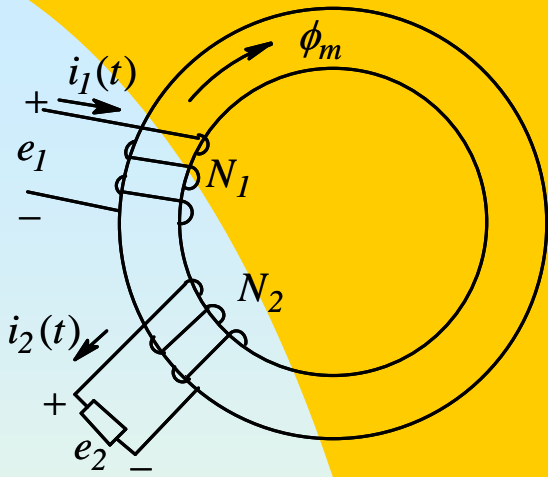Transformer with Load Connected to the Secondary



(a)

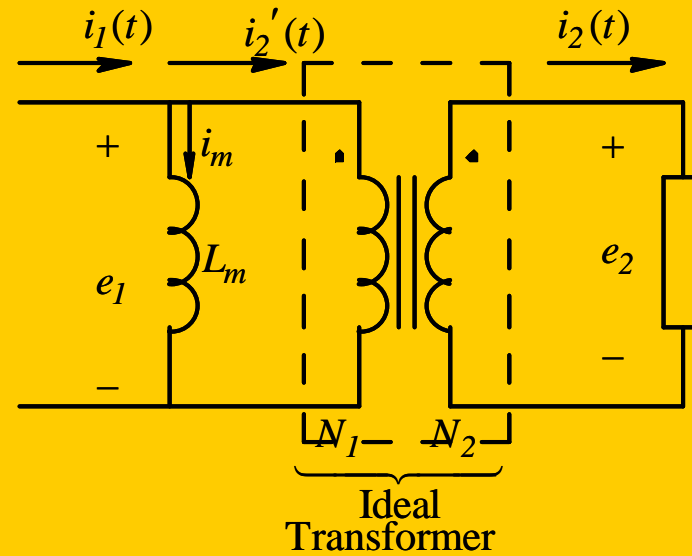

(b)

$$N_1 i_2' = N_2 i_2$$

$$\frac{i_2'(t)}{i_2(t)} = \frac{N_2}{N_1} \quad \frac{\bar{I}_2'}{\bar{I}_2} = \frac{N_2}{N_1}$$

$$i_1(t) = i_m(t) + i_2'(t)$$

$$\bar{I}_1 = \bar{I}_m + \bar{I}_2'$$

Transformer Equivalent Circuit:

