

Chapter 4

Ohm's Law, Power, and Energy

Ohm's Law

- Current in a resistive circuit
 - Directly proportional to its applied voltage
 - Inversely proportional to its resistance

$$I = \frac{E}{R}$$

Ohm's Law

- For a fixed resistance
 - Doubling voltage doubles the current
- For a fixed voltage
 - Doubling resistance halves the current

3

Ohm's Law

- Also expressed as $E = IR$ and $R = E/I$
- Express all quantities in base units of volts, ohms, and amps or utilize the relationship between prefixes

4

Ohm's Law in Graphical Form

- Linear relationship between current and voltage
- $y = mx$
 - y is the current
 - x is the voltage
 - m is the slope


5

Ohm's Law in Graphical Form

- Slope (m) determined by resistor conductance

6

Ohm's Law in Graphical Form

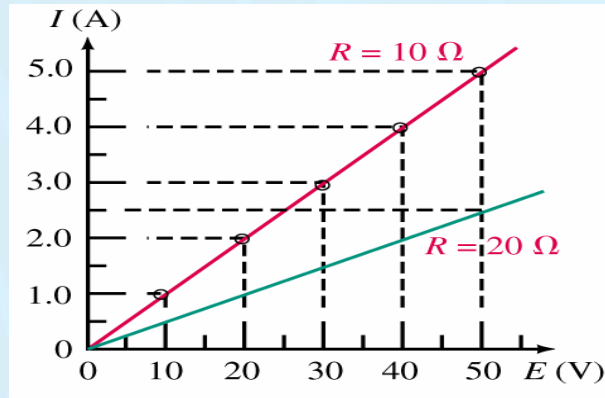

7

Open Circuits

- Current can only exist where there is a conductive path
- Open circuit
 - When there is no conductive path

8

Open Circuits

- If $I = 0$
 - Ohm's Law gives $R = E/I = E/0 \rightarrow$ infinity
- An open circuit has infinite resistance

9

Voltage Symbols

- Voltage sources
 - Uppercase E
- Voltage drops
 - Uppercase V
- $V = IR$
 - IR drops


10

Voltage Polarities

- Polarity of voltage drops across resistors is important in circuit analysis
- Drop is + to – in the direction of conventional current
- To show this, place plus sign at the tail of current arrow

11

Voltage Polarities

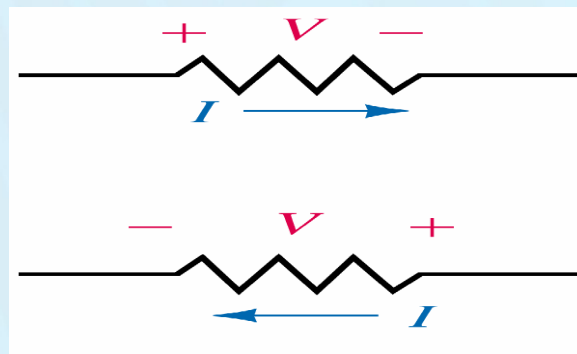

12

Current Direction

- Current usually proceeds out of the positive terminal of a voltage source
- If the current is actually in this direction, it will be supplying power to the circuit

13

Current Direction

- If the current is in the opposite direction (going into the positive terminal), it will be absorbing power (like a resistor)


14

Current Direction

- See two representations of the same current on next slide
- Notice that a negative current actually proceeds in a direction opposite to the current arrow

15

Current Direction

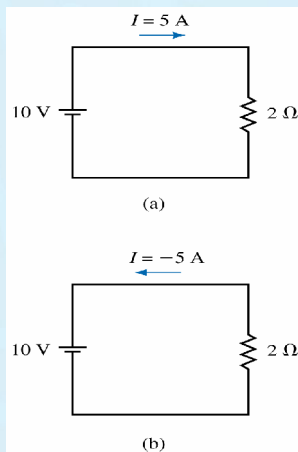

16

Power

- The greater the power rating of a light, the more light energy it can produce each second
- The greater the power rating of a heater, the more heat energy it can produce

17

Power

- The greater the power rating of a motor, the more mechanical work it can do per second
- Power is related to energy
 - Capacity to do work

18

Power

- Power is the rate of doing work
 - Power = Work/time
- Power is measured in **watts (W)**
- Work and energy measured in **joules (J)**
- One watt =
 - One joule per second

19

Power in Electrical Systems

- From $V = W/Q$ and $I = Q/t$, we get
$$P = VI$$
- From Ohm's Law, we can also find that
$$P = I^2R \text{ and } P = V^2/R$$
- Power is always in watts

20

Power in Electrical Systems

- We should be able to use any of the power equations to solve for V , I , or R if P is given

- For example:

$$I = \sqrt{\frac{P}{R}}$$

$$V = \sqrt{PR}$$

21

Power Rating of Resistors

- Resistors must be able to safely dissipate their heat without damage
- Common power ratings of resistors are 1/8, 1/4, 1/2, 1, or 2 watts

22

Power Rating of Resistors

- A safety margin of two times the expected power is customary
- An overheated resistor
 - Often the symptom of a problem rather than its cause

23

Energy

- Energy =
 - Power × time
- Units are joules
- Watt-seconds
 - Watt-hours or kilowatt-hours

24

Energy

- Energy use is measured in kilowatt-hours by the power company
- For multiple loads
 - Total energy is sum of the energy of individual loads

25

Energy

- Cost =
 - Energy × cost per unit or
- Cost =
 - Power × time × cost per unit

26

Energy

- To find the cost of running a 2000-watt heater for 12 hours if electric energy costs \$0.08 per kilowatt-hour:
 - Cost = 2kW × 12 hr × \$0.08 Cost = \$1.92

27

Law of Conservation of Energy

- Energy can neither be created nor destroyed
 - Converted from one form to another
- Examples:
 - Electric energy into heat
 - Mechanical energy into electric energy

28

Law of Conservation of Energy

- Energy conversions
 - Some energy may be dissipated as heat, giving lower efficiency

29

Efficiency

- Poor efficiency in energy transfers results in wasted energy
- An inefficient piece of equipment generates more heat
 - Heat must be removed

30

Efficiency

- Efficiency (in %) is represented by η (Greek letter eta)
 - Ratio of power out to power

$$\eta = \frac{P_{\text{out}}}{P_{\text{in}}} \times 100 \%$$

- Heat removal requires fans and heat sinks

31

Efficiency

- Always less than or equal to 100%
- Efficiencies vary greatly:
 - Power transformers may have efficiencies of up to 98%
 - Some amplifiers have efficiencies below 50%

32

Efficiency

- To find the total efficiency of a system
 - Obtain product of individual efficiencies of all subsystems:

$$\eta_{\text{Total}} = \eta_1 \times \eta_2 \times \eta_3 \times \dots$$

33

This document was created with Win2PDF available at <http://www.daneprairie.com>.
The unregistered version of Win2PDF is for evaluation or non-commercial use only.