

Chapter 9

Network Theorems

Superposition Theorem

- Total current through or voltage across a resistor or branch
 - Determine by adding effects due to each source acting independently
- Replace a voltage source with a short

Superposition Theorem

- Replace a current source with an open
- Find results of branches using each source independently
 - Algebraically combine results

3

Superposition Theorem

- Power
 - Not a linear quantity
 - Found by squaring voltage or current
- Theorem does not apply to power
 - To find power using superposition
 - Determine voltage or current
 - Calculate power

4

Thévenin's Theorem

- Lumped linear bilateral network
 - May be reduced to a simplified two-terminal circuit
 - Consists of a single voltage source and series resistance


5

Thévenin's Theorem

- Voltage source
 - Thévenin equivalent voltage, E_{Th} .
- Series resistance is Thévenin equivalent resistance, R_{Th}

6

Thévenin's Theorem

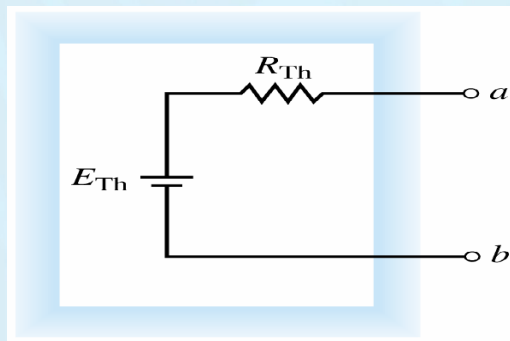

7

Thévenin's Theorem

- To convert to a Thévenin circuit
 - First identify and remove load from circuit
- Label resulting open terminals

8

Thévenin's Theorem

- Set all sources to zero
- Replace voltage sources with shorts, current sources with opens
- Determine Thévenin equivalent resistance as seen by open circuit

9

Thévenin's Theorem

- Replace sources and calculate voltage across open
- If there is more than one source
 - Superposition theorem could be used

10

Thévenin's Theorem

- Resulting open-circuit voltage is Thévenin equivalent voltage
- Draw Thévenin equivalent circuit, including load

11

Norton's Theorem

- Similar to Thévenin circuit
- Any lumped linear bilateral network
 - May be reduced to a two-terminal circuit
 - Single current source and single shunt resistor


12

Norton's Theorem

- $R_N = R_{Th}$
- I_N is Norton equivalent current

13

Norton's Theorem

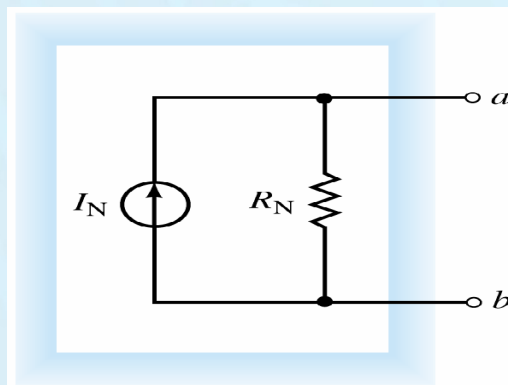

14

Norton's Theorem

- To convert to a Norton circuit
 - Identify and remove load from circuit
- Label resulting two open terminals
- Set all sources to zero

15

Norton's Theorem

- Determine open circuit resistance
 - This is Norton equivalent resistance
- Note
 - This is accomplished in the same manner as Thévenin equivalent resistance

16

Norton's Theorem

- Replace sources and determine current that would flow through a short place between two terminals
- This current is the Norton equivalent current

17

Norton's Theorem

- For multiple sources
 - Superposition theorem could be used
- Draw the Norton equivalent circuit
 - Including the load


18

Norton's Theorem

- Norton equivalent circuit
 - May be determined directly from a Thévenin circuit (or vice-versa) by using source transformation theorem

19

Norton's Theorem

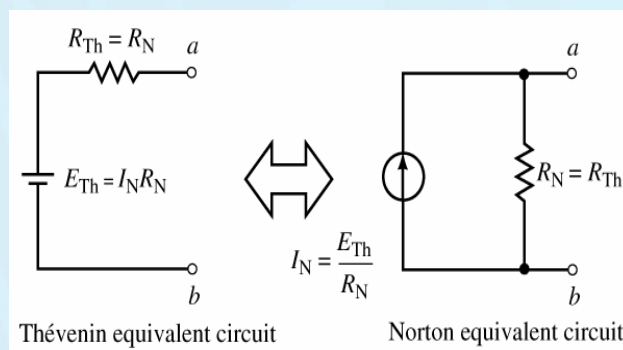

20

Maximum Power Transfer

- Load should receive maximum amount of power from source
- Maximum power transfer theorem states
 - Load will receive maximum power from a circuit when resistance of the load is exactly the same as Thévenin (or Norton) equivalent resistance of the circuit

21

Maximum Power Transfer

- To calculate maximum power delivered by source to load
 - Use $P = V^2/R$
- Voltage across load is one half of Thévenin equivalent voltage

22

Maximum Power Transfer

- Current through load is one half of Norton equivalent current

$$P_{\max} = \frac{E_{\text{Th}}^2}{4 R_{\text{Th}}} = \frac{I_{\text{N}}^2 R_{\text{N}}}{4}$$


23

Maximum Power Transfer

- Power across a load changes as load changes by using a variable resistance as the load


24

Maximum Power Transfer

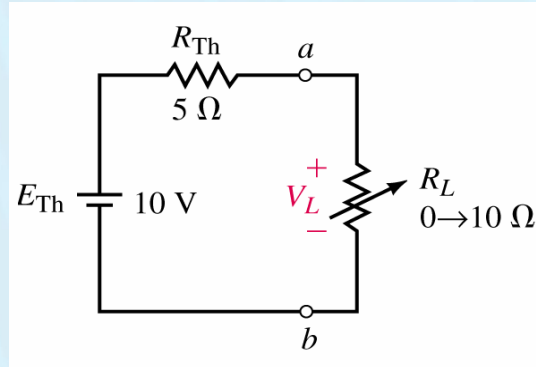

25

Maximum Power Transfer

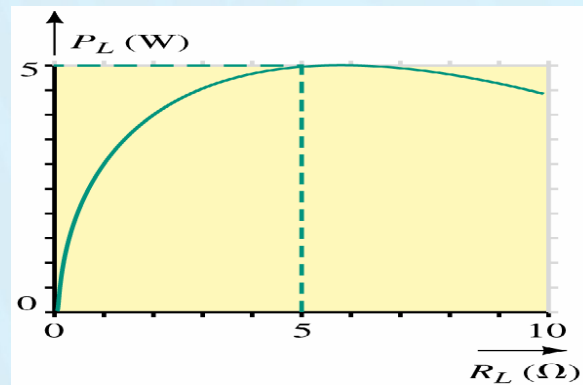

26

Efficiency

- To calculate efficiency:

$$\eta = \frac{P_{\text{out}}}{P_{\text{in}}}$$

$$\eta = \frac{P_{\text{out}}}{P_{\text{in}}} \times 100\%$$

$$\eta = \frac{\frac{E_{\text{Th}}^2}{4R_{\text{Th}}}}{\frac{E_{\text{Th}}^2}{2R_{\text{Th}}}} \times 100\% = 50\%$$

27

Substitution Theorem

- Any branch within a circuit may be replaced by an equivalent branch
 - Provided the replacement branch has same current voltage
- Theorem can replace any branch with an equivalent branch
- Simplify analysis of remaining circuit


28

Substitution Theorem

- Part of the circuit shown is to be replaced with a current source and a $240\ \Omega$ shunt resistor
 - Determine value of the current source

29

Substitution Theorem

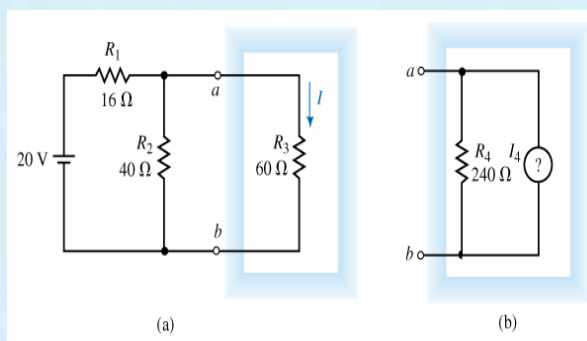

30

Millman's Theorem

- Used to simplify circuits that have
 - Several parallel-connected branches containing a voltage source and series resistance
 - Current source and parallel resistance
 - Combination of both

31

Millman's Theorem

- Other theorems may work, but Millman's theorem provides a much simpler and more direct equivalent

32

Millman's Theorem

- Voltage sources
 - May be converted into an equivalent current source and parallel resistance using source transformation theorem
- Parallel resistances may now be converted into a single equivalent resistance

33

Millman's Theorem

- First, convert voltage sources into current sources
- Equivalent current, I_{eq} , is just the algebraic sum of all the parallel currents

34

Millman's Theorem


- Next, determine equivalent resistance, R_{eq} , the parallel resistance of all the resistors
- Voltage across entire circuit may now be calculated by:

$$E_{eq} = I_{eq} R_{eq}$$

35

Millman's Theorem

- We can simplify a circuit as shown:

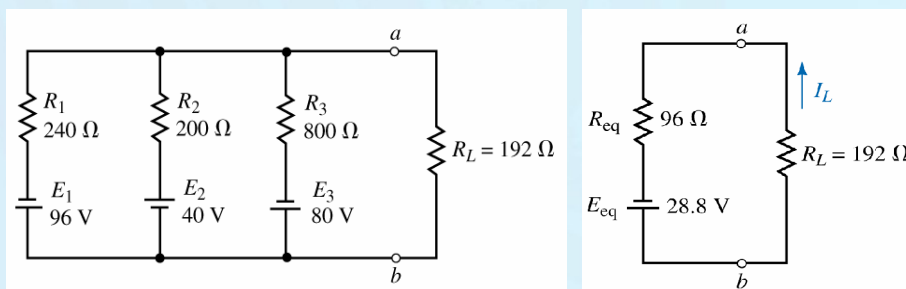

36

Reciprocity Theorem

- A voltage source causing a current I in any branch
 - May be removed from original location and placed into that branch

37

Reciprocity Theorem

- Voltage source in new location will produce a current in original source location
 - Equal to the original I

38

Reciprocity Theorem

- Voltage source is replaced by a short circuit in original location
- Direction of current must not change

39

Reciprocity Theorem

- A current source causing a voltage V at any node
 - May be removed from original location and connected to that node
- Current source in the new location
 - Will produce a voltage in original location equal to V

40

Reciprocity Theorem

- Current source is replaced by an open circuit in original location
- Voltage polarity cannot change

41

This document was created with Win2PDF available at <http://www.daneprairie.com>.
The unregistered version of Win2PDF is for evaluation or non-commercial use only.