


Chapter 11

Capacitive Charging, Discharging, and Simple Waveshaping Circuits

Introduction

- Circuit
 - Capacitor charging and discharging
 - Transient voltages and currents result when circuit is switched

Introduction

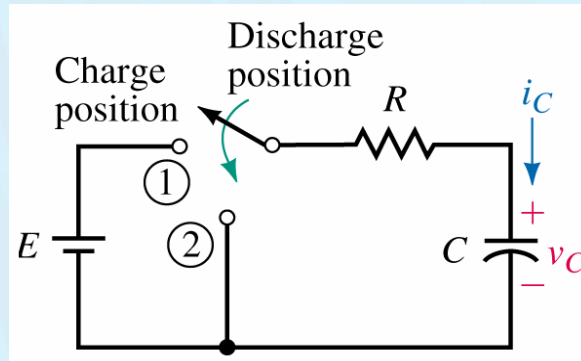

3

Capacitor Charging

- Charging a capacitor that is discharged
 - When switch is closed, the current instantaneously jumps to E/R
 - Exponentially decays to zero
- When switching, the capacitor looks like a short circuit

4


Capacitor Charging

- Voltage begins at zero and exponentially increases to E volts
- Capacitor voltage cannot change instantaneously

5

Capacitor Charging

- Capacitor voltage has shape shown:

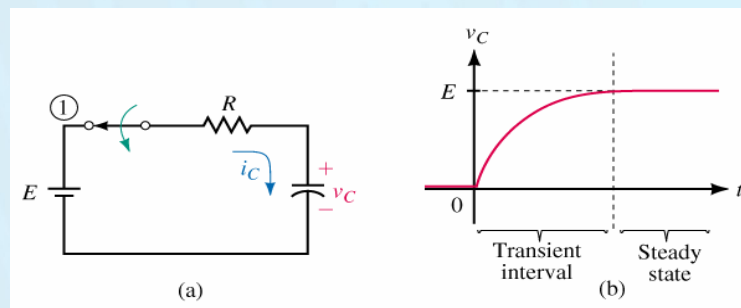

6

Steady State Conditions

- Circuit is at steady state
 - When voltage and current reach their final values and stop changing
- Capacitor has voltage across it, but no current flows through the circuit
- Capacitor looks like an open circuit

7


Capacitor Discharging

- Assume capacitor has E volts across it when it begins to discharge
- Current will instantly jump to $-E/R$
- Both voltage and current will decay exponentially to zero

8

Capacitor Discharging

- Here are the decay waveforms:

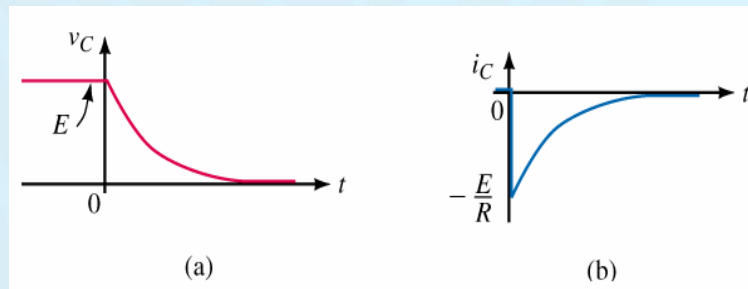

9

Capacitor Charging Equations

- Voltages and currents in a charging circuit do not change instantaneously
- These changes over time are exponential changes

10

Capacitor Charging Equations

- Equation for voltage across the capacitor as a function of time is

$$v_C = E \left(1 - e^{-t/RC} \right)$$

11

Capacitor Charging Equations

- Voltage across resistor is found from KVL: $E - v_C$

$$V_R = E e^{-t/RC}$$


- The current in the circuit is

$$i_C = \frac{E}{R} e^{-t/RC}$$

12

Capacitor Charging Equations

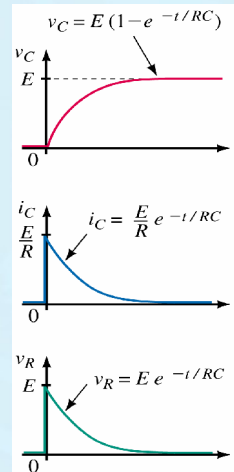- Values may be determined from these equations
- Waveforms are shown to right



13

The Time Constant

- Rate at which a capacitor charges depends on product of R and C
- Product known as time constant
- $\tau = RC$
- τ (Greek letter tau) has units of seconds

14

Duration of a Transient

- Length of time that a transient lasts depends on exponential function $e^{-t/\tau}$
- As t increases
 - Function decreases
 - When the t reaches infinity, the function decays to zero

15

Duration of a Transient

- For all practical purposes, transients can be considered to last for only five time constants

16

Capacitor with an Initial Voltage

- Voltage denoted as V_0
 - Capacitor has a voltage on it
- Voltage and current in a circuit will be affected by initial voltage

17

Capacitor with an Initial Voltage

$$v_C = E + (V_0 - E)e^{-t/\tau}$$

$$i_C = \frac{E - V_0}{R} e^{-t/\tau}$$

18

Capacitor Discharging Equations

- If a capacitor is charged to voltage V_0 and then discharged, the equations become

$$v_C = V_0 e^{-t/\tau}$$

$$v_R = -V_0 e^{-t/\tau}$$

$$i_C = -\frac{V_0}{R} e^{-t/\tau}$$

19


Capacitor Discharge Equations

- Current is negative because it flows opposite to reference direction
- Discharge transients last five time constants
- All voltages and currents are at zero when capacitor has fully discharged

20

Capacitor Discharge Equations

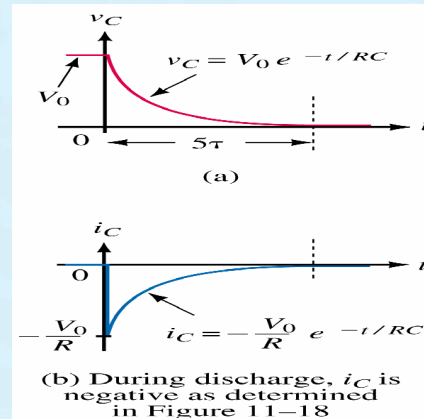- Curves shown represent voltage and current during discharge



21

More Complex Circuits

- You may have to use Thévenin's theorem (those with multiple resistors)
- Remove capacitor as the load and determine Thévenin equivalent circuit

22

More Complex Circuits

- Use R_{Th} to determine τ
- $\tau = R_{Th} \cdot C$
- Use E_{Th} as the equivalent source voltage


23

An *RC* Timing Application

- *RC* circuits
 - Used to create delays for alarm, motor control, and timing applications
- Alarm unit shown contains a threshold detector
 - When input to this detector exceeds a preset value, the alarm is turned on

24

An RC Timing Application

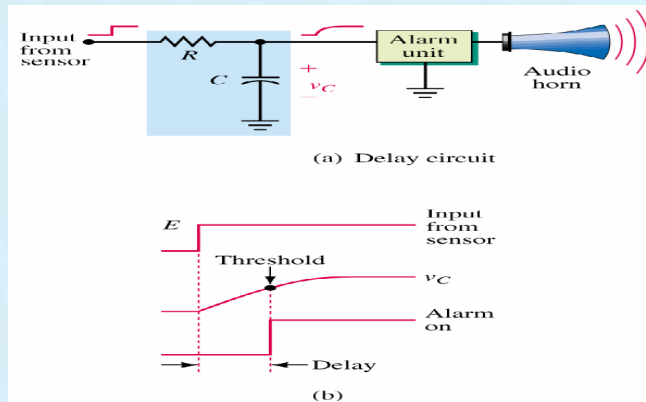

25

Pulse Response of RC Circuits

- Pulse
 - Voltage or current that changes from one level to another and back again
- Periodic waveform
 - Pulse train is a repetitive stream of pulses

26

Pulse Response of *RC* Circuits

- Square wave
 - Waveform's time high equals its time low
- Length of each cycle of a pulse train is its period

27

Pulse Response of *RC* Circuits

- Number of pulses per second is its pulse repetition frequency
- Width of pulse compared to its period is its duty cycle
- Usually given as a percentage

28

Pulse Response of *RC* Circuits

- Pulses have a rise and fall time
 - Because they do not rise and fall instantaneously
- Rise and fall times are measured between the 10% and 90% points

29

The Effect of Pulse Width

- Width of pulse relative to a circuit's time constant
 - Determines how it is affected by an *RC* circuit
- If pulse width $\gg 5\tau$
 - Capacitor charges and discharges fully
 - With the output taken across the resistor, this is a differentiator circuit

30

The Effect of Pulse Width

- If pulse width = 5τ
 - Capacitor fully charges and discharges during each pulse
- If the pulse width $\ll 5\tau$
 - Capacitor cannot fully charge and discharge
 - This is an integrator circuit



31

Simple Waveshaping Circuits

- Circuit (a) provides approximate integration if $5\tau \gg T$
- Circuit (b) provides approximate differentiation if $T \gg 5\tau$

32

Simple Waveshaping Circuits

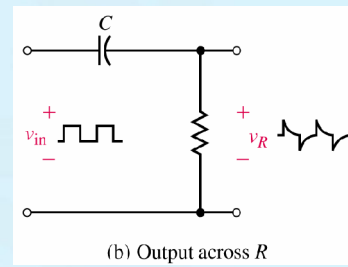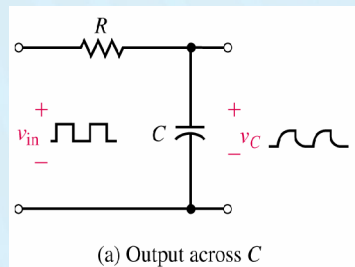

33

Capacitive Loading

- Capacitance
 - Occurs when conductors are separated by insulating material
 - Leads to stray capacitance
 - In high-speed circuits this can cause problems

34

This document was created with Win2PDF available at <http://www.daneprairie.com>.
The unregistered version of Win2PDF is for evaluation or non-commercial use only.