

## Chapter 14

### Inductive Transients

## Transients

- Voltages and currents during a transitional interval
  - Referred to as transient behavior of the circuit
- Capacitive circuit
  - Voltages and currents undergo transitional phase
  - Capacitor charges and discharges

## Transients

- Inductive circuit
  - Transitional phase occurs as the magnetic field builds and collapses

3

## Voltage Across an Inductor

- Induced voltage across an inductor is proportional to rate of change of current

$$V_L = L \frac{\Delta i}{\Delta t}$$

4

## Voltage Across an Inductor

- If inductor current could change instantaneously
  - Its rate of change would be infinite
  - Would cause infinite voltage



5

## Continuity of Current

- Infinite voltage is not possible
  - Inductor current cannot change instantaneously
  - It cannot jump from one value to another, but must be continuous at all times
- Use observation when analyzing circuits

6

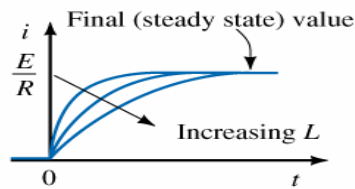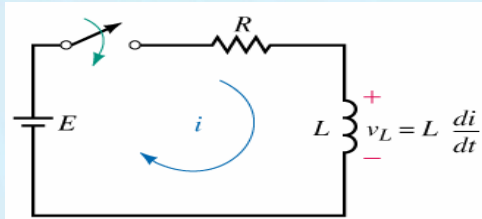Circuit and  
Waveforms  
for  
Current  
Build-up



(b) Adding inductance causes  
a transient to appear.  
 $R$  is held constant here

7

## Inductor Voltage

- Immediately after closing the switch on an  $RL$  circuit
  - Current is zero
  - Voltage across the resistor is zero

8

## Inductor Voltage

- Voltage across resistor is zero
  - Voltage across inductor is source voltage
- Inductor voltage will then exponentially decay to zero

9

## Open-Circuit Equivalent

- After switch is closed
  - Inductor has voltage across it and no current through it
- Inductor with zero initial current looks like an open circuit at instant of switching

10

## Open-Circuit Equivalent

- This statement will later be applied to include inductors with nonzero initial currents

11

## Initial Condition Circuits

- Voltages and currents in circuits immediately after switching
  - Determined from the open-circuit equivalent

12

## Initial Condition Circuits

- By replacing inductors with opens
  - We get initial condition circuit
- Initial condition networks
  - Yield voltages and currents only at switching

13

## Circuit Current

- Current in an  $RL$  circuit is an exponentially increasing function of time
- Current begins at zero and rises to a maximum value

$$i(t) = \frac{E}{R} \left( 1 - e^{-Rt/L} \right)$$

14

## Circuit Voltages

- Voltage across resistor is given by  $i \cdot R$
- Voltage across resistor is an increasing function as well (because the inductor current is passing through it)

$$v_R = E \left( 1 - e^{-\frac{Rt}{L}} \right)$$

15

## Circuit Voltages

- By KVL, voltage across inductor is

$$E - v_R$$

- Voltage across inductor is an exponentially decreasing function of time

$$v_L = E \cdot e^{-Rt/L}$$

16



## Time Constant

- $\tau = L/R$
- Units are seconds
- Equations may now be written as

$$i = \frac{E}{R} (1 - e^{-t/\tau})$$

$$v_L = E \cdot e^{-t/\tau}$$

$$v_R = E (1 - e^{-t/\tau})$$

17

## Time Constant

- The larger the inductance
  - The longer the transient
- The larger the resistance
  - The shorter the transient

18

## Time Constant

- As  $R$  increases
  - Circuit looks more and more resistive
  - If  $R$  is much greater than  $L$
  - Circuit looks purely resistive

19

## Interrupting Current in an Inductive Circuit

- When switch opens in an  $RL$  circuit
  - Energy is released in a short time
  - This may create a large voltage
  - Induced voltage is called an inductive kick
- Opening of inductive circuit may cause voltage spikes of thousands of volts

20

## Interrupting a Circuit

- Switch flashovers are generally undesirable
  - They can be controlled with proper engineering design
- These large voltages can be useful
  - Such as in automotive ignition systems

21


## Interrupting a Circuit

- It is not possible to completely analyze such a circuit
  - Resistance across the arc changes as the switch opens

22
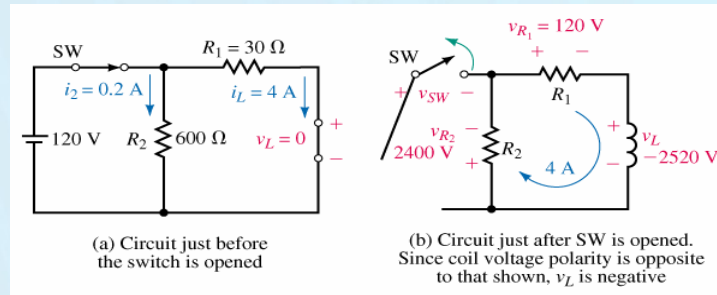
## Interrupting a Circuit

- In circuit shown, we see changes after switch opens:



23

## Inductor Equivalent at Switching

- Current through an inductor
  - Same after switching as before switching
- An inductance with an initial current
  - Looks like a current source at instant of switching
- Its value is value of current at switching

24

## De-energizing Transients

- If an inductor has an initial current  $I_0$ , equation for current becomes

$$i = I_0 e^{-t/\tau'}$$

- $\tau' = L/R$ .  $R$  equals total resistance in discharge path

25

## De-energizing Transients

- Voltage across inductor goes to zero as circuit de-energizes

$$V_L = V_0 e^{-t/\tau'}$$

where

$$V_0 = -I_0 R_T$$

26

## De-energizing Circuits

- Voltage across any resistor is product of current and that resistor

$$v_R = R \cdot I_0 e^{-t/\tau}$$

- Voltage across each of resistors goes to zero

27

## More Complex Circuits

- For complex circuits
  - Like capacitive circuits
    - Necessary to determine Thévenin equivalent circuit using inductor as the load

28

## More Complex Circuits

- $R_{Th}$  is used to determine time constant
- $\tau = L/R_{Th}$
- $E_{Th}$  is used as source voltage

29

This document was created with Win2PDF available at <http://www.daneprairie.com>.  
The unregistered version of Win2PDF is for evaluation or non-commercial use only.