

Chapter 17

Power in AC Circuits

Active Power

- Instantaneous power to a load is $p = v \cdot i$
- In an ac circuit
 - p may be positive sometimes and negative other times
- Average value of the power, P
 - Real power

Active Power

- Average value of instantaneous power, real power, active power, and average power mean the same thing

3

Reactive Power

- During times when p is negative, power is being returned from load
- This can happen for inductive or capacitive loads

4

Reactive Power

- Power that flows into these loads and back out is called the reactive power
- Average value of reactive power is zero

5

Power to a Resistive Load

$$p = vi = (V_m \sin \omega t)(I_m \sin \omega t)$$

$$p = V_m I_m \sin^2 \omega t$$

$$p = \frac{V_m I_m}{2} (1 - \cos 2\omega t)$$

6

Power to a Resistive Load

- p is always positive (except when zero)
- Power flows only from source to load
 - Power is absorbed by the load
- Power to a pure resistance consists of active power only

7

Average Power

- Average value of power is halfway between zero and peak value of $V_m I_m$
- $P = V_m I_m / 2$
- If V and I are in RMS values
 - Then $P = VI$

8

Average Power

- Also, $P = I^2R$ and $P = V^2/R$
- Active power relationships for resistive circuits are the same for ac as for dc

9

Power to an Inductive Load

- Voltage and current of an inductor are 90° out of phase
 - Average power to an inductance over a full cycle is zero
- There are no power losses associated with a pure inductance

10

Power to an Inductive Load

- Power that flows into and out of a pure inductance is reactive power only

11

Power to an Inductive Load

- $p_L = VI \sin 2\omega t$ (V and I rms values)
- Product VI is the reactive power, Q_L
- $Q_L = VI = I^2 X_L = V^2 / X_L$
- Units are VARs

12

Power to an Inductive Load

- VAR means Volt-Amperes-Reactive
- Inductive reactive power is represented as positive

13

Power to a Capacitive Load

- Voltage and current are 90° out of phase
 - Average power over one complete cycle is equal to zero
- There are no power losses associated with a pure capacitance

14

Power to a Capacitive Load

- Power that flows into and out of a pure capacitance is reactive power only
- This power cycle is 180° out of phase with the inductive cycle

15

Power to a Capacitive Load

- $p_C = -VI \sin 2\omega t$
- $Q_C = VI$
- $Q_C = I^2 X_C = V^2 / X_C$
- Capacitive reactive power is represented as negative
- Units are VARs

16

Power in More Complex Circuits

- It does not matter how a circuit or system is connected
 - Sum of the power is found by summing individual powers
- Total real power P is found by summing each of the individual real powers

17

Power in More Complex Circuits

- Total Reactive power Q is found by summing individual Q 's
 - Inductive powers are positive
 - Capacitive powers are negative

18

Apparent Power

- Power to a load is VI
- If load has both resistance and reactance
 - Product is neither the real power nor the reactive power, but a combination of both

19


Apparent Power

- This is called the apparent power, S
- $S = VI = I^2Z = V^2/Z$
- Units are volt-amperes (VA)

20

Relationship Between P , Q , and S

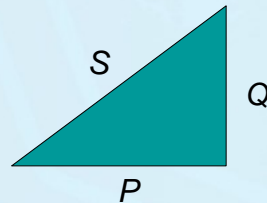- P , Q , and S are related by the “power triangle”



$$S = \sqrt{P^2 + Q^2}$$

21

Active and Reactive Power Equations

- $P = VI \cos \theta = S \cos \theta$
- $Q = VI \sin \theta = S \sin \theta$
- V and I are RMS values
- θ is the phase angle between V and I
- Q is positive for inductive circuits and negative for capacitive circuits

22

Power Factor

- Ratio of real power to apparent power is called the power factor, F_p
- $F_p = P/S = \cos \theta$
- Angle θ is angle between voltage and current

23

Power Factor

- For pure resistance $\theta = 0^\circ$
- For inductance, $\theta = 90^\circ$
- For capacitance, $\theta = -90^\circ$
- For a circuit containing a mixture, θ is somewhere between 0° and $\pm 90^\circ$

24

Power Factor

- Unity power factor
 - For a purely resistive circuit, the power factor will be one
- For load containing resistance and inductance
 - Power factor will be less than one and lagging
 - Current lags the voltage

25

Power Factor

- For a circuit containing resistance and capacitance
 - F_p is less than one and is leading

26

Why Equipment Is Rated in VA

- A highly reactive load
 - May seem to require a small amount of power while requiring a large current
- Equipment is rated in VA to prevent overloading the circuit

27

Why Equipment Is Rated in VA

- Size of electrical apparatus required by a load
 - Governed by its VA requirements

28

Power Factor Correction

- A load with a small power factor can draw a large current
- Can be alleviated by
 - Cancelling some or all reactive components of power by adding reactance of opposite type to the circuit
 - This is power factor correction

29

Power Factor Correction

- Industrial customers may pay a penalty for low power factors due to large currents required for highly reactive loads

30

AC Power Measurement

- To measure power in an ac circuit you need a wattmeter
- Meter consists of
 - Current-sensing circuit
 - Voltage-sensing circuit
 - Multiplier circuit
 - Averaging circuit

31

AC Power Measurement

- This will measure load voltage and current and find the product and the angle between these

32

Effective Resistance

- At high frequencies
 - Resistance of a circuit may change
- $R_{\text{eff}} = P/I^2$
 - Anything that affects P will affect resistance

33

Effective Resistance

- Changing magnetic fields may set up eddy currents in conductors
 - These cause power losses that affect effective resistance

34

Effective Resistance

- Ferromagnetic materials
 - Power losses due to hysteresis effects
- Magnetically induced voltages created by a changing magnetic field cause a non-uniform current called a skin effect
 - Causes an increase in resistance
 - Energy escapes due to radiation resistance

35

This document was created with Win2PDF available at <http://www.daneprairie.com>.
The unregistered version of Win2PDF is for evaluation or non-commercial use only.