

## Chapter 19

### Methods of AC Analysis

## Dependent Sources

- Voltages and currents of independent sources
  - Not dependent upon any voltage or current elsewhere in the circuit
- In some circuits
  - Operation of certain devices replaces device with an equivalent model

## Dependent Sources

- Models are dependent upon an internal voltage or current elsewhere in the circuit

3

## Dependent Sources

- Have a magnitude and phase angle determined by voltage or current at some other circuit element multiplied by a constant  $k$
- Magnitude of  $k$  is determined by parameters within particular model

4

## Dependent Sources

- Units of constant correspond to required quantities in the equation

5

## Source Conversion

- A voltage source  $E$  in series with an impedance  $Z$ 
  - Equivalent to a current source  $I$  having the same impedance  $Z$  in parallel
- $I = E/Z$
- $E = IZ$

6

## Source Conversion

- Voltages and currents at terminals will be the same
  - Internal voltages and currents will differ

7

## Source Conversion

- A dependent source may be converted by the same method
- Controlling element external to circuit
- If controlling element is in the same circuit as the dependent source
  - Procedure cannot be used

8

## Mesh Analysis

- Method exactly the same as for dc
  - Convert all sinusoidal expressions into phasor notation
  - Convert current sources to voltage sources
  - Redraw circuit, simplifying the given impedances

9

## Mesh Analysis

- Assign clockwise loop currents to each interior closed loop
- Show polarities of all impedances

10

## Mesh Analysis

- Apply KVL to each loop and write resulting equations
- Voltages that are voltage rises in the direction of the assumed current are positive
  - Voltages that drop are negative

11

## Mesh Analysis

- Solve the resulting simultaneous linear equations or matrix equations

12

## Nodal Analysis

- Method is exactly the same as for dc
- Nodal analysis will calculate all nodal voltages with respect to ground
- Convert all sinusoidal expressions into equivalent phasor notation

13

## Nodal Analysis

- Convert all voltage sources to current sources
- Redraw the circuit
  - Simplifying given impedances and expressing impedances as admittances

14

## Nodal Analysis

- Assign subscripted voltages to nodes
  - Select an appropriate reference node
- Assign assumed current directions through all branches
- Apply KCL to each node
- Solve resulting equations for node voltages

15

## Delta-to-Wye Conversion

- Impedance in any arm of a Y circuit
  - Determined by taking the product of two adjacent  $\Delta$  impedances at this arm
  - Divide by the summation of the  $\Delta$  impedances

16



## Delta-to-Wye Conversion

$$Z_1 = \frac{Z_b Z_c}{Z_a + Z_b + Z_c}$$

$$Z_2 = \frac{Z_a Z_c}{Z_a + Z_b + Z_c}$$

$$Z_3 = \frac{Z_a Z_b}{Z_a + Z_b + Z_c}$$

17

## Wye-to-Delta Conversions

- Any impedance in a  $\Delta$ 
  - Determined by summing all possible two-impedance product combinations of the Y
  - Divide by impedance found in opposite branch of the Y

18

## Wye-to-Delta Conversions

$$Z_a = \frac{Z_1 Z_2 + Z_1 Z_3 + Z_2 Z_3}{Z_1}$$

$$Z_b = \frac{Z_1 Z_2 + Z_1 Z_3 + Z_2 Z_3}{Z_2}$$

$$Z_c = \frac{Z_1 Z_2 + Z_1 Z_3 + Z_2 Z_3}{Z_3}$$

19

## Bridge Networks

- Bridge circuits are used to measure the values of unknown components
- Any bridge circuit is balanced when the current through branch between two arms is zero

20

## Bridge Networks

- The condition of a balanced bridge occurs when

$$\frac{Z_1}{Z_3} = \frac{Z_2}{Z_4}$$

21

## Bridge Networks

- When a balanced bridge occurs in a circuit
  - Equivalent impedance of bridge is found by removing central **Z** and replacing it by a short or open circuit
- Resulting **Z** is then found by solving series-parallel circuit

22

## Bridge Networks

- For an unbalanced bridge
  - $Z$  can be determined by  $\Delta$ -to-Y conversion or mesh analysis


23

## Maxwell Bridge

- Used to determine the  $L$  and  $R$  of an inductor having a large series resistance
- $L = R_2 R_3 C$     $R = R_2 R_3 / R_1$

24

## Maxwell Bridge

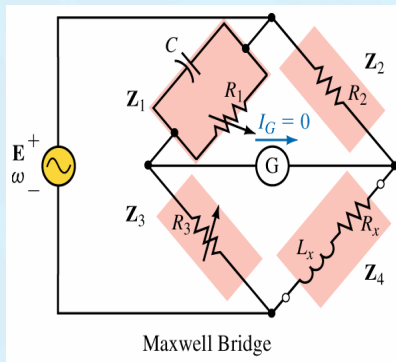

25

## Hay Bridge


- Used to measure the  $L$  and  $R$  of an inductor having a small series resistance

26
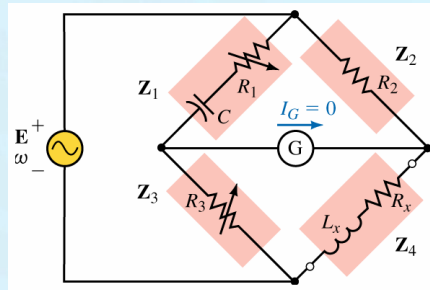
## Hay Bridge

$$L_x = \frac{R_2 R_3 C}{\omega^2 R_1^2 C^2 + 1}$$

$$R_x = \frac{\omega^2 R_1 R_2 R_3 C^2}{\omega^2 R_1^2 C^2 + 1}$$




27

## Schering Bridge

- Used to determine an unknown capacitance

$$C = \frac{R_1 C_3}{R_2}$$

$$R = \frac{C_1 R_2}{C_3}$$

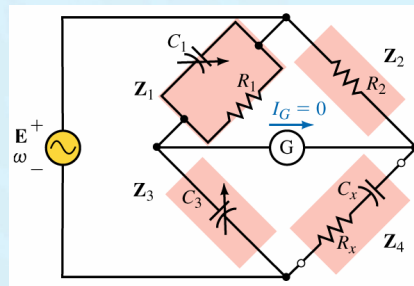

28

This document was created with Win2PDF available at <http://www.daneprairie.com>.  
The unregistered version of Win2PDF is for evaluation or non-commercial use only.