

Chapter 21


Resonance

Series Resonance

- Simple series resonant circuit
 - Has an ac source, an inductor, a capacitor, and possibly a resistor
- $\mathbf{Z}_T = R + jX_L - jX_C = R + j(X_L - X_C)$
 - Resonance occurs when $X_L = X_C$
 - At resonance, $\mathbf{Z}_T = R$


Series Resonance

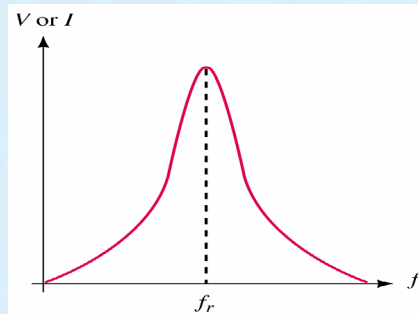- Response curves for a series resonant circuit



3

Series Resonance

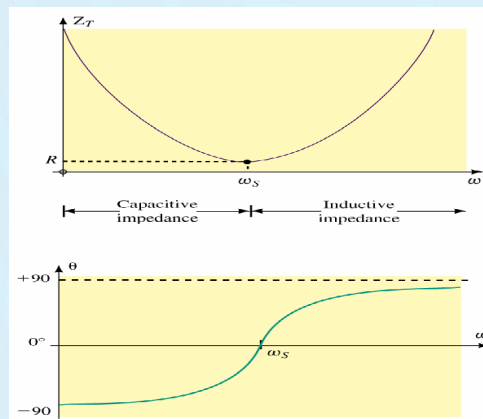

4

Series Resonance

- Since $X_L = \omega L = 2\pi fL$ and $X_C = 1/\omega C = 1/2\pi fC$ for resonance set $X_L = X_C$
 - Solve for the series resonant frequency f_s

$$\omega_s = \frac{1}{\sqrt{LC}} \text{ (rad/sec)}$$

$$f_s = \frac{1}{2\pi\sqrt{LC}} \text{ (Hz)}$$

5

Series Resonance

- At resonance
 - Impedance of a series resonant circuit is small and the current is large
- $I = E/Z_T = E/R$

6

Series Resonance

- At resonance

$$V_R = IR$$

$$V_L = IX_L$$

$$V_C = IX_C$$

7

Series Resonance

- At resonance, average power is $P = I^2R$
- Reactive powers dissipated by inductor and capacitor are I^2X
- Reactive powers are equal and opposite at resonance

8

The Quality Factor, Q

- Q = reactive power/average power
 - Q may be expressed in terms of inductor or capacitor

$$Q_s = \frac{I^2 X_L}{I^2 R} = \frac{X_L}{R} = \frac{\omega L}{R}$$

- For an inductor, $Q_{\text{coil}} = X_L / R_{\text{coil}}$

9

The Quality Factor, Q

- Q is often greater than 1
 - Voltages across inductors and capacitors can be larger than source voltage

$$Q_s = \frac{IX}{IR} = \frac{V}{E}$$

10

The Quality Factor, Q

- This is true even though the sum of the two voltages algebraically is zero

11

Impedance of a Series Resonant Circuit

- Impedance of a series resonant circuit varies with frequency

$$Z_T = R + j\omega L - \frac{j}{\omega C}$$

$$Z_T = R + j\left(\frac{\omega^2 LC - 1}{\omega C}\right)$$

$$Z_T = \sqrt{R^2 + \left(\frac{\omega^2 LC - 1}{\omega RC}\right)^2}$$

$$\theta = \tan^{-1}\left(\frac{\omega^2 LC - 1}{\omega RC}\right)$$

12

Bandwidth

- Bandwidth of a circuit
 - Difference between frequencies at which circuit delivers half of the maximum power
- Frequencies, f_1 and f_2
 - Half-power frequencies or the cutoff frequencies

13

Bandwidth

- A circuit with a narrow bandwidth
 - High selectivity
- If the bandwidth is wide
 - Low selectivity

14

Bandwidth

- Cutoff frequencies
 - Found by evaluating frequencies at which the power dissipated by the circuit is half of the maximum power

15

Bandwidth

$$I_{\text{hpf}} = \frac{I_{\text{max}}}{\sqrt{2}}$$

$$\omega_1 = 2\pi f_1 = \frac{-R}{2L} + \sqrt{\frac{R^2}{4L^2} + \frac{1}{LC}}$$

$$\omega_2 = 2\pi f_2 = \frac{R}{2L} + \sqrt{\frac{R^2}{4L^2} + \frac{1}{LC}}$$

16

Bandwidth

- From $BW = f_2 - f_1$
- $BW = R/L$
- When expression is multiplied by ω on top and bottom
 - $BW = \omega_s/Q$ (rad/sec) or $BW = f_s/Q$ (Hz)

17

Series-to-Parallel Conversion

- For analysis of parallel resonant circuits
 - Necessary to convert a series inductor and its resistance to a parallel equivalent circuit

$$R_P = \frac{R_S^2 + X_{LS}^2}{R_S}$$

$$X_{LP} = \frac{R_S^2 + X_{LS}^2}{X_{LS}}$$

$$Q = \frac{X_{LS}}{R_S} = \frac{R_P}{X_{LP}}$$

18

Series-to-Parallel Conversion

- If Q of a circuit is greater than or equal to 10
 - Approximations may be made
- Resistance of parallel network is approximately Q^2 larger than resistance of series network
 - $R_P \approx Q^2 R_S$
 - $X_{LP} \approx X_{LS}$

19

Parallel Resonance

- Parallel resonant circuit
 - Has X_C and equivalents of inductive reactance and its series resistor, X_{LP} and R_S
- At resonance
 - $X_C = X_{LP}$

20


Parallel Resonance

- Two reactances cancel each other at resonance
 - Cause an open circuit for that portion
- $Z_T = R_p$ at resonance

21

Parallel Resonance

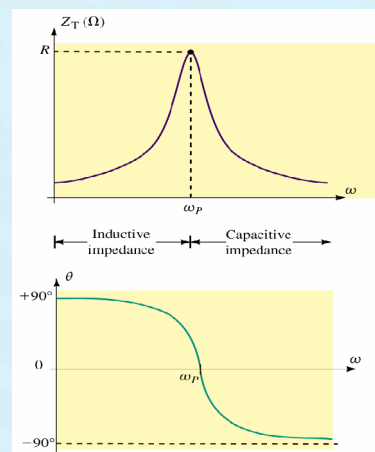- Response curves for a parallel resonant circuit



22

Parallel Resonance

- From $X_C = X_{LP}$
 - Resonant frequency is found to be

$$f = \frac{1}{2\pi\sqrt{LC}} \sqrt{1 - \frac{R^2C}{L}}$$

23

Parallel Resonance

- If $(L/C) \gg R$
 - Term under the radical is approximately equal to 1
- If $(L/C) \geq 100R$
 - Resonant frequency becomes

$$f = \frac{1}{2\pi\sqrt{LC}}$$

24

Parallel Resonance

- Because reactances cancel
 - Voltage is $V = IR$
- Impedance is maximum at resonance
 - $Q = R/X_C$
- If resistance of coil is the only resistance present
 - Circuit Q will be that of the inductor

25

Parallel Resonance

- Circuit currents are

$$I_R = \frac{V}{R}$$

$$I_L = \frac{V}{X_L} = QI$$

$$I_C = \frac{V}{X_C} = QI$$

26

Parallel Resonance

- Magnitudes of currents through the inductor and capacitor
 - May be much larger than the current source

27

Bandwidth

- Cutoff frequencies are

$$\omega_1 = \frac{1}{2RC} - \sqrt{\frac{1}{4R^2C^2} + \frac{1}{LC}}$$

$$\omega_2 = \frac{1}{2RC} + \sqrt{\frac{1}{4R^2C^2} + \frac{1}{LC}}$$

28

Bandwidth

- $BW = \omega_2 - \omega_1 = 1/RC$
- If $Q \geq 10$
 - Selectivity curve becomes symmetrical around ω_p

29

Bandwidth

- Equation of bandwidth becomes

$$BW = \frac{X_C \omega_P}{R}$$

$$BW = \frac{\omega_P}{Q_P}$$

- Same for both series and parallel circuits

30

This document was created with Win2PDF available at <http://www.daneprairie.com>.
The unregistered version of Win2PDF is for evaluation or non-commercial use only.