

Chapter 23

Transformers and Coupled Circuits

Transformer Construction

- Transformer is a magnetically coupled circuit
- It consists of two coils wound on a common core

Transformer Construction

- Power flows from one circuit to the other circuit
 - Through the medium of the magnetic field

3

Transformer Construction

- There is no electrical connection between the two coils
- Coil (winding) on side of the transformer to which we apply power is called primary

4

Transformer Construction

- Coil on side to which we connect the load is called the secondary

5

Transformer Construction

- Iron-core transformers
 - Generally used for low-frequency applications (such as audio and power)
- Iron core provides an easy path for magnetic flux

6

Transformer Construction

- Two basic construction types
 - Core and shell
- Each type uses laminated sheets of metal to reduce eddy currents

7

Transformer Construction

- Air-core and ferrite-core types
 - Used for high-frequency applications (such as radio frequencies)

8

Transformer Construction

- These do not have high hysteresis and eddy-current losses of iron-core transformers
- Ferrite
 - Increases coupling between coils while maintaining low losses

9

Transformer Construction

- Transformer may be used to change polarity of an ac voltage
 - Depending on the directions of its windings

10

Transformer Construction

- If most of the flux produced by one of the coils links the other
 - Coils are tightly coupled
 - Otherwise loosely coupled
- All transformer operations are described by Faraday's law

11

Voltage Ratio for Ideal Transformers

- If we apply Faraday's law, where N is the number of turns and ϕ is the flux, then

$$e_p = N_p \frac{\Delta\Phi}{\Delta t}$$

$$e_s = N_s \frac{\Delta\Phi}{\Delta t}$$

$$\frac{e_p}{e_s} = \frac{N_p}{N_s}$$

12

Voltage Ratio for Ideal Transformers

- Ratio of primary voltage to secondary voltage
 - Equal to ratio of the number of turns

13

The Turns Ratio

- Turns ratio (or the transformation ratio)
 - $a = N_p/N_s$
- Also, $e_p/e_s = a$

14

The Turns Ratio

- A step-up transformer
 - Secondary voltage is higher than the primary voltage ($a < 1$)
- A step-down transformer
 - Secondary voltage is lower ($a > 1$)

15

The Current Ratio

- In an ideal transformer
 - Power in equals power out ($\eta = 100\%$)
- Ratios of the current are

$$e_p i_p = e_s i_s$$

$$\frac{i_p}{i_s} = \frac{e_s}{e_p} = \frac{1}{a}$$

16

The Current Ratio

- If voltage is stepped up
 - Current is stepped down, and vice versa

17

Reflected Impedance

- A load impedance Z_L connected directly to a source is seen as Z_L
- Impedance will be seen by the source differently
 - If a transformer is connected between the source and the load

18

Reflected Impedance

- Reflected impedance, Z_p , is given by
 - $Z_p = a^2 Z_L$

19

Reflected Impedance

- Load characteristics do not change
 - Capacitive loads still look capacitive, etc.
- A transformer can make a load look larger or smaller
 - Depending on the turns ratio

20

Reflected Impedance

- Using a transformer
 - We can match loads to sources (such as amplifiers)
- Relates to the maximum power theorem discussed in a previous section

21

Transformer Ratings

- Transformers are rated in terms of voltage and apparent power
- Rated current can be determined from these ratings

22

Transformer Ratings

- By dividing the apparent power rating by the voltage rating
 - Rated current is determined, regardless of the power factor

23

Power Supply Transformers

- Used to convert the incoming 120 V source to voltage levels required by circuit
- Some have a multi-tapped secondary winding to provide different voltages for different applications

24

Power Supply Transformers

- Typically, an incoming voltage is
 - Stepped down
 - Rectified
 - Smoothed by a filter
 - Passed through a voltage regulator

25

Transformers in Power Systems

- Transformers are used at generating stations to raise voltage for transmission
 - This lowers losses in the transmission lines
- At the user end
 - Voltage is stepped down

26

Transformers in Power Systems

- Transformers have a split secondary
 - This permits both 120-V and 240-V loads to be supplied from the same transformer
- For residential use
 - Single phase is used

27

Isolation Applications

- Transformers are sometimes used to isolate equipment
- Isolation transformers are often used to make measurements involving high voltages

28

Isolation Applications

- They can also ensure that a grounded metal chassis is not connected to a hot wire

29

Isolation Applications

- Readings can be made on an oscilloscope
 - Must have a grounded lead without shorting circuit components across ground connections by using a 1:1 transformer

30

Impedance Matching

- A transformer can be used to raise or lower apparent impedance of a load
- Impedance matching
 - Sometimes used to match loads to amplifiers to achieve maximum power transfer

31

Impedance Matching

- If load and source are not matched
 - A transformer, with the proper turns ratio, can be inserted between them

32

Autotransformers

- In autotransformers
 - Primary circuit is not electrically isolated from its secondary
 - They cannot be used as isolation transformers

33

Autotransformers

- Smaller and cheaper than conventional transformers with the same load kVA

34

Practical Iron-Core Transformers

- Non-ideal transformers have several effects that cause loss of power
- Leakage flux
 - Will appear as small inductances in series with the windings

35

Practical Iron-Core Transformers

- Winding resistance
- Core losses due to eddy currents and hysteresis
- Magnetizing current

36

Transformer Efficiency

- Efficiency is ratio of output power to input power
 - Given as a percentage.
- Losses
 - Due to power losses in the windings and in core

37

Transformer Efficiency

- Large transformers can have efficiencies of 98 to 99 percent
- Smaller transformers have efficiencies of about 95 percent

38

Transformer Tests

- Losses may be determined by making tests on transformers
- Short-circuit tests
 - Determine losses due to resistance of windings
- Open-circuit tests will determine core losses

39

Voltage and Frequency Effects

- As applied voltage increases, core flux increases, causing greater magnetization current
 - Therefore, transformers should be operated only at or near their rated voltage

40

Voltage and Frequency Effects

- At very low frequencies
 - Core flux and the magnetizing current increases
 - Causing large internal voltage drops
- At very high frequencies
 - Stray capacitances and inductances cause voltage drops

41

Loosely Coupled Circuits

- Circuits without an iron core, where only a portion of the flux produced by one coil links another
- Cannot be characterized by turns ratios
 - They are characterized by self- and mutual inductances

42

Loosely Coupled Circuits

- Expressed by coefficient of coupling
 - Air-core
 - Ferrite-core transformers
 - General inductive circuit coupling

43

Loosely Coupled Circuits

- Self-induced voltage in a coil is
 - $v = L di/dt$
- Mutually induced voltage of a coil is
 - $v = M di/dt$
 - M is mutual inductance between coils

44

Loosely Coupled Circuits

- In each coil
 - Induced voltage is the sum of its self-induced voltage
 - Plus voltage mutually induced due to the current in the other coil

45

Loosely Coupled Circuits

- Coefficient of coupling, k
 - Describes degree of coupling between coils
- Mutual inductance depends on k :

$$M = k\sqrt{L_1L_2}$$

46

Loosely Coupled Circuits

- Coupled impedance is

$$\mathbf{Z}_{in} = \mathbf{Z}_p + \frac{(\omega M)^2}{\mathbf{Z}_s + \mathbf{Z}_L}$$

47

This document was created with Win2PDF available at <http://www.daneprairie.com>.
The unregistered version of Win2PDF is for evaluation or non-commercial use only.