

## Chapter 24

### Three-Phase Systems

## Three-Phase Voltage Generation

- Three-phase generators
  - Three sets of windings and produce three ac voltages
- Windings are placed  $120^\circ$  apart
  - Voltages are three identical sinusoidal voltages  $120^\circ$  apart

## Three-Phase Voltage Generation

- Set of voltages such as these are balanced
- If you know one of the voltages
  - The other two are easily determined

3

## Four-Wire Systems

- Three loads have common return wire called neutral
- If load is balanced
  - Current in the neutral is zero
- Current is small
  - Wire can be smaller or removed
  - Current may not be zero, but it is very small

4

## Four-Wire Systems

- Outgoing lines are called line or phase conductors

5

## Three-Phase Relationships

- Line voltages
  - Voltages between lines either at the generator ( $E_{AB}$ ) or at the load ( $V_{AB}$ )

6

## Three-Phase Relationships

- **Phase voltages**
  - Voltages across phases
    - For a Y load, phases are from line to neutral
    - For  $\Delta$  load, the phases are from line to line

7

## Three-Phase Relationships

- Line currents
  - Currents in line conductors
- Phase currents
  - Currents through phases
  - For a Y load two currents are the same

8

## Voltages in a Wye Circuit

- For a balanced Y system
  - Magnitude of line-to-line voltage is  $\sqrt{3}$  times the magnitude of phase voltage
- Each line-to-line voltage
  - Leads corresponding phase voltage by  $30^\circ$
- Line-to-line voltages form a balanced set

9

## Voltages for a Wye Circuit

- Nominal voltages
  - 120/208-V
  - 277/480-V
  - 347/600-V systems

10

## Voltages for a Wye Circuit

- Given any voltage at a point in a balanced, three-phase Y system
  - Determine remaining five voltages using the formulas

$$\mathbf{V}_{ab} = \sqrt{3}\mathbf{V}_{an} \angle 30^\circ$$

$$\mathbf{E}_{AB} = \sqrt{3}\mathbf{E}_{AN} \angle 30^\circ$$

11

## Currents for a Wye Circuit

- Line currents
  - Same as phase currents
  - $\mathbf{I}_a = \mathbf{V}_{an} / \mathbf{Z}_{an}$
- Line currents form a balanced set
  - If you know one current
    - Determine the other five currents by inspection

12

## Currents for a Delta Load

- In a balanced delta
  - The magnitude of the line current is  $\sqrt{3}$  times the magnitude of the phase current

13

## Currents for a Delta Load

- Each line current lags its corresponding phase current by  $30^\circ$
- For any current in a balanced, three-phase delta load
  - Determine remaining currents by inspection

14

## Power in a Balanced System

- To find total power in a balanced system
  - Determine power in one phase
  - Multiply by three
- Use ac power formulas previously developed

15

## Power in a Balanced System

- Since magnitudes are the same for all three phases, simplified notation may be used

16



## Active Power to a Balanced Wye Load

- $P_{\phi} = V_{\phi} I_{\phi} \cos \theta_{\phi}$
- $P_T = 3P_{\phi} = 3V_{\phi} I_{\phi} \cos \theta_{\phi}$
- $P_T = \sqrt{3} V_L I_L \cos \theta_{\phi}$
- $P_{\phi} = I_{\phi}^2 R_{\phi}$
- $P_T = 3I_{\phi}^2 R_{\phi}$

17

## Reactive Power to a Balanced Wye Load

- $Q_{\phi} = V_{\phi} I_{\phi} \sin \theta_{\phi}$
- $Q_T = \sqrt{3} V_L I_L \sin \theta_{\phi}$
- $Q_{\phi} = I_{\phi}^2 X_{\phi}$
- Units are VARs

18

## Apparent Power to a Balanced Wye Load

- $S_{\phi} = V_{\phi} I_{\phi}$
- $S_T = \sqrt{3} V_L I_L$
- $S_{\phi} = I_{\phi}^2 Z_{\phi}$

19

## Apparent Power to a Balanced Wye Load

- Units are VAs
- Power factor is

$$F_p = \cos \theta_{\phi} = P_T / S_T = P_{\phi} / S_{\phi}$$

20

## Power to a Balanced Delta Load

- Power formulas for  $\Delta$  load are identical to those for Y load
- In all these formulas
  - Angle  $\theta_\phi$  is phase angle of the load impedance

21

## Power to a Balanced Delta Load

- You can also use single-phase equivalent in power calculations
  - Power will be power for just one phase

22

## Measuring Power in Three-Phase Circuits

- Measuring power to a 4-wire Y load requires three wattmeters (one meter per phase)
- Loads may be balanced or unbalanced
- Total power is sum of individual powers

23

## Measuring Power in Three-Phase Circuits

- If load could be guaranteed to be balanced
  - Only one meter would be required
  - Its value multiplied by 3

24

## Measuring Power in Three-Phase Circuits

- For a three-wire system
  - Only two meters are needed
- Loads may be Y or  $\Delta$
- Loads may be balanced or unbalanced
- Total power is algebraic sum of meter readings

25

## Measuring Power in Three-Phase Circuits

- Power factor for a balanced load
  - Obtain from wattmeter readings using a watts ratio curve

$$\tan\theta_{\phi} = \sqrt{3} \left( \frac{P_h - P_{\ell}}{P_h + P_{\ell}} \right)$$

26

## Measuring Power in Three-Phase Circuits

- From this,  $\theta$  can be determined
- Power factor can then be determined from  $\cos \theta$

27

## Unbalanced Loads

- Use Ohm's law
  - For unbalanced four-wire Y systems without line impedance
- Three-wire and four-wire systems with line and neutral impedance
  - Require use of mesh analysis

28

## Unbalanced Loads

- One of the problems with unbalanced loads
  - Different voltages are obtained across each phase of the load and between neutral points

29

## Unbalanced Loads

- Unbalanced four-wire  $\Delta$  systems without line impedance are easily handled
  - Source voltage is applied directly to load
- Three-wire and four-wire systems with line and neutral impedance
  - Require use of mesh analysis

30

## Power System Loads

- Single-phase power
  - Residential and business customers
- Single-phase and three-phase systems
  - Industrial customers
  - Therefore, there is a need to connect both single-phase and three-phase loads to three-phase systems

31

## Power System Loads

- Utility tries to connect one third of its single-phase loads to each phase
- Three-phase loads are generally balanced

32



## Power System Loads

- Real loads
  - Seldom expressed in terms of resistance, capacitance, and inductance
  - Rather, real loads are described in terms of power, power factors, etc.

33

This document was created with Win2PDF available at <http://www.daneprairie.com>.  
The unregistered version of Win2PDF is for evaluation or non-commercial use only.