

## Chapter 30

### Operational Amplifiers


## Introduction

- Characteristics
  - High input impedance
  - Low output impedance
  - High open-loop gain
  - Two inputs
  - One output
  - Usually + and – dc power supplies
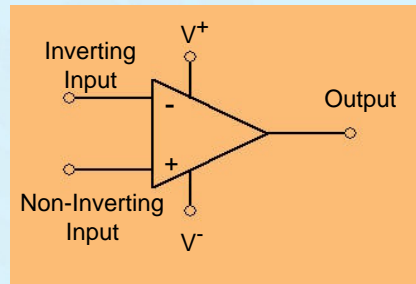
## Introduction

- Ideal Characteristics

- $Z_{in}$  (inverting)  $\approx \infty$
- $Z_{in}$  (non-inverting)  $\approx \infty$
- $Z_{out} \approx 0$
- $A_v \approx \infty$




3
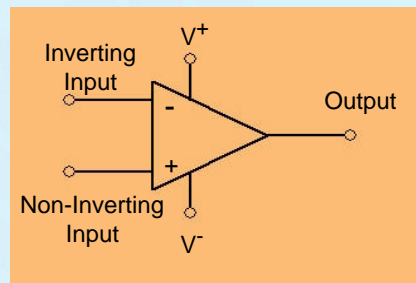
## Introduction

- Uses


- Comparators
- Voltage amplifiers
- Oscillators
- Active filters
- Instrumentation amplifiers



4
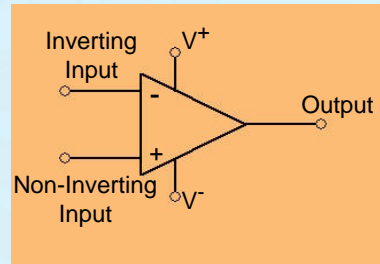
## Introduction

- Single-ended amplifier
  - One input grounded
  - Signal at other input
- Double-ended amplifier/Differential amplifier
  - Signals at both inputs




5

## Differential Amplifier and Common-Mode Signals

- Basic differential amplifier
  - $Q_1$  identical to  $Q_2$
  - $R_{C1} = R_{C2}$
  - $\therefore I_{C1} = I_{C2}$  and emitter currents equal
  - Also,  $I_C \approx I_E$  for high  $\beta$
  - and  $V_{BE} \approx 0.7 \text{ V}$
- Similar calculation of Bias

6
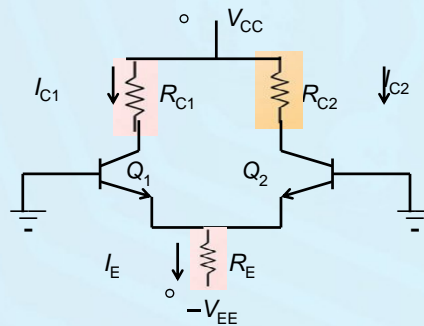
## Differential Amplifier and Common-Mode Signals




7

## Differential Amplifier and Common-Mode Signals

- Apply same signal to both Bases

$$V_{out} = V_{out1} - V_{out2} \approx 0$$

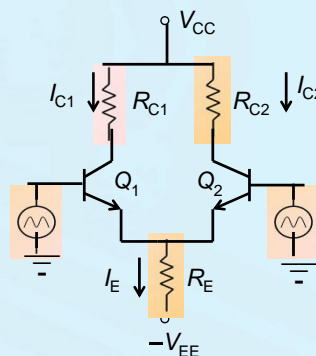
- Eliminates common-mode signals
- 60 Hz
- Noise



8
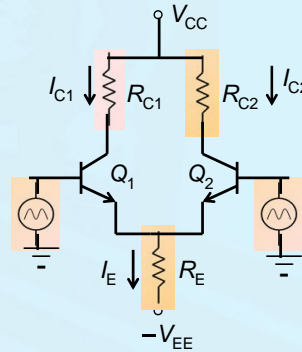
## Differential Amplifier and Common-Mode Signals

- Apply sinusoids to both bases:
  - Same amplitude, 180° difference in phase,
- ∴ if  $V_{in1} = -V_{in2}$   
 $V_{out} = 2V_{in}$



9

## Differential Amplifier and Common-Mode Signals

- Common-mode signals
  - Differential voltage gain

$$A_{vd} = \frac{v_{out}}{v_d}$$

also called open-loop voltage gain

$$20,000 \leq A_v \leq 200,000$$

10

## Differential Amplifier and Common-Mode Signals

- Common-mode signals
  - Common-mode voltage gain

$$A_{vc} = \frac{v_{out}}{v_c}$$

11

## Differential Amplifier and Common-Mode Signals

- Common-mode rejection ratio (CMRR)
  - Equations

$$CMRR = \frac{A_{vd}}{A_{vc}}$$

$$[CMRR]_{db} = 20 \log_{10}(CMRR)$$


- Values

$$70db \leq CMRR \leq 90db$$

12
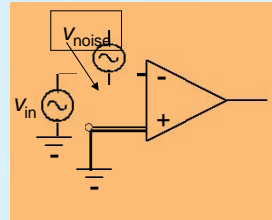
## Differential Amplifier and Common-Mode Signals

- Noise
  - Static in audio signal
  - Increases as signal is amplified
  - Common mode signal
  - Significantly reduced by differential amplifier



13

## Negative Feedback

- Op-amp
  - Large differential, open-loop voltage gain
    - $A_{vol} \approx 100,000$
  - Small input yields saturated output ( $V_{CC}$  or  $V_{EE}$ )

14

## Negative Feedback


- Negative feedback
  - Returns a portion of output signal to the input
  - Open-loop voltage gain decreased

15

## Negative Feedback

- Input impedance still high
- Output impedance low
- Circuit voltage gain,  $A_v$ 
  - Adjustable
  - Stable

$$A_v = \frac{V_{out}}{V_{in}}$$

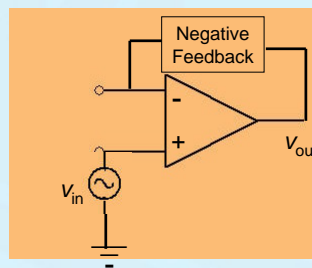


16



## Inverting Amplifier

- Basic circuit

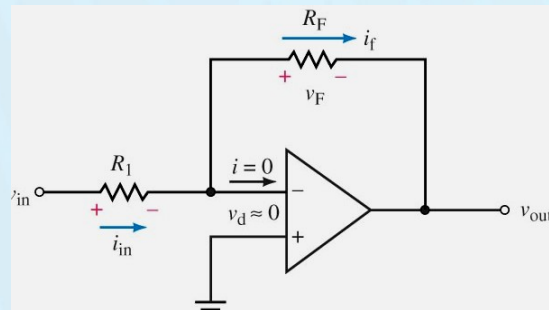

17

## Inverting Amplifier

- Output  $180^\circ$  out of phase with input
- Significant decrease in gain
  - Gain now called closed-loop voltage gain
- Output impedance  $\approx 0$
- $v_d \approx 0$

18

## Inverting Amplifier

- Inverting input at virtual ground,  $v_{in(-)} \approx 0$
- $i_{in}$  to op-amp  $\approx 0$
- Input current only dependent on  $v_{in}$  and  $R_1$
- $A_{vcl}$  only dependent on input resistor and feedback resistor

$$i_{in} = \frac{v_{in}}{R_1}$$

$$A_{vcl} = \frac{v_{out}}{v_{in}} = -\frac{i_{in} R_F}{i_{in} R_1}$$

$$A_{vcl} = -\frac{R_F}{R_1}$$

19

## Inverting Amplifier


- Model

$$v_d \approx 0$$

$$R_{in} \approx \infty$$

$$i_{in} = i_f$$

$$z_{in} \approx R_1$$

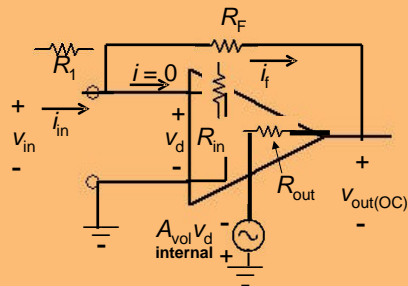


## Inverting Amplifier

- Low output impedance


$$Z_{out} = \frac{V_{out(OC)}}{i_{out(SC)}}$$
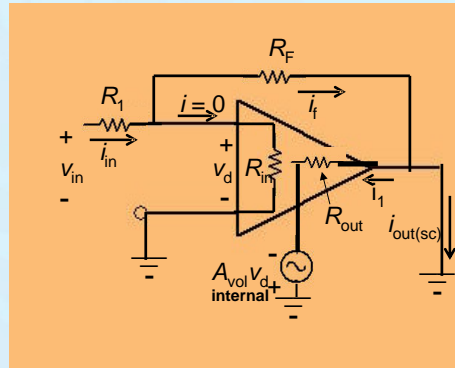
$$Z_{out} = (1 - A_{vcl}) \left( \frac{R_{out}}{A_{vol}} \right)$$



## Non-Inverting Amplifier

- Circuit

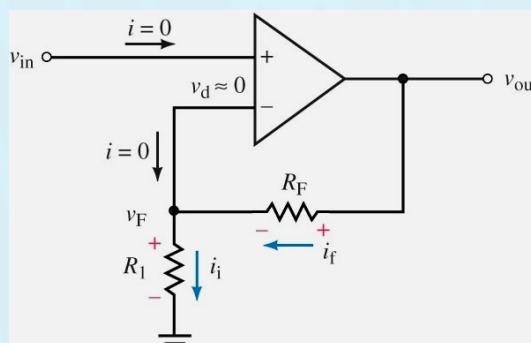

## The Non-Inverting Amplifier

- Very high input impedance
- Voltage gain related to the two resistors
- Very low output impedance
- Excellent buffer

23

## Non-Inverting Amplifier

- Differential voltage
  - $v_d \approx 0$
- Input current to op-amp
  - $i = 0$
- Closed-loop voltage gain ( $A_{vcl}$ ) is a resistor ratio

24

## Non-Inverting Amplifier

$$A_v = \frac{v_{out}}{v_{in}}$$

$$A_v = \frac{R_F i_F + R_1 i_F}{R_1 i_F}$$

$$A_{vcl} = \frac{R_F}{R_1} + 1$$


25

## Non-Inverting Amplifier

- Model
- Input impedance

$$i_{in} = \frac{v_d}{R_{in}}$$
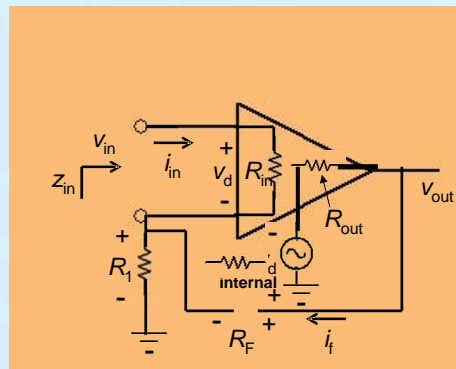
$$z_{in} = \left( 1 + \frac{A_{vol}}{A_{vcl}} \right) R_{in}$$




## Non-Inverting Amplifier

- Model
- Output impedance

$$i_{out(sc)} = i_2 + i_f$$
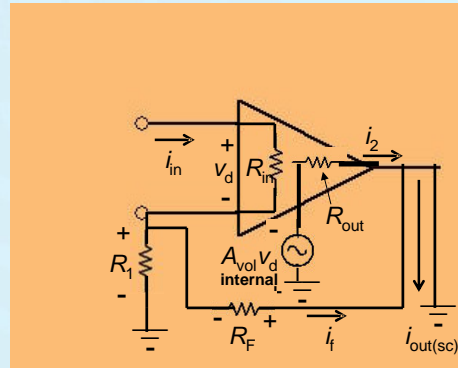
$$z_{out} = \left( \frac{A_{vcl}}{A_{vol}} \right) R_{out}$$




## Non-Inverting Amplifier

- Very high  $z_{in}$
- Very low  $z_{out}$
- Good buffer circuit
- Also called voltage follower (gain = 1)
- Or adjustable gain  $> 1$
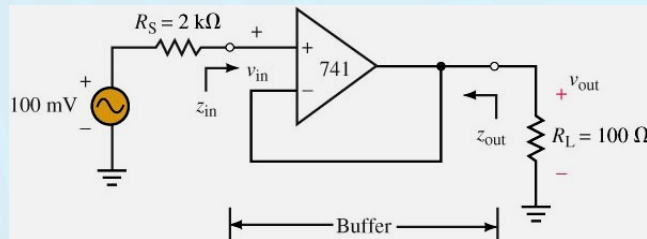
## Non-Inverting Amplifier

- Voltage Follower Buffer Circuit
  - Gain = 1
  - High impedance source drives low impedance load



29

## Op-Amp Specifications

- LM 741 series
  - Inexpensive
  - Widely used
  - Good general specifications
  - Characteristic of all op-amp specifications
- Provide Minimum, Typical, and Maximum ratings

30

## Op-Amp Specifications

- Input Offset Voltage,  $V_{io}$ 
  - LM741C,  $V_{io}$  typical is 2 millivolts
  - Model is voltage source with value,  $V_{io}$  in series with + input

31

## Op-Amp Specifications

- Input Offset Voltage,  $V_{io}$ 
  - Without feedback this would saturate output with no input
  - With negative feedback, output due to  $V_{io}$  is closed-loop gain times  $V_{io}$

32



## Op-Amp Specifications

- Input Offset Current,  $I_{OS}$
- $I_{OS}$  = Difference between bias currents at + and – inputs of op-amp
- 741C typical  $I_{OS}$  is 20 nanoamps
- Multiplying resistor used to measure  $I_{OS}$

33

## Op-Amp Specifications

- Input Resistance
  - 741C: minimum = .3 M $\Omega$ , typical = 2 M $\Omega$
- Open-Loop Voltage gain ( $A_{VOL}$ )
  - 741C:  $A_{VOL}$  = Large Signal Voltage Gain
    - minimum = 20,000, typical = 200,000
  - Closely related to Bandwidth,  $BW$

34


## Op-Amp Specifications

- Gain-bandwidth product  
– 741C = 1,000,000 =  $10^6$  MHz

35

## Op-Amp Specifications

- Gain versus frequency curve for op-amp

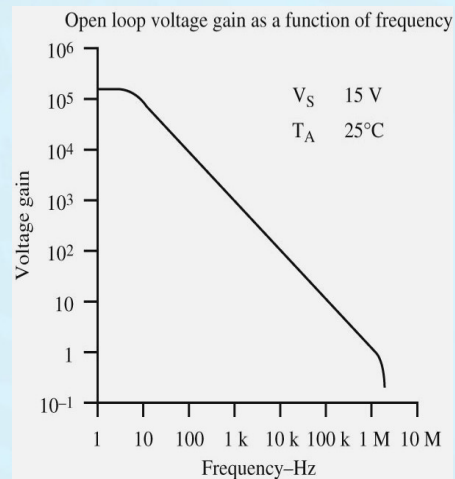

36

## Op-Amp Specifications

- Slew rate
  - Maximum rate of change of output voltage

$$\text{Slew Rate} = \frac{\Delta V}{\Delta t}$$

- 741C maximum slew rate = 0.5 V/  $\mu$  sec

37

## Op-Amp Specifications

- Fastest time for output to go from 0 to 10 volts is 20  $\mu$  sec
- Can distort waveforms that have too fast a rise time

38

## Op-Amp Specifications

- Slew rate required for Sinusoid with frequency  $f$  and amplitude  $A$
- Maximum amplitude of a sine wave with frequency  $f$  for a given slew rate

$$v = A \sin(\omega t)$$

$$\frac{dv}{dt} = \omega A \cos(\omega t)$$

$$\text{slew rate} = 2\pi f A$$


$$f_{\max} = \frac{\text{slew rate}}{2\pi A}$$

$$A_{\max} = \frac{\text{slew rate}}{2\pi f}$$

39
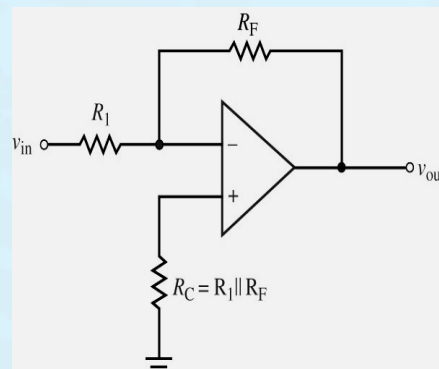
## Op-Amp Specifications

- Bias Compensation: use  $R_C = R_1 \parallel R_F$



40

## Troubleshooting an Op-Amp Circuit

- Problems occur when circuit is first built
- Most important
  - Correct connection of dual power supply
- Connecting a – supply to a + input (or vice versa) can burn out an op-amp
- Single earth ground
- Short connecting wires

41

This document was created with Win2PDF available at <http://www.daneprairie.com>.  
The unregistered version of Win2PDF is for evaluation or non-commercial use only.