

## Chapter 31

### Applications of Op-Amps

## Comparators

- Op-amp as a Comparator
  - No negative feedback
  - Output saturates with very small + or – input


## Comparators

- Comparator
  - Non-linear device
  - $v_{out}$  has two discrete values,  $\pm V_{SAT}$
  - $v_{out} = +V_{SAT}$  if + input is greater than – input
  - $v_{out} = -V_{SAT}$  if – input is greater than + input

3
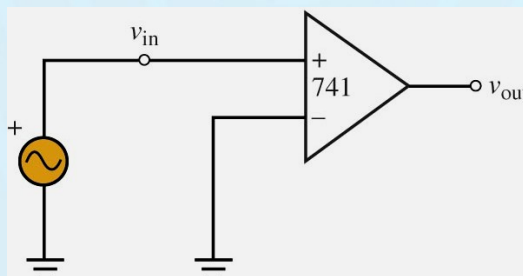
## Comparators


- A comparator circuit: Sine wave in, square wave out



4
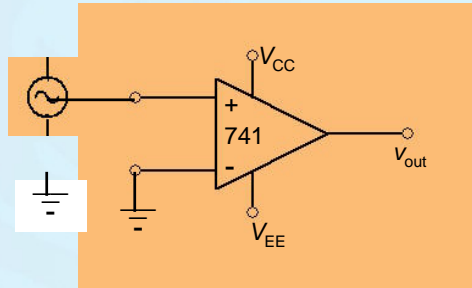
## Comparators

- Input sine wave
- Output square wave  $V_{out} = \pm V_{SAT}$
- $+V_{SAT}$  (determined by  $V_{CC}$ ) when sinusoid is +
- $-V_{SAT}$  (determined by  $V_{EE}$ ) when sinusoid is -



5


## Comparators

- Compare input waveform to reference
- Reference can be ground or dc source
- Can compare two waveforms
- Specialized comparator IC's also available
- Detects when waveform reaches given level

6

## Comparators


- Zero-Crossing Detector

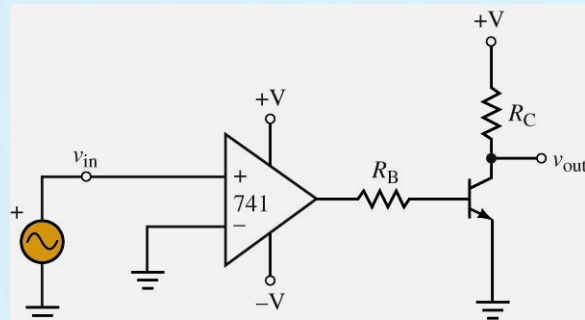

7

## Voltage Summing Amplifier

- Circuit

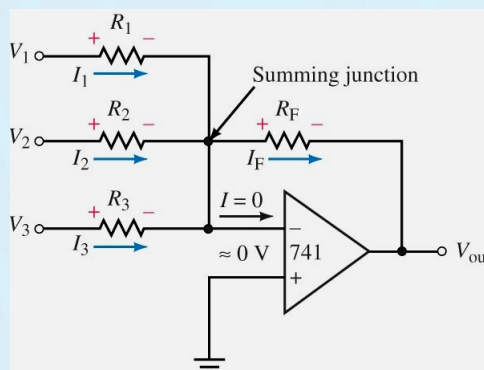

8

## Voltage Summing Amplifier

- Inverse sum

$$I_F = I_1 + I_2 + I_3$$

$$V_{out} = -I_f R_f$$

$$\frac{R_F}{R_1}$$

9

## Voltage Summing Amplifier

- Multiplies each input by

$$V_{out} = -\left(\frac{R_F}{R_1}V_1 + \frac{R_F}{R_2}V_2 + \frac{R_F}{R_3}V_3\right)$$


10

## Integrators and Differentiators

- In general

$$v_{\text{out}} = -\frac{Z_F}{Z_1} v_{\text{in}}$$

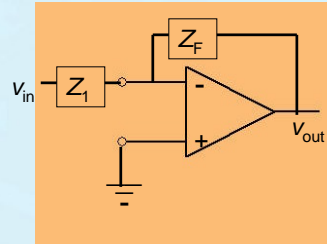- Using resistors and capacitors
  - Integrators
  - Differentiators



11

## Integrators and Differentiators

- Voltage across capacitor

$$v_C(t) = \frac{1}{C} \int_0^t i(t) dt + V_0$$

- Current through capacitor

$$i_C(t) = C \frac{dv_C}{dt}$$


12

## Integrators and Differentiators

- Op-amp Integrator

$$v_C(t) = \frac{1}{R_1 C} \int_0^t v_{in}(t) dt + V_0$$
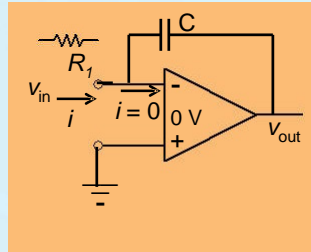
$$v_{out}(t) = \frac{1}{R_1 C} \int_0^t v_{in}(t) dt$$




13

## Integrators and Differentiators

- Op-amp differentiator

$$v_{out}(t) = -R_F C \frac{dv_{in}}{dt}$$


- Circuit inherently unstable

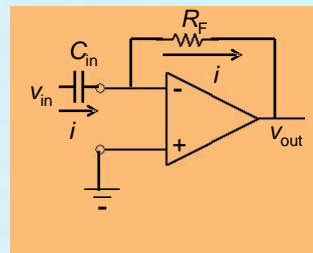

14

## Integrators and Differentiators

- Stable op-amp differentiator

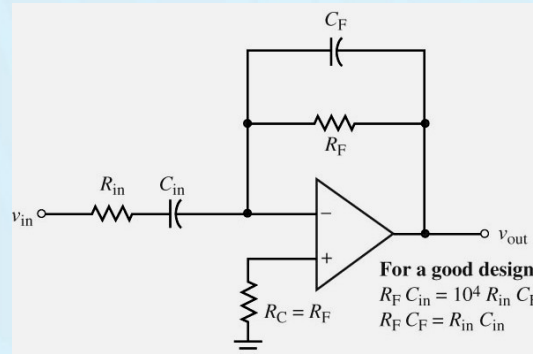

15

## Instrumentation Amplifiers


- Op-amp in differential amplifier configuration
- Noise suppression
- High CMRR
- Reasonable gain
- IC instrumentation amps

16



## Instrumentation Amplifiers

- An op-amp instrumentation amp circuit

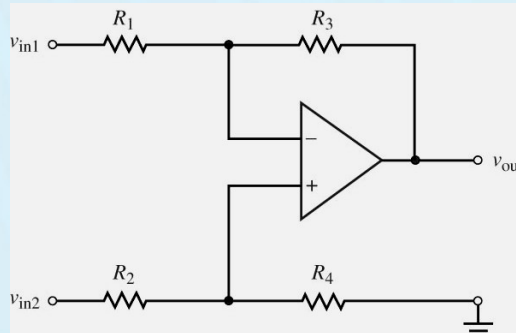

17

## Instrumentation Amplifiers

- Measurement of very small voltages
- Transducer
  - Converts a physical change into an electrical change

18

## Instrumentation Amplifiers

- Strain gage
  - Converts force into  $\Delta R$
  - $\Delta R$  is milliohms
  - Use bridge circuit

19

## Instrumentation Amplifiers

- Strain gage example
  - Thin metal foil (resistor) on plastic backing
  - Glued to metal bar
  - Bar subjected to tension and compression

20

## Instrumentation Amplifiers

- Strain gage example
  - Tension
    - Resistance of strain gage is  $R + \Delta R$
  - Compression
    - Resistance of strain gage is  $R - \Delta R$

21

## Active Filters

- Basic filter types
  - Passive elements, gain  $< 1$
  - Low-pass
  - High-pass
  - Bandpass
  - Band reject

22

## Active Filters

- With op-amps/active filters
  - Gain can be  $\geq 1$
  - Filter response closer to ideal

23


## Active Filters

- Low-pass ( $R_F = R_1$ )

$$v_{out} = v_C = \frac{Z_C}{R_1 + Z_C} v_{in} = \frac{1}{R_1 + \frac{1}{j\omega C}} v_{in}$$

$$TF(j\omega) = \frac{1}{1 + j\omega R_1 C}$$

- Add resistor for gain  $> 1$

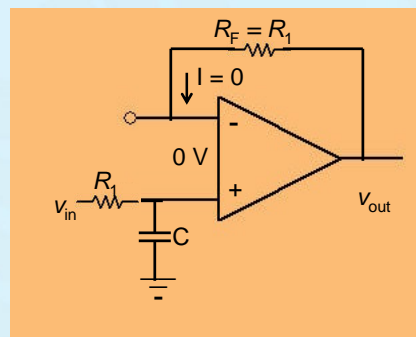

24


## Active Filters

- High-pass ( $R_F = R_1$ )

$$v_{out} = v_R = \frac{R_1}{R_1 + Z_C} v_{in} = \frac{R_1}{R_1 + \frac{1}{j\omega C}} v_{in}$$

$$TF(j\omega) = \frac{R_1 C}{1 + j\omega R_1 C}$$

- Add resistor for gain > 1

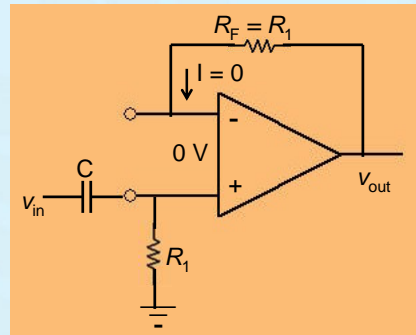

25

## Active Filters

- dc gain
  - Easily achieved
  - Not used much due to gain-bandwidth product
- Example
  - GBWP =  $10^6$ , Gain = 10
  - Cutoff for filter (HP or LP) only  $10^5$

26

## Active Filters

- Bandpass
- Wideband
  - Cascade HP and LP active filters
  - LP must have higher cutoff frequency
  - HP and LP cutoff frequencies far apart
- Narrowband
  - Can use single op-amp


27

## Active Filters

- Narrowband BP circuit

$$f_0 = \frac{0.1125}{RC} \sqrt{1 + \frac{R}{R_1}}$$

$$BW = \frac{0.1591}{RC}$$

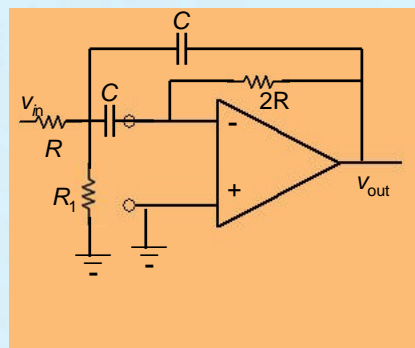

28

## Active Filters

- Active notch filter
  - Cascade narrowband BP filter
  - Adder circuit
  - Result is  $1 - (\text{frequency response of BP filter})$
  - Frequency at resonant frequency of BP filter will be eliminated

29

## Voltage Regulation

- Voltage regulator
  - Constant voltage to load
  - Specified current range
  - Specified input voltage range
  - Zener diode regulator
    - Inefficient
    - Dissipates power

30

## Voltage Regulation


- Types of regulators
  - Fixed voltage regulator
  - Variable voltage regulator
  - Switching regulator
- Specialized IC regulators
  - For different voltages, e.g. +5 V, –5 V, +12 V, –12 V, +15 V, –15 V, etc.

31
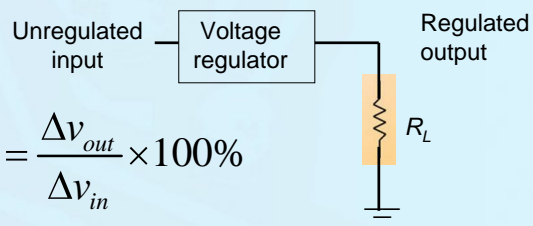
## Voltage Regulation

- Line Regulation
  - Small output change with change in input

$$\% \text{ line regulation} = \frac{\Delta v_{out}}{\Delta v_{in}} \times 100\%$$



32



## Voltage Regulation

- Load regulation
  - Small output voltage change with smaller  $R_L$


$$\% \text{ load regulation} = \frac{V_{NL} - V_{FL}}{V_{FL}} \times 100\%$$

- $V_{NL}$  = no-load voltage (open-circuit load)
- $V_{FL}$  = full-load voltage (specified by manufacturer)

33
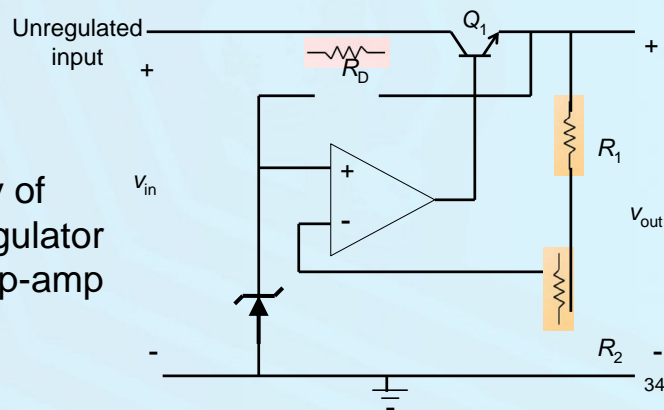
## Voltage Regulation


- Circuit to increase efficiency of Zener regulator with an op-amp




34
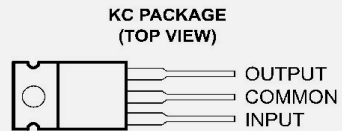
## Voltage Regulation

- Three-terminal IC regulators
  - 7800 series, positive voltage
  - 7900 series, negative voltage



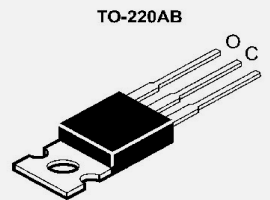
The COMMON terminal is in electrical contact with the mounting base.



35
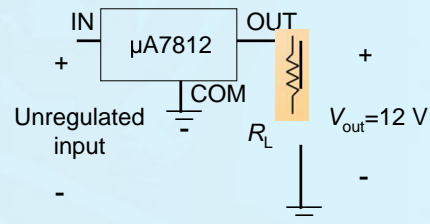
## Voltage Regulation

- 5 V output, 7805
- 12 V output, 7812
- –5 V output, 7905
- –12 V output, 7912



36

## Voltage Regulation

- Ripple
- Greatly reduced by IC regulator

$$[\textit{ripple rejection}]_{dB} = 20 \log \frac{V_{r(in)}}{V_{r(out)}}$$

$V_{r(in)}$  = input ripple voltage

$V_{r(out)}$  = output ripple voltage

37

This document was created with Win2PDF available at <http://www.daneprairie.com>.  
The unregistered version of Win2PDF is for evaluation or non-commercial use only.