

Chapter 33

Thyristors and Optical Devices

Introduction to Thyristors

- Thyristors
 - Switch
 - On-state, off-state
 - Unilateral or bilateral
 - Latching
 - High power

Introduction to Thyristors


- Thyristors
 - Sinusoidal
 - Firing angle
 - Conduction angle

3

Triggering Devices

- Used to pulse switching devices
- Diac
 - 3-layer
 - Bi-directional conduction
 - Breakover voltage
 - Blocking region

Symbols

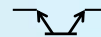


4

Triggering Devices

- Unijunction Transistor (UJT)
 - 3-terminal device
 - Intrinsic standoff ratio
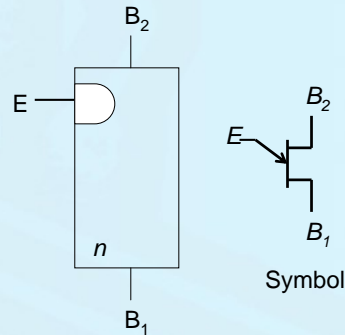
$$\eta = \frac{R_{B1}}{R_{B1} + R_{B2}} = \frac{R_{B1}}{R_{BB}}$$



5

Triggering Devices

- UJT
 - $0.5 < \eta < 0.9$
 - Emitter region heavily doped
 - $V_E - B_1 = 0$, *p-n* junction reverse biased
 - Increase $V_E - B_1$, reach peak point (maximum current)

6

Triggering Devices

- UJT
 - Continue increase, reach valley point
 - Further increase $V_E - B_1$, UJT is saturated


7

Triggering Devices

- UJT relaxation oscillator

$$T = R_E C_E \ln \left(\frac{1}{1 - \eta} \right)$$

$$f = \frac{1}{T}$$

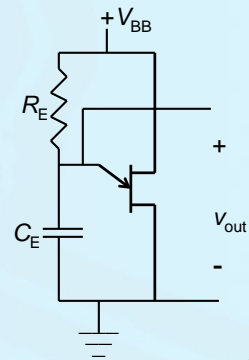

8

Silicon Controlled Rectifiers (SCRs)

- 4-layer device, $p-n-p-n$
- Anode (A)
 - Cathode (K)
 - Gate (G)
- Unidirectional


9

Silicon Controlled Rectifiers (SCRs)

- High-power (I up to 2500 A, V up to 2500 V)
- Phase control
- Small V_{AK} when On

10

SCRs

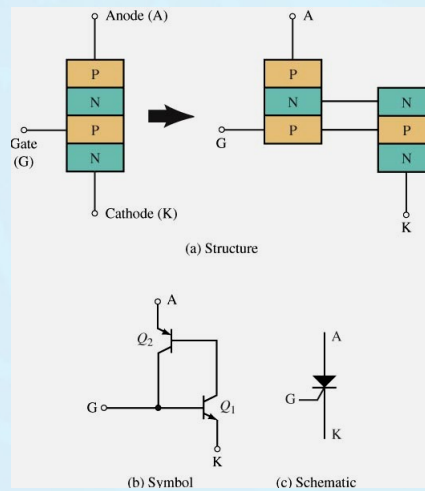

11

SCRs

- Operation
 - $I_G = 0$, no anode current
 - $I_G > I_{GT} \rightarrow$ regenerative feedback \rightarrow high I_{AK}
 - $I_{AK} < I_H \rightarrow$ turn off $\rightarrow I_{AK} = 0$

12

SCRs

- Can cause SCR turn-on
 - High temperature
 - High $\Delta V/\Delta t$ (noise)
 - Radiation

13


SCRs

- Specifications
 - V_{DRM} or V_{RRM} Peak Repetitive Off-state Voltage
 - $I_{\text{T(RMS)}}$ On-State RMS current (maximum)
 - I_{TSM} Peak Non-Repetitive Surge current
 - I_{GT} Gate trigger current
 - I_{L} Latching current
 - I_{H} Holding current

14

SCRs

- SCR phase control

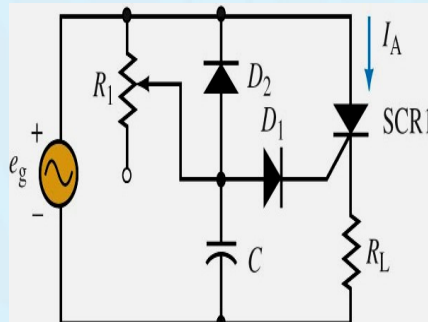

15

SCRs

- Small R_1
 - Short RC time constant
 - SCR turns on rapidly, close to 0°
- Large R_1
 - long RC time constant
 - SCR turns on slowly, close to 180°

16


SCRs

- Too large R_1
 - SCR does not turn on

17

Triacs

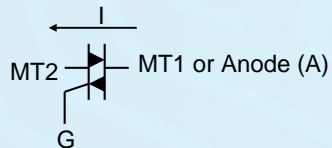- 3-terminal switch
- Bi-directional current
- Symbol



- Gate trigger may be either + or – pulse

18

Triacs

- Characteristics
 - Direct replacement for mechanical relays
 - Trigger circuit for full-wave control
 - 4 modes
 - Remains on in either direction until $I < I_H$
 - Blocking region, $I \approx \mu$ amps
 - Small voltage across Triac when On

19


Triacs

- Specifications
 - Similar to SCR
 - P_{GM} Peak Gate Power
 - $P_{G(AV)}$ Average Gate Power
 - V_{GM} Peak Gate Voltage
 - V_{GT} Gate trigger voltage
 - t_{gt} Turn-On Time

20

Triacs

- Phase control light dimmer

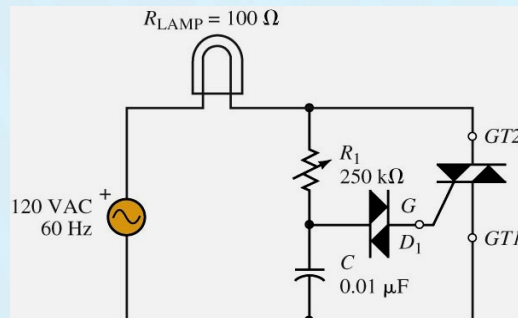

21

Triacs

- Circuit operation
 - Turn-off due to small load current
 - Capacitor charges/discharges through load
 - DIAC is bi-directional
 - RC time constant $\rightarrow 0^\circ$ to 180° turn on in each direction

22

Power Control Fundamentals

- Review equations
- Control
 - Lamp intensity
 - Heat from a resistive heater
 - Speed of a motor

23

Power Control Fundamentals

$$P = \frac{V_{rms}^2}{R}$$

$$V_{rms} = \sqrt{\frac{\int_0^T [V(t)]^2 dt}{T}}$$

$$V_{rms(FW)} = \frac{V}{\sqrt{2}} \quad V_{rms(HW)} = \frac{V}{2}$$

24

Power Control Fundamentals

- Delayed turn-on, full-wave signal

$$V_{rms(FW)} = \sqrt{\frac{\int_{\theta_F}^T [V \sin \theta]^2 d\theta}{\pi}}$$


- Delayed turn-on, half-wave signal

$$V_{rms(HW)} = \sqrt{\frac{\int_{\theta_F}^{\pi} [V \sin \theta]^2 d\theta}{2\pi}}$$

25

Power Control Fundamentals

- V and P curves for full-wave control

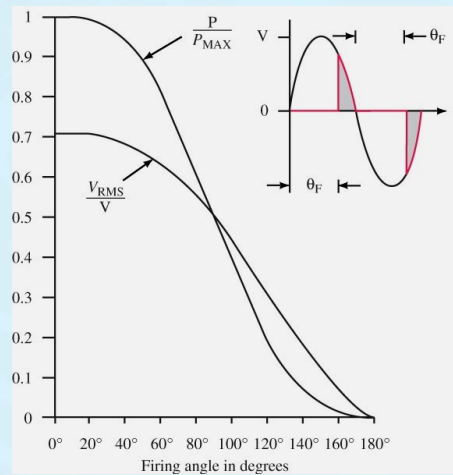

26

Introduction to Optical Devices

- Opto-electronic devices wavelength
 - Current → light
 - Light → current
 - c = speed of light in a vacuum
 - c = 3×10^8 m/s

$$\lambda = \frac{c}{f}$$

27

Introduction to Optical Devices

- Electromagnetic spectrum
 - Visible ($380 < \lambda \text{ (nm)} < 750$)
 - Infrared region ($750 < \lambda \text{ (nm)} < 1000$)

$$1 \text{ \AA} = 1 \times 10^{-10} \text{ m} = 0.1 \text{ nm}$$

28

Introduction to Optical Devices

- LED is a diode
 - When forward biased
 - Electron-hole recombination energy
 - Photons released: $E = hf$, h is Planck's constant
 - $h = 6.626 \times 10^{-34}$ Joules · seconds
 - High energy → visible spectrum
 - Lower energy → IR spectrum

29

Introduction to Optical Devices

- LED advantages
 - Low voltage
 - Rapid change in light output with input V change
 - Long life
 - LED output can be matched to photodetector

30

Introduction to Optical Devices

- LED disadvantages
 - Easily damaged
 - Brightness dependent on temperature
 - Chromatic dispersion
 - Inefficient compared to LCDs

31

Photodetectors

- R varies with light intensity
 - Photoresistors
- Voltage or current varies with light intensity
 - Photodiodes
 - Phototransistors
 - Light-Activated SCRs (LASCRs)

32


Photodetectors

- Photodiodes
 - Reverse biased
 - Low ambient light → very small current, I_D (small leakage current)
 - High ambient light → increased current, I_D (increase in minority carriers)

33

Photodetectors

- Photodiodes
 - Symbol

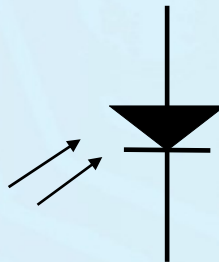

34

Photodetectors

- Phototransistor
 - Base open
 - Light on reverse-biased CB junction
 - Increase minority carriers
 - Increase I_C

35

Photodetectors

- Phototransistor
 - Usually used as a switch
 - Off $\rightarrow I_C = 0$
 - On $\rightarrow I_C > 0$



36

Photodetectors

- LASCR
 - Light-Activated SCR or photo-SCR
 - Symbol
 - Light turns LASCR on
 - Open gate or resistor on gate to control sensitivity



37

Optocouplers

- Couple two circuits
 - LED and Photodetector in single circuit
- Electrical isolation
 - Medical equipment
 - High voltage circuit to digital circuit

38


Optocouplers

- Use as
 - Linear device
 - Digital buffer

39

Optocouplers

- Phototransistor optocoupler

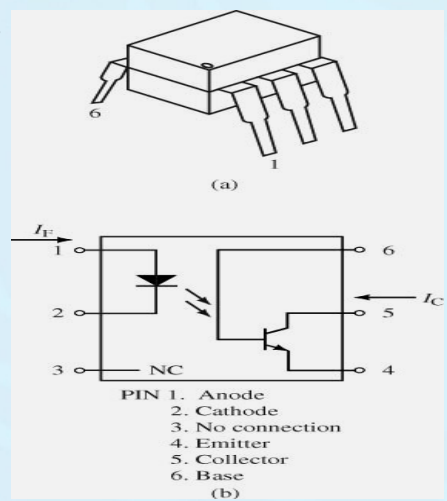

40

Optocouplers

- Current transfer ratio
- $0.1 < \text{CTR} < 1$

$$\text{CTR} = \frac{I_C}{I_F}$$

41

Optocouplers

- Operation
 - High diode current in input circuit yields
 - High diode light output which yields
 - High collector current in output circuit

42

Semiconductor LASERS

- Light Amplification through Stimulated Emission of Radiation
- Operation
 - Similar to LEDs
 - Monochromatic (same frequency)
 - Coherent (same phase) output
 - Small pulse dispersion

43

This document was created with Win2PDF available at <http://www.daneprairie.com>.
The unregistered version of Win2PDF is for evaluation or non-commercial use only.